Some of you may already have the optional Yaesu FIF-232 interface in which case you should be almost ready to go. However for those of you that don't here is a little background information and a few ideas.

The C.A.T. interface on the back of the FT990 provides TTL level serial data. As your Macintosh uses RS-232 levels we need to do some form of voltage conversion between TTL and RS232. As it turns out this is a lot easier than you might think.

I personally would recommend using the MAX232 chip. This is really a very clever little device. From a single + 5 volt supply it will provide full TTL <> RS232 conversion including the -12 and +12 lines. It is also capable of providing full handshaking however as the FT990 does not use any form of handshaking we don't need to worry about that.

See "Interface Diagram," in the help menu for the circut diagram.

The only thing we really need to think about is where to get the +5 volts supply line from. Well you could always use the 13.8 volts available from pin 7 of the REMOTE socket on the back of the rig. In case you are worried about this Yaesu list pin 7 of the REMOTE socket for been used to power an external device. Put a 5 volt regulator between the rig and the interface. It's also a good idea to place a fuse in this line as the rig can only supply 200mA. To recap, make sure it's fused, a 100mA fuse should do it, make sure you use a 5 volt regulator.

If you feel a little nervous about taking power from the rig try this. Get a battery holder, one that will take three AA batteries and connect that to the interface. Yes I know this will only supply 4.5 volts to the interface but to be honest it's what I'm using right now and it works just fine, of course if does mean that you will have to change the batteries every now and then.

Maplin Electronics here in the U.K sell a RS232 to TTL converter kit complete with PCB and all parts,

details are,

Maplin Electronics, Telephone 24 hour sales line. (0702) 554161

Order	Code	Type		Price
LM75S	RS232/TTL	Converter	Full Kit	£10.75
GD93B	RS232/TTL	Converter	PCB only	£3.25
AM10L	RS232/TTL	Converter	Fully Assembled	£14.95

## \*NOTE,

I WILL NOT BE HELD RESPONSIBLE FOR ANY DAMAGE IN ANY WAY WHAT-SO-EVER CAUSED TO EITHER PERSON OR EOUIPMENT!

These are the pin/wiring details for the FT990 <> Maplin Interface <> Macinotsh. However if you use or build a different interface you should be able to use the data line names as reference.

FT990 pin	#	Maplin pin #	(TTL side)
1	Ground	4	Ground
2	TX Data	5	RX Data
3	RX Data	2	TX Data

One last thing, I have built a couple of different interfaces for use with this stack and found the same problem with all of them. The data output from my FT990 seems to be a little on the shy side in terms of voltage swing (+ 5v to 0v). I have found that the use of a 1K pull-down resistor between the TX data line from the transceiver and Ground solved this problem. I usually build this into the interface and have included it into the interface diagram.