

//

|= =|

|= Advanced Pearl Box =|

|= 07/01/89 (APB) 07/01/89 =|

|= Tested and Created by: Dispater =|

|= =|

//

INTRO: After reading the fucked up shit on the original pearl box, I decided that there was an easier and cheaper way of doing the same thing with an IC and parts you probably have just laying around the house.

PARTS: CD4049 RCA integrated circuit

.1 uF disk capacitor

1 uF 16V electrolytic capacitor

1K resistor

10K resistor

1meg pot

1N914 diode

some SPST momentary pushbutton switches


9 Volt battery & clip

and miscalanious shit you should have laying around the house.

STATE-OF-THE-ART-NEATO TEXT SCHEMATIC:

correct


*This Schematic was salvaged and is

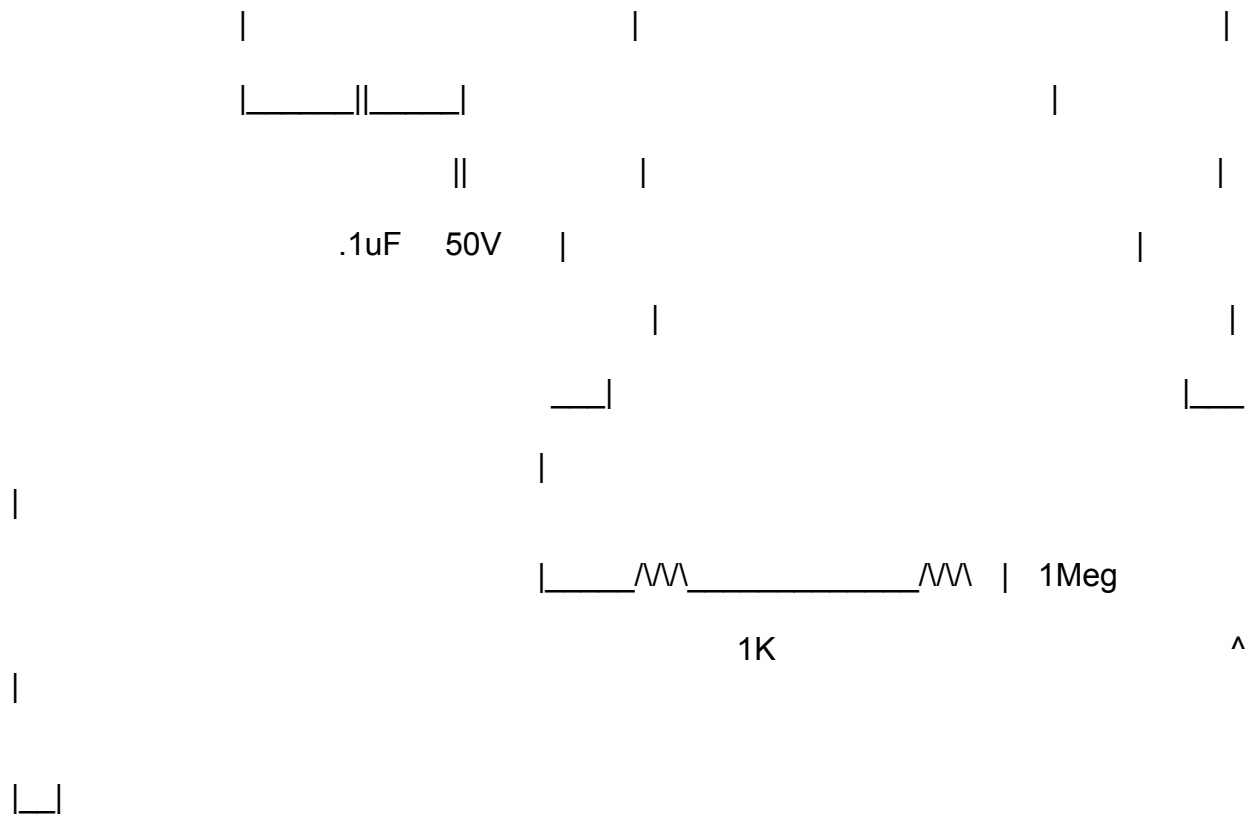

EXTRAS:

To keep tones that you wanna use frequently like 1850 Hz then all you have to do is put in a variable resistor and adjust it to where you have the correct tone, then just put a push-putton switch on the line.

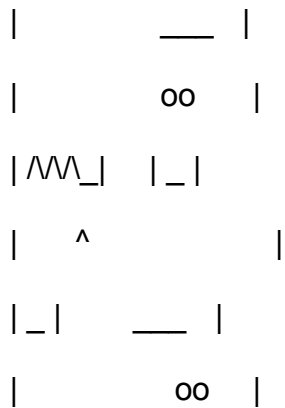You can link them together in a chain, etc.



| ^ ^ _ | | _ |

| ^ |

| _ | |

! | !

: (etc) :

There are many other good mods to make to the box so have phun and be smart.