

=====


- C1, C2:.....5mf or .5uf ceramic disk capacitors
- Q1:.....NPN transistor (2N2222 works best)
- S1:.....Normally open momentary SPST switch
- S2:.....SPST toggle switch
- B1:.....Standard 9-Volt battery
- R1:.....Single turn, 50k potentiometer
- R2:..... " " 100k potentiometer
- [R3:..... " " 500k potentiometer
- R4:..... " " 1meg potentiometer
- SPKR:.....Standard 8-ohm speaker
- T1:.....Mini transformer (8-ohm works best)
- Misc:.....Wire, solder, soldering iron, PC board or perfboard, box to
contain the completed unit, battery clip


Instructions for building The Pearl Box:

=====

Since the instruction are EXTREMELY diffucult to explain in words, you will be given a schematic instead. It will be quite diffucult to follow but try it any way. There is also a Hi-Res picture you can get that shows the schematic in great detail.

(Schematic for The Pearl Box)

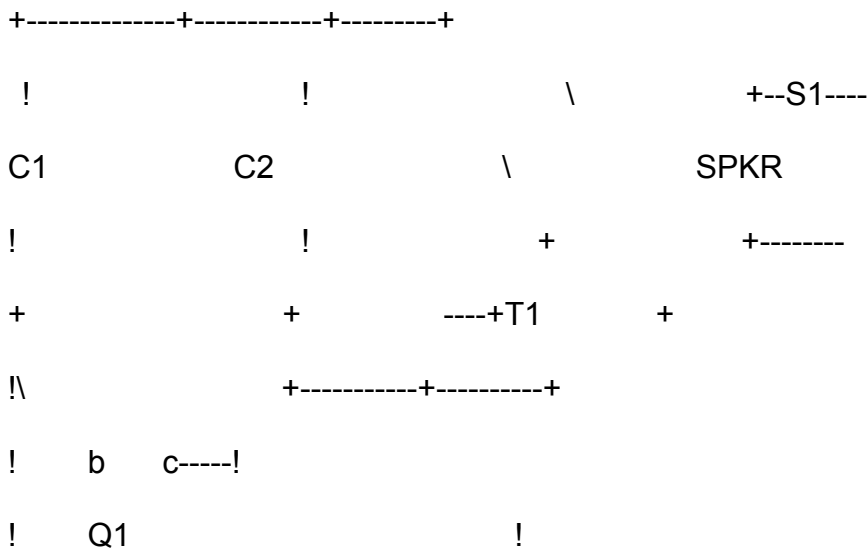

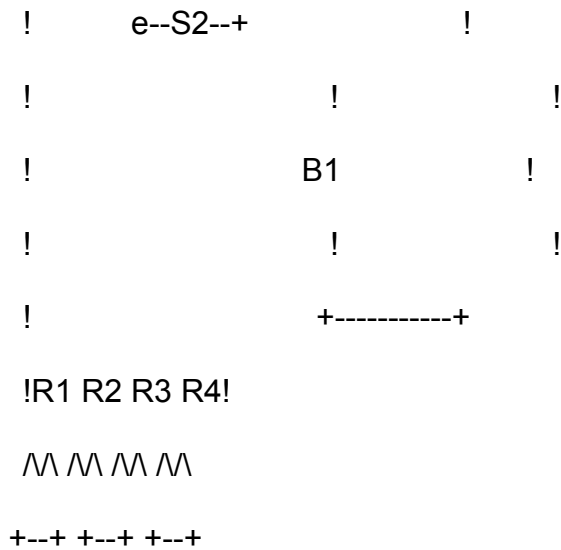

*again as good as it gets

Now that you are probably thoroughly confused, let me explain a few minor details. The potentiometer area is rigged so that the left pole is connected to the center pole of the potentiometer next to it. The middle terminal of T1 is connected to the piece of wire that runs down to the end of the battery.

Correct operation of The Pearl Box:
 =====

You may want to get some dry-transfer decals at Radio Shack to make this job a lot easier. Also, some knobs for the tops of the potentiometers may be useful too. Use the decals to calibrate the knobs.

R1 is the knob for the ones place, R2 is for the tens place, R3 is for the hundreds place and R4 is for the thousands place. S1 is for producing the tones and S2 is for power.

Step 1: Turn on the power and adjust the knobs for the desired tone.

(Example: For 2600 hz- R1=0:R2=0:R3=6:R4=2)

Step 2: Hit the pushbutton switch and VWALA! You have the tone. If you don't have a tone recheck all connections and schematic.

The Lunatic Phringe BBS

312-965-3677 3/12/24 x100 Baud