

Materials you will need

- (1) 9 volt battery with battery clip
 - (1) 25-mfd, 15 volt electrolytic capacitor
 - (2) .0047 mfd capacitors
 - [(1) .022 mfd capacitor
 - (1) 51 pf capacitor
 - (1) 365 pf variable capacitor
 - (1) Transistor antenna coil
 - (1) 2N366 transistor
 - (1) 2N464 transistor
 - (1) 100k resistor
 - (1) 5.6k resistor
 - (1) 10k resistor
 - (1) 2meg potentiometer with SPST switch
- Some good wire, solder, soldering iron, board to put it on, box (optional)


Schematic for The Lunch Box

[This may get a tad confusing but just print it out and pay attention.]

```

[!]
!
51 pf
!
---+--- -----base collector
!      )(          2N366      +---+---//---GND
365 pf  ()          emitter      !
!      )(          !          !
+----- ---+---      !          !
!          ! !          !          !
GND          / .022mfd !          !
          10k\ !          !          !
          / GND      +-----emitter
[          !          !          !          2N464
          /          .0047      !          base collector
2meg \---+          !          ! +-----+          !
          /          !          GND      ! !          !
          GND          ! !          !
+-----+.0047+-----+          !          !
          !          +--25mfd---+
          -----+          !          !
microphone          +--//---+
          -----+ 100k          !

```

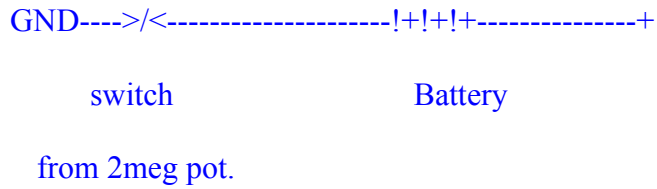

!

[

Notes about the schematic

=====

1. GND means ground
2. The GND near the switch and the GND by the 2meg potentiometer should be connected
3. Where you see:)(

 ()

)(it is the transistor antenna coil with 15 turns of

 regular hook-up wire around it.
4. The middle of the loop on the left side (the left of "()") you should run a wire down to the "+" which has nothing attached to it. There is a .0047 capacitor on the correct piece of wire.
5. For the microphone use a magnetic earphone (1k to 2k).
- [6. Where you see "[!]" is the antenna. Use about 8 feet of wire to broadcast approx 300ft. Part 15 of the FCC rules and regulation says you can't broadcast over 300 feet without a license. (Hahaha). Use more wire for an

antenna for longer distances. (Attach it to the black wire on the fone line for about a 250 foot antenna!)

Operation of the Lunch Box

This transmitter will send the signals over the AM radio band. You use the variable capacitor to adjust what freq. you want to use. Find a good unused freq. down at the lower end of the scale and you're set. Use the 2 meg pot. to adjust gain. Just fuck with it until you get what sounds good. The switch on the 2meg is for turning the Lunch Box on and off. When everything is adjusted, turn on an AM radio adjust it to where you think the signal is. Have [a friend say some shit thru the Box and tune in to it. That's all there is to it. The plans for a simple receiver are shown below:

The Lunch Box receiver

- (1) 9 volt battery with battery clip
- (1) 365 pf variable capacitor
- (1) 51 pf capacitor
- (1) 1N38B diode
- (1) Transistor antenna coil


(1) 2N366 transistor


(1) SPST toggle switch

(1) 1k to 2k magnetic earphone

[Schematic for receiver

=====

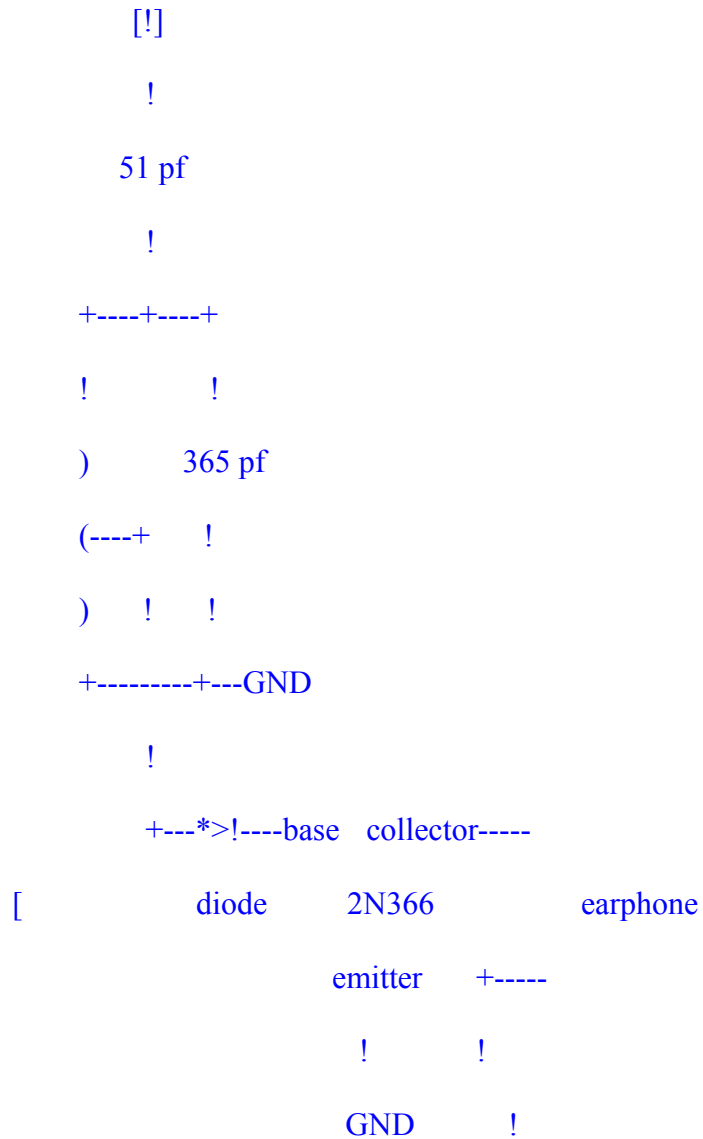

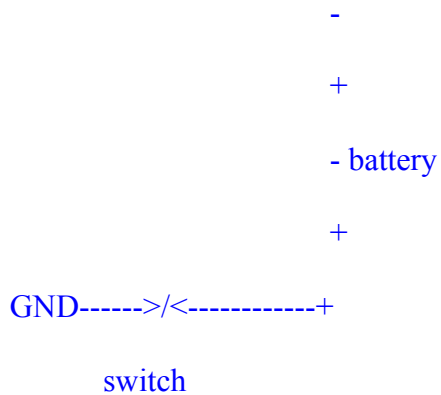

Closeing statement

=====

This two devices can be built for under a total of \$10.00. Not too bad. Using [these devices in illegal ways is your option. If you get caught, I accept NO responsibility for your actions. This can be alot of fun if used correctly.

Hook it up to the red wire (I think) on the fone line and it will send the conversation over the air waves. If you have any problems or are confused, leave me mail on:Hi-Times=702/832/7469 Warez House=702/827/9273