
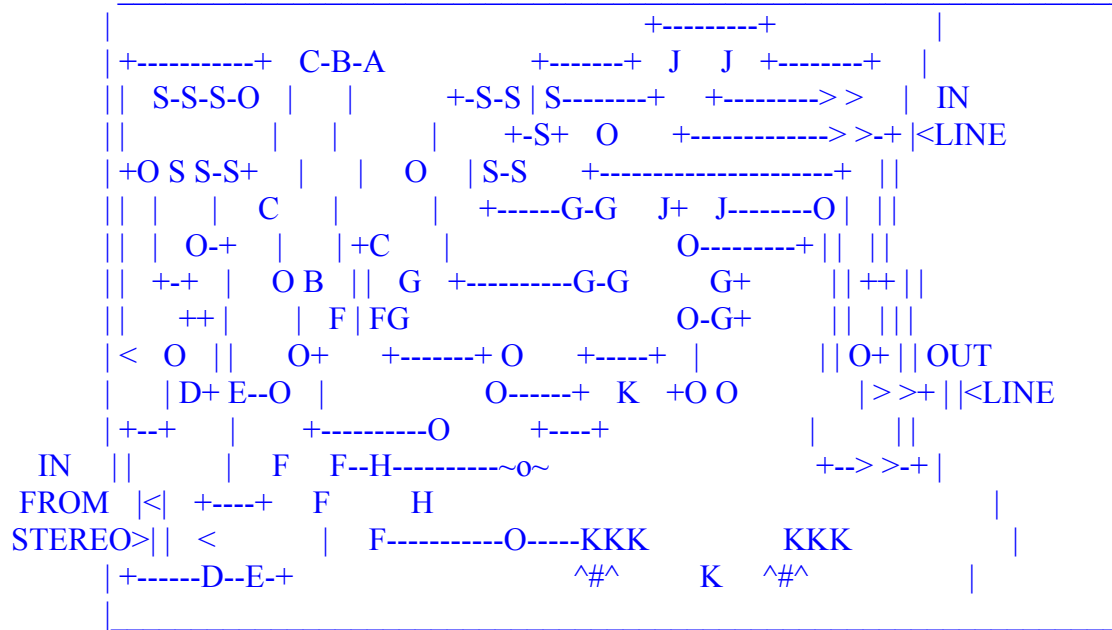


Wiring Diagram -Advanced

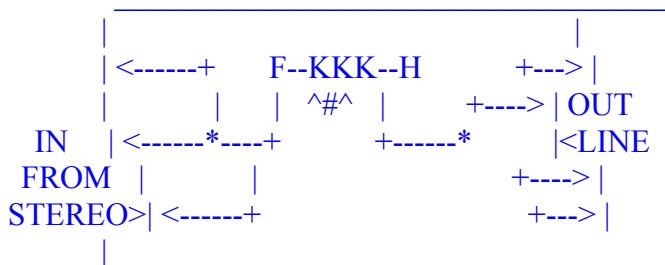Switch for Volume Hi/Lo Switch for Power On/Off



Wiring Diagram -Basic



Now some of the Benefits of this wonderful little device is that you can record conversations, at whatever volume you want, without those bothersome beeps the answering machines make. Or another fun thing is call up a Rodent Bridge and blast this thing with your stereo at full... Wala! The bridge will most likely be clear, even they won't sit through that shit. It is a good idea to hit Radio Shack for a project box and soderless curcuit board, because this can be messy and a project box can easily make you look like a pro. One more use for it is if your computer can generate tones to match a Box of some sort, this makes a GREAT amplifier for it, with almost no loss in

clarity. If you have any problems with a humm or it intercepting radio transmissions, then call up good-old Bell and get a line static clearer dealy and splice that into the box via the outgoing line, which SHOULD clear it up. If that does not seem to help, try putting a 9v battery (you know, the square ones) on the red and green phone lines, because this will make up for the power the box drains from the line. Hope you enjoy the plans and Be watching for more from me! L8r...

The Video Vindicator

Downloaded From P-80 Systems 304-744-2253