
*

*

*

THE HOW TO SERIES

*

*

*

*

PART III

*

*

*

*

TRON BOX

*

*

*

*

BY: CAP'N CRUNCH

*

*

*

*

MONOLITH PRODUCTIONS

*

-----R----F----

I I I

I I I

I-
(C) (C) (C)
I I I

I-
I I I

I

(C)=CAPACITOR

F =FUSE

R =RESISTOR

I,- ARE WIRE

PARTS LIST:

(3) ELECTROLYTIC CAPACITORS RATED AT 50V(LOWEST) .47UF

(1) 20-30OHM 1/2 WATT RESISTOR (1) 120VOLT FUSE (AMP RATING BEST TO USE

AT

LEAST HALF OF TOTAL HOUSE CURRENT OR EVEN LESS IT KEEPS YOU FROM BLOWING YOUR

BREAKER JUST IN CASE...)

(1) POWER CORD (CUT UP AN EXTENSTION CORD. NEED PLUG PART AND WIRE)

(1) ELECTRICALLY INSULATED BOX

REST OF SIF YOUR DONT FILL COMFORTABLE ABOUT ELECTRICITY THEN DONT PLAY WITH

THIS THERE IS VOLTAGE PRESENT THAT WILL ***KILL*** YOU.....

THE THING WORKS WHEN THE LOAD IN YOUR HOUSE IS LOW LIKE AT NIGHT TIME. IT

WILL PUT A REVERSE PHASE SIGNAL ON THE LINE AND CANCEL OUT THE OTHER PHASE AND

PUT A REVERSE PHASE RUNNING EVERY THING IN THE HOUSE. WELL IF YOU HAVE EVER

SWITCHED THE POWER LEADS ON A D.C. (BATTERY POWERED) MOTOR YOU WILL SEE THAT IT

RUNS BACKWARDS WELL YOUR ELECTRIC METER SORT OF WORKS THIS WAY...SO REVERSE

PHASE MAKES THE METER SLOW DOWN AND IF YOUR LUCKY IT WILL GO BACKWARDS. ANYWAY

IT MEANS A CHEAPER ELECTRIC BILL

THE BAY OF PIGS

404-992-4053

10MEG