

CD32

COLLABORATORS

	TITLE : CD32		
ACTION	NAME	DATE	SIGNATURE
WRITTEN BY		August 24, 2024	

REVISION HISTORY

NUMBER	DATE	DESCRIPTION	NAME

Contents

1	CD32	1
1.1	CD32 Connection Hacks	1

Chapter 1

CD32

1.1 CD32 Connection Hacks

CD32 Connection Hacks

Daniel Pfund

April 24, 1995

Abstract

This text file describes:

- o How to connect the CD32 with your Amiga;
- o How to connect the CD32 with an Amiga 2000 style keyboard.

But before you read further, please note that you still do need a CD-ROM to be able to boot the CD32 and communicate with another computer. In my case, I used the Network CD from Almathera.

1 Disclaimer:

I (Daniel Pfund) wrote this file purely to help other people to connect their CD32 with other peripherals. I am glad to help, but I am in no way responsible if you destroy/damage your CD32 while attempting to make these connections. I have tried to keep the information as accurate as possible, but if you find an error, please contact me immediately! "Author" at the end of this file for the addresses where you can reach me).

Also please note that although this is no way a major electronics project, you should at least know how to solder correctly! Don't attempt this if you have never soldered before...

2 Introduction:

As you read in the abstract, this file will describe how to connect several items to your CD32. I wanted to list here some other references you might find useful (that's where I got the information from).

1. The CD32FAQ. You can get it by FTP at: "ftp.demon.co.uk:/pub/amiga/
-

info/cd32-faq.txt". This is really the main reference and you will find a huge amount of information here. The only problem being that it is very difficult to access the FTP site, even at non prime time hours.

2. Article posted by Anders Stenkvis (ask_me@elixir.e.kth.se) called "CD32 expansion port info". It has all the pinouts you need, but contains at least one error (the one I've found!), so I don't know if the rest is correct. . .

3 Parts needed

The following parts are needed:

- o 1 MAX 232
- o 1 16 pin IC socket (optional)
- o 4 1 microF electrolytic capacities (or 10 microF goes also) rated 16V
- o 1 mini DIN 6 poles male
- o 1 DIN 5 poles female
- o 1 DB-25 female
- o 2 m (more or less) of 2 conductors (+shield) wire
- o 20 cm (more or less) of 5 conductors (+shield) wire
- o 1 led (optional, see section 4)
- o 1 330 ohms (or 470) resistor (optional)
- o 1 box to put the whole thing into (optional. . .)

All the parts should be available at your local electronics store and the only costly part is the MAX 232 (~ 6\$), and all the parts would cost you about 12\$.

4 The cable:

Once you have got all the parts you need, you can start putting them together following the accompanying schematic in the IFF file. The way you do this is entirely up to you. All you have to do is connect together the pins with the same name. You can do it very easily on a piece of veroboard or completely professionally on a circuit. I've not provided the PCB plan, but it is not very difficult to invent one.

As you can see, you can add a led to check if the CD32 is on and everything is working fine. This is absolutely not mandatory. You will just need an extra led and a resistor to limit the current going through it.

5 Author:

You can contact me via snail mail at:

Daniel Pfund

19, ch. de Tirelonge
CH-1213 Onex
Switzerland

You can also reach me via E-Mail (preferred !): "Pfund@uni2a.unige.ch"
or if this address doesn't work any more (in a couple of years) you can
still write to me at: "hb9vbc@pccr01.cern.ch". (Note the zero, not an o !)

History:

v 1.1 (25.04.95)

- o Corrected an error in the pinouts of the IFF picture. Thanks to Paul Day (pday@gate.net) for the error report;
- o Changed the IFF file to 2 bit planes (B&W) only.

v 1.0 (10.04.95)

- o Initial release to Aminet in "hard/hack" directory.

[Back To Main Menu](#)

[Back To Projects Menu](#)
