

Technote Number 1138

High-Speed SDRAM Design Considerations

CONTENTS

[Defining the Problem](#)

[Problem Areas](#)

[Why This Hasn't Been As Much a Problem In the Past](#)

[Design Considerations for Modern RAM Modules](#)

[Additional Notes & Comments](#)

[Summary](#)

This Technote describes some of the design issues that should be considered by developers of high-speed SDRAM DIMM modules for Macintosh computers.

With ever-increasing computer speeds, it is more difficult than ever to design reliable memories that remain stable over time & temperature variations. However, following a few high-speed design guidelines and techniques can save time and valuable resources, as well as produce a more stable and reliable product.

This note is directed at memory developers who are involved in the design and manufacture of high-speed RAM memory modules for Macintosh computers.

Defining the Problem

RAM module design is becoming ever more critical. Modules that previously worked in some older, slower Macintosh computers may experience intermittent problems--or may not work at all--in newer, faster machines. Trace lengths, noise, timing, and bus loading have all become critical concerns in today's high-speed systems.

Problem Areas

The following lists some potential problem areas for RAM module designers:

- A. Routing of signal lines;
- B. Partial stuffing options;
- C. Signal line lengths;
- D. Bypass capacitor distribution; and
- E. Clock timing.

Why This Hasn't Been As Much a Problem In the Past

Designing stable RAM memories has always been difficult, but the relatively slow speed buses of the past have allowed considerable margins in the designs. Pushing systems faster has generally resulted in pushing CPU speeds to new levels, and this will surely continue as the technology moves forward. However, this is becoming increasingly difficult to accomplish. In order to squeeze more performance out of today's systems, memory and I/O speeds are being boosted, which also necessitates keeping the entire system in balance. As a result, we are increasing memory bus speeds in order to improve overall system performance as much as possible. These new higher bus speeds are exposing many limitations in traditional RAM module design.

Design Considerations for Modern RAM Modules


There are many techniques that may be applied to RAM memory designs that will help improve their stability. First, plan your design topology with care. Look carefully at signal line lengths and try to match them as closely as possible. Pay particular attention to the address bus, since this is usually the most heavily loaded. Furthermore, try to plan the simplest routing of each byte of the data bus. Give some thought to the placement of the RAMs and clock chips to accomplish these goals.

If you plan on having stuffing options in your product (i.e., partially stuffed versions), be sure to place the stuffed RAMs at the end of the signal lines to avoid unterminated stubs. Moreover, make sure the loading of clocks is balanced in all possible stuffing options.

Design your product for 100Mhz operation. Also, hand-route your critical signal paths, if possible. Many autorouters are not capable of doing a very good job with highly constrained signals. Even the autorouters that are capable might not be very efficient because of all the design constraints involved. Often these critical signals are better being hand-routed anyway, in order to accomplish the job in a reasonable amount of time. Keep in mind that if this is a new design threshold, it may take a couple of iterations of hand routing to get a feel for the actual design constraints.

Plan for dedicated power and ground planes with bypass caps placed as closely to the RAMs as possible. Ensure an adequate number of vias from the connector pads to power and ground, and to the devices. One via for each power and ground pin per device is recommended. Twenty-five mil (.025) traces for power and ground pins is highly recommended, but under no circumstances should less than ten mil (.010) be used.


Finally, use zero-delay buffers for the clocks. The Cypress CY2305 is a good example, and serves as an excellent solution for both memory and PCI clocking. This device will always attempt to adjust its CLKOUT signal for zero skew compared to the REF input. Because of this property, there are several design methods that can be used for the device:

 

Reference 1

Cypress CY2305 Clock Buffer Adjustable Delay Configuration

In Reference 1, the CLK1..4 outputs can be advanced or delayed by adjusting the C_{load} on the CLKOUT signal. The more load applied to CLKOUT, the more advanced the CLK1..4 signals become relative to REF. By contrast, the less load applied to CLKOUT, the more delayed the CLK1..4 signals become relative to REF. This means that, within reason, the clocks may be adjusted to compensate for the actual loads being presented by the driven devices (in this case, the RAMs). The ratio of loading to advance/delay timing is roughly 50 ps/pf (see Cypress specification for exact numbers). Note, it is important to load all CLK1..4 outputs evenly in order to minimize clock skew between individual outputs themselves.

 

Reference 2

Cypress CY2305 Clock Buffer Automatic Delay Configuration

If there is no specific delay or advance required on the clocks relative to the REF, the Reference 2 design may be employed. In this case, CLKOUT is directly used as one of the driving clock signals. Since the device will zero skew the REF to CLKOUT signals, then all of the remaining CLK2..4 signals will also stay in phase with the REF signal regardless of the actual loading involved (again, all loads are assumed equal).

Lastly, in order to increase memory density, some manufacturers are paralleling memories together. This technique is known as "stacking" or composite memories. Some designs exist that utilize a version of the stacking technology in which the individual RAM devices are soldered together on the substrate. This is simply a modern version of the composite memory products of several years ago in which multiple SIMM or DIMM modules were plugged into a single combiner substrate, which was then plugged into the host. Other techniques employ internal RAM device designs in which multiple die are actually wired in parallel inside the chip packaging. In both cases, bus loading and timing become critical due to the parallel bus nature of the architecture. At the time of this writing, Apple does not endorse either of these

techniques, or any other technology based on device-stacking.

Additional Notes & Comments

The following are some important items that you may need to consider when working through the problem:

- Match the number of devices the clocks are driving;
- Ensure clocks are also balanced in partially stuffed products;
- Examine signal lengths from CAD/CAM output, both absolute and relative;
- Hand route critical signals where possible (or at least analyze autorouted signals); and
- Do not rely on stacked devices in your product designs.

Summary

As systems get faster, good stable RAM memory designs are becoming increasingly difficult to accomplish. However, products can be designed that behave well, provided enough care and thought is put into their design beforehand.

Further References

- [Low Cost 3.3V Zero Delay Buffer for PC and SDRAM, Cypress Semiconductor Corporation](#)
- [JESD 21 C Configurations for Solid State Memories](#)
- [Intel PC Memory Specifications](#)
- [Technote 1055: SIMMs to DIMMs: Making Sense Out of Memory Expansion for the Power Macintosh](#)
- [Technote HW33: Composite SIMMs Not Supported](#)

Downloadables



[Acrobat version of this Note \(K\).](#)

To contact us, please use the [Contact Us](#) page.
Updated: 31-August-98

[Technotes](#)
[Previous Technote](#) | [Next Technote](#)
[Contents](#)