
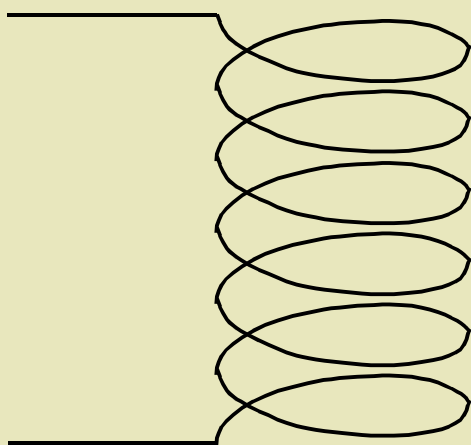


# The Design of a Relay Computer


*Harry Porter, Ph.D.*  
Portland State University

April 24, 2006

 






## Double Throw Relay

 


## Double Throw Relay

 


# Four Pole, Double Throw Relay

  




# Four Pole, Double Throw Relay

 



 




# Schematic Diagrams

 
 
 


# Schematic Diagrams

   


*Assume other terminal  
is connected to ground*

# Schematic Diagrams

   


*Assume other terminal  
is connected to ground*


# The “NOT” Circuit

 


<u>in</u>	<u>out</u>
0	1
1	0

 

# The “NOT” Circuit

 


<u>in</u>	<u>out</u>
0	1
1	0

 


Convention:  
“1” = +12V  
“0” = not connected

# The “NOT” Circuit

 


<u>in</u>	<u>out</u>
0	1
1	0

 


Convention:  
“1” = +12V  
“0” = not connected



# The "OR" Circuit

 

<b>b</b>	<b>c</b>	<b>OUT</b>
0	0	0
0	1	1
1	0	1
1	1	1


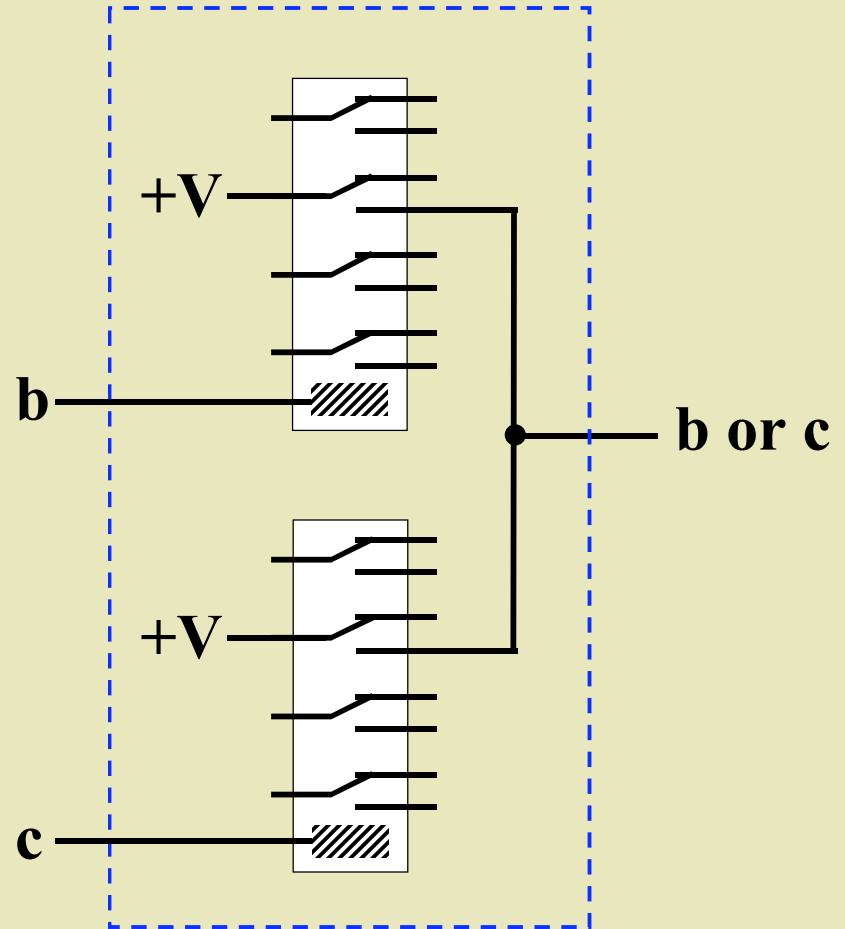


# An Optimization?

 
 




# An Optimization?

 
 


# An Optimization?

  



**Whoops!**

# An Optimization?

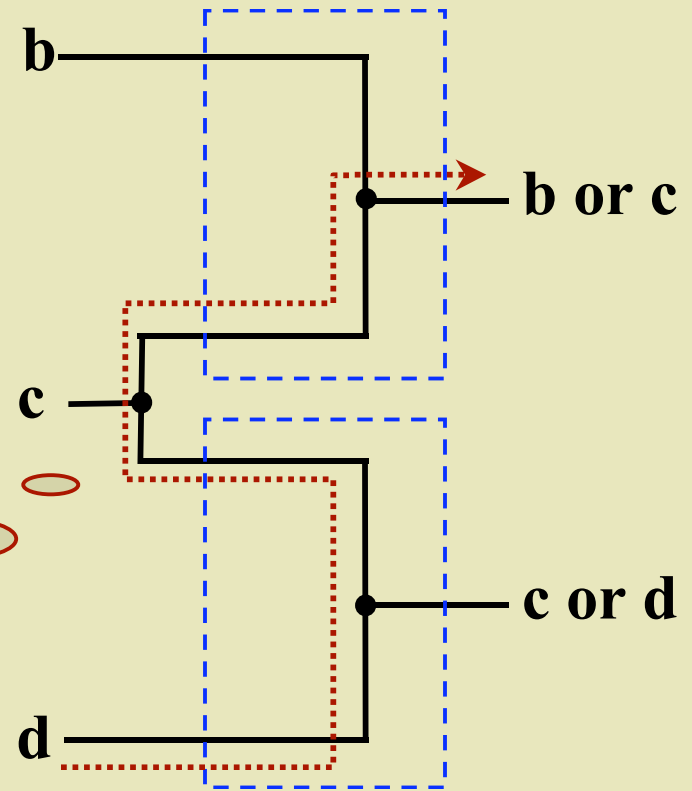 


**Whoops!**

# An Optimization?

  


# 1-Bit Logic Circuit

b	c	NOT	AND	OR	XOR
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

 


# 1-Bit Logic Circuit

b	c	NOT	AND	OR	XOR
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

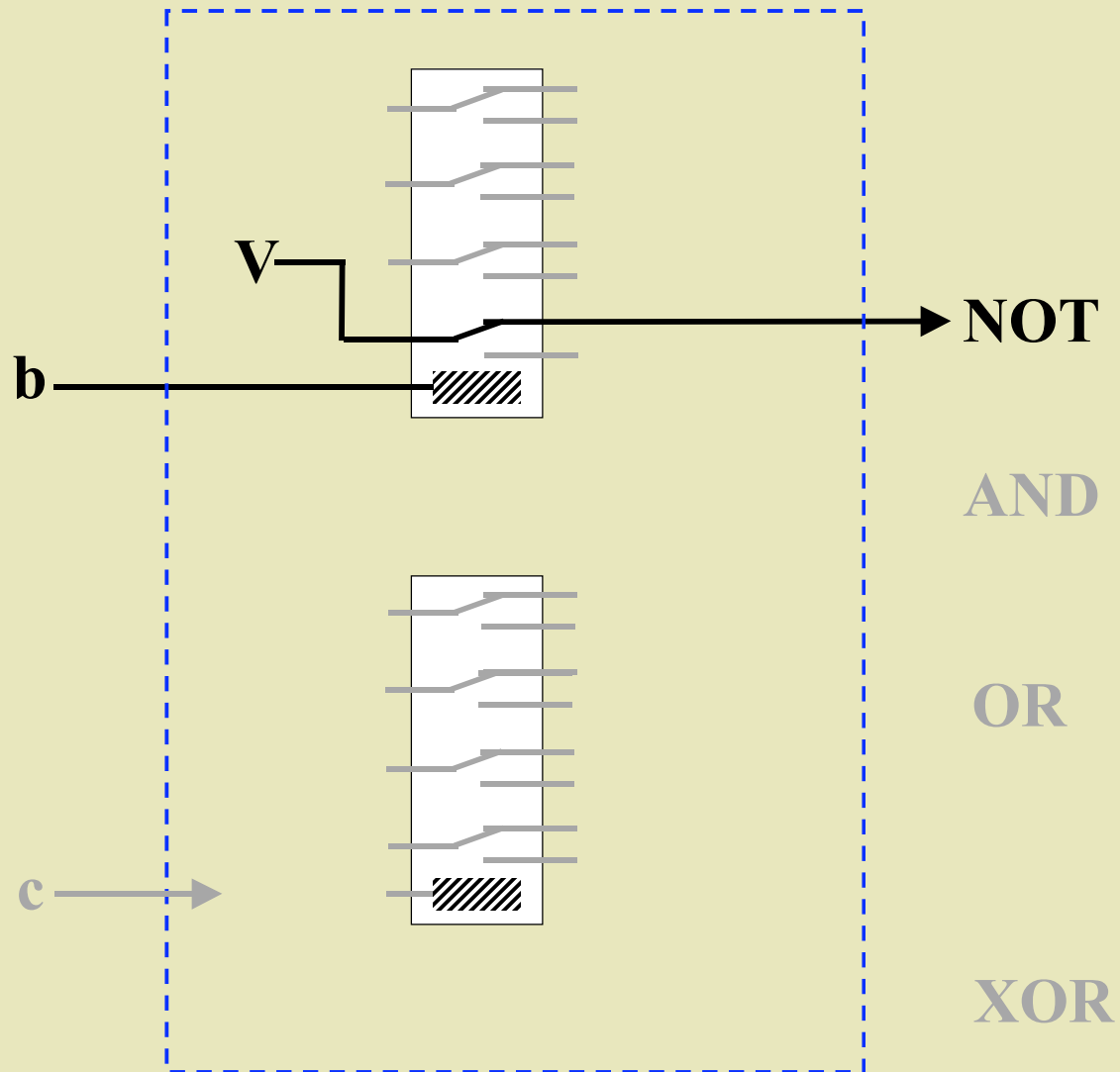


# 1-Bit Logic Circuit

<b>b</b>	<b>c</b>	<b>NOT</b>	<b>AND</b>	<b>OR</b>	<b>XOR</b>
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

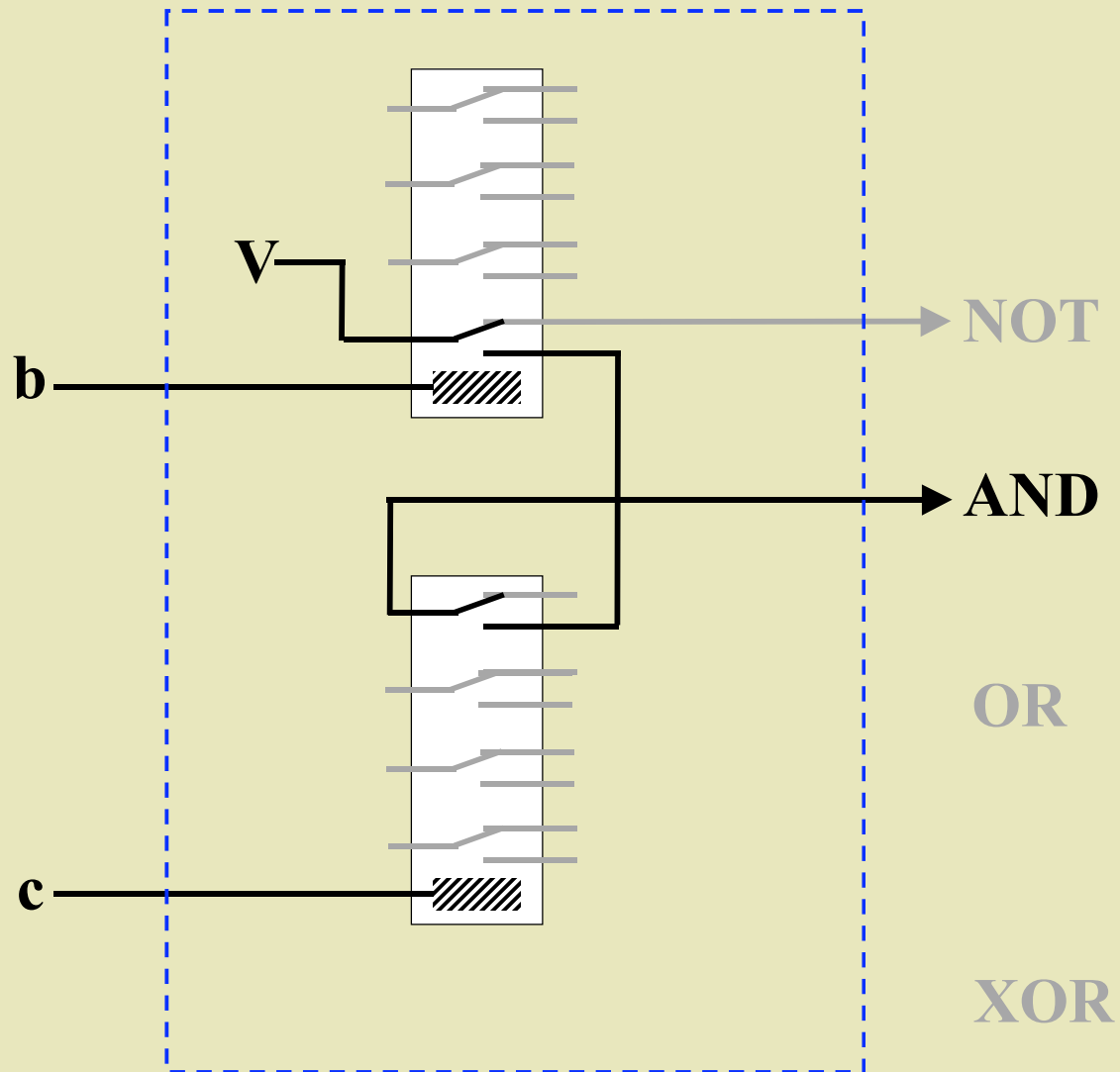

# 1-Bit Logic Circuit


<b>b</b>	<b>c</b>	<b>NOT</b>	<b>AND</b>	<b>OR</b>	<b>XOR</b>
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

 




# 1-Bit Logic Circuit

<b>b</b>	<b>c</b>	<b>NOT</b>	<b>AND</b>	<b>OR</b>	<b>XOR</b>
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

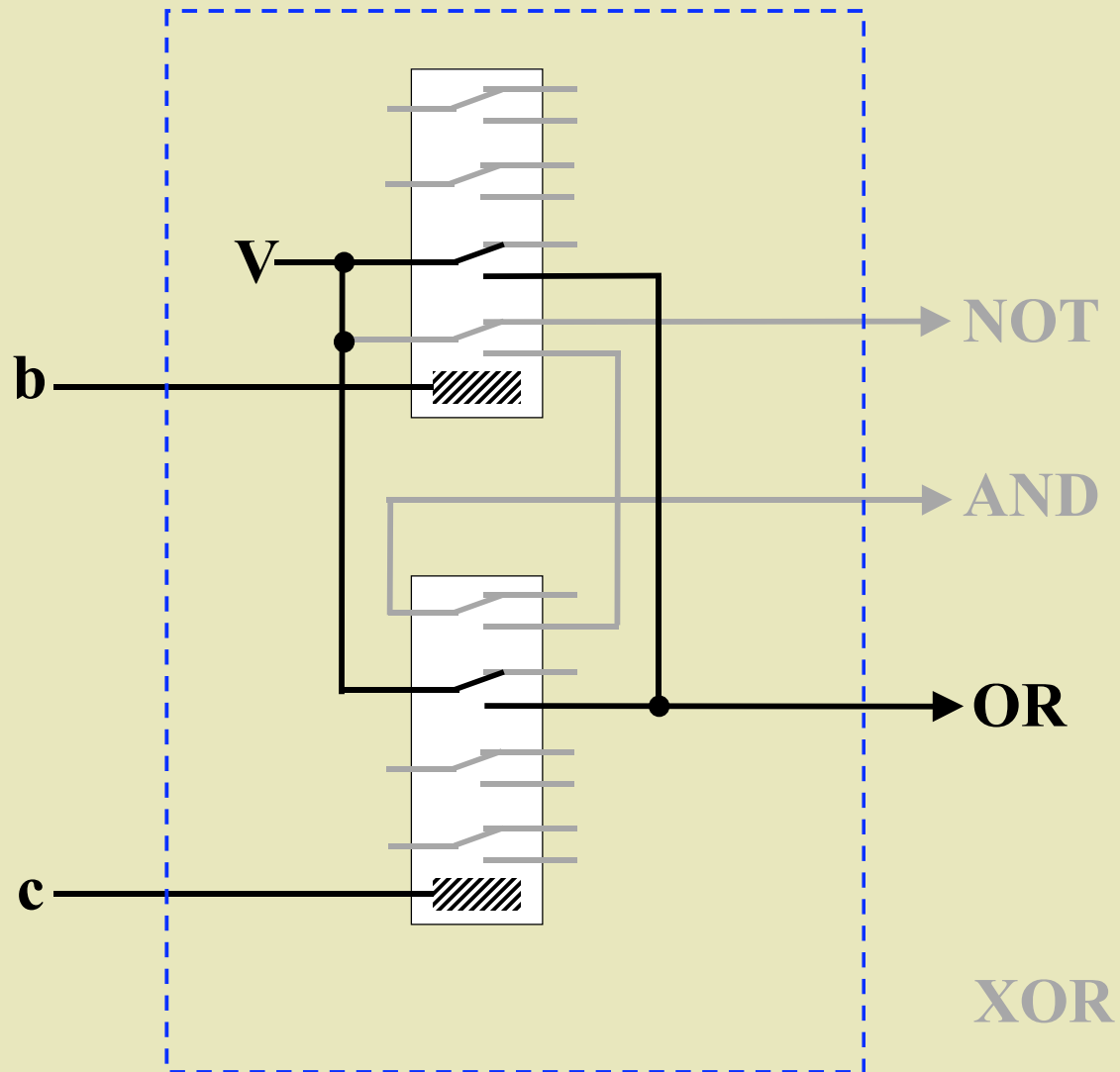

# 1-Bit Logic Circuit


<b>b</b>	<b>c</b>	<b>NOT</b>	<b>AND</b>	<b>OR</b>	<b>XOR</b>
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

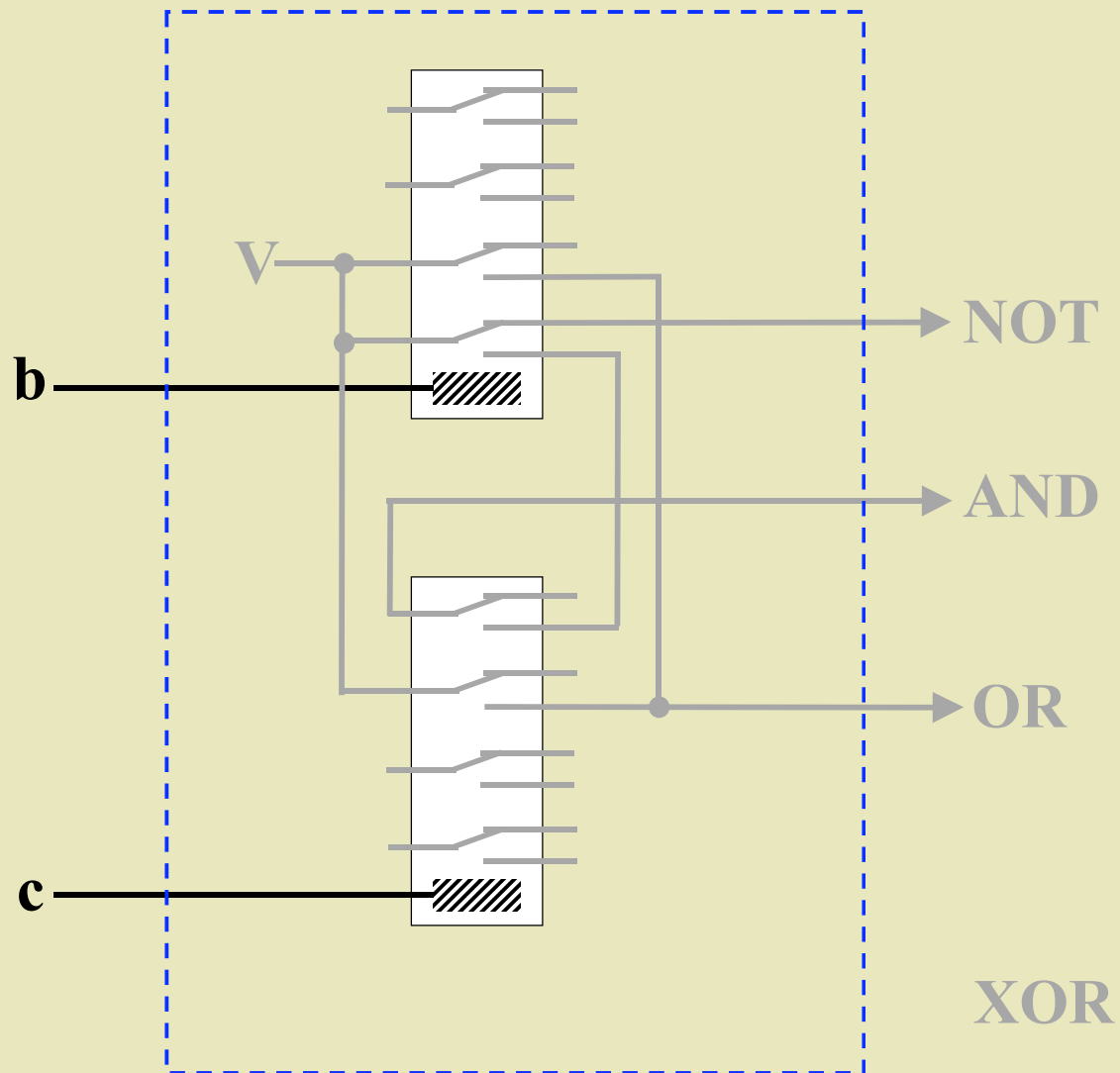

XOR


# 1-Bit Logic Circuit

<b>b</b>	<b>c</b>	<b>NOT</b>	<b>AND</b>	<b>OR</b>	<b>XOR</b>
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

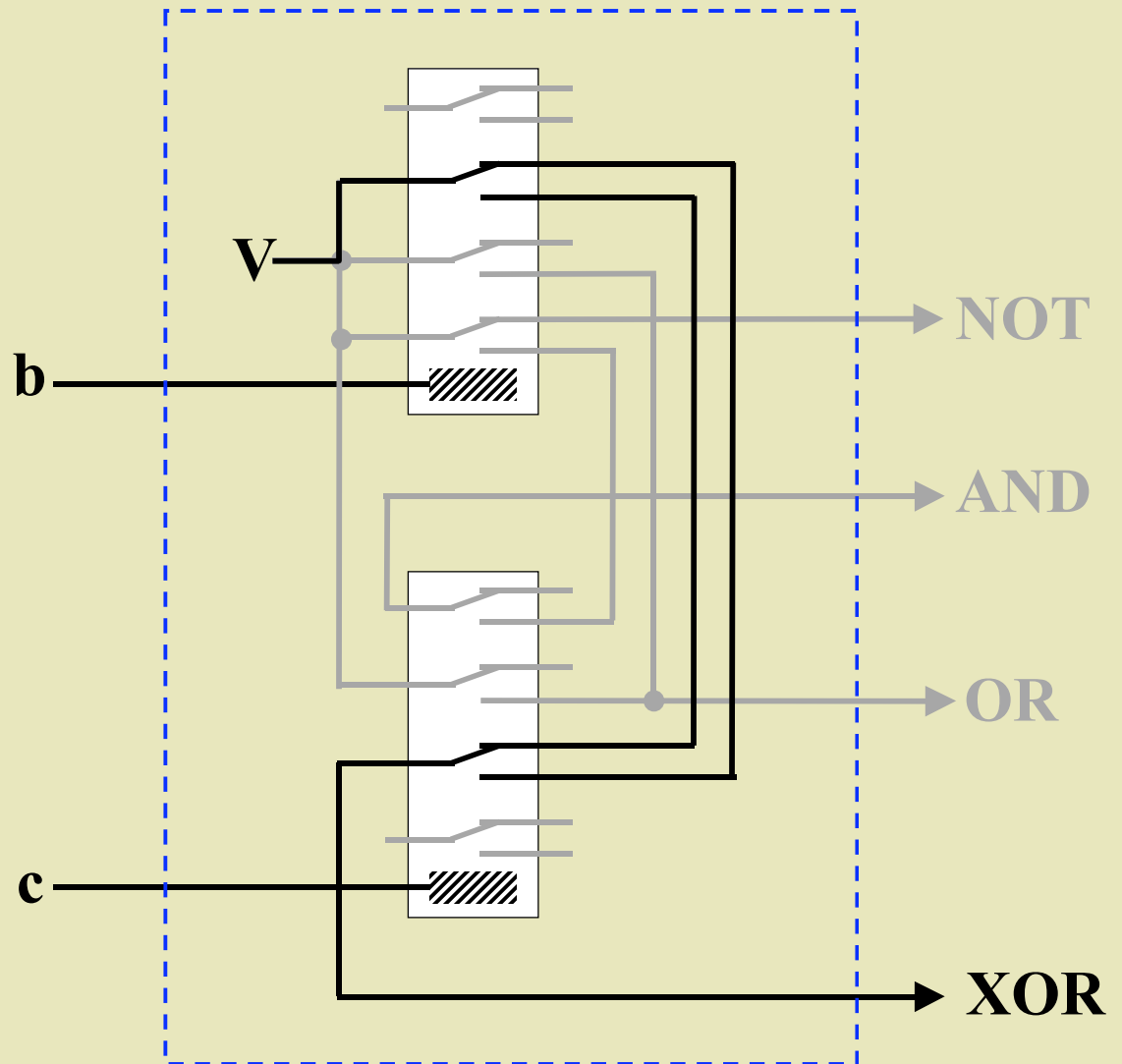


# 1-Bit Logic Circuit

<b>b</b>	<b>c</b>	<b>NOT</b>	<b>AND</b>	<b>OR</b>	<b>XOR</b>
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

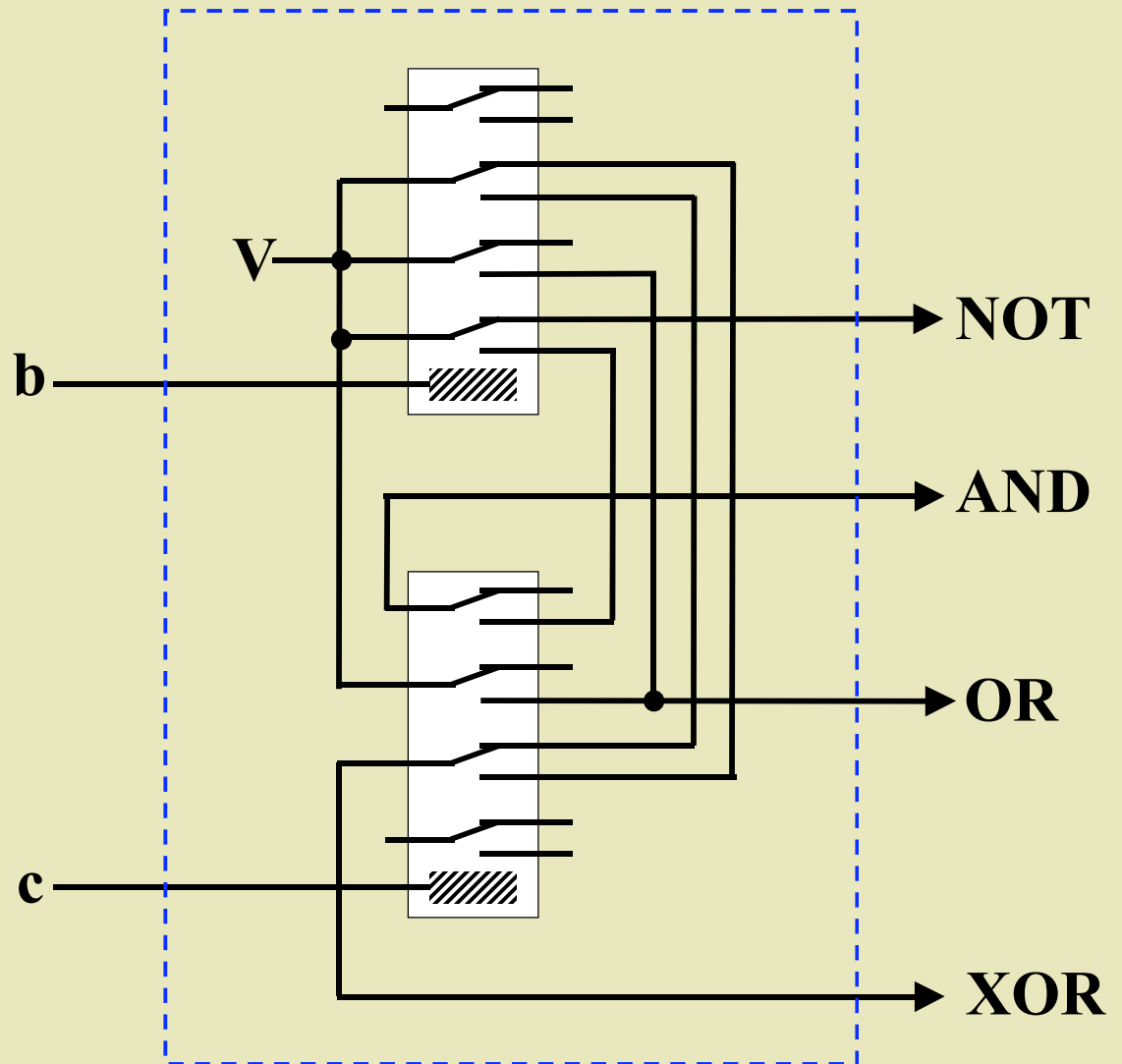


*Eight 1-bit circuits can be combined  
to build an...*

## 8-Bit Logic Circuit

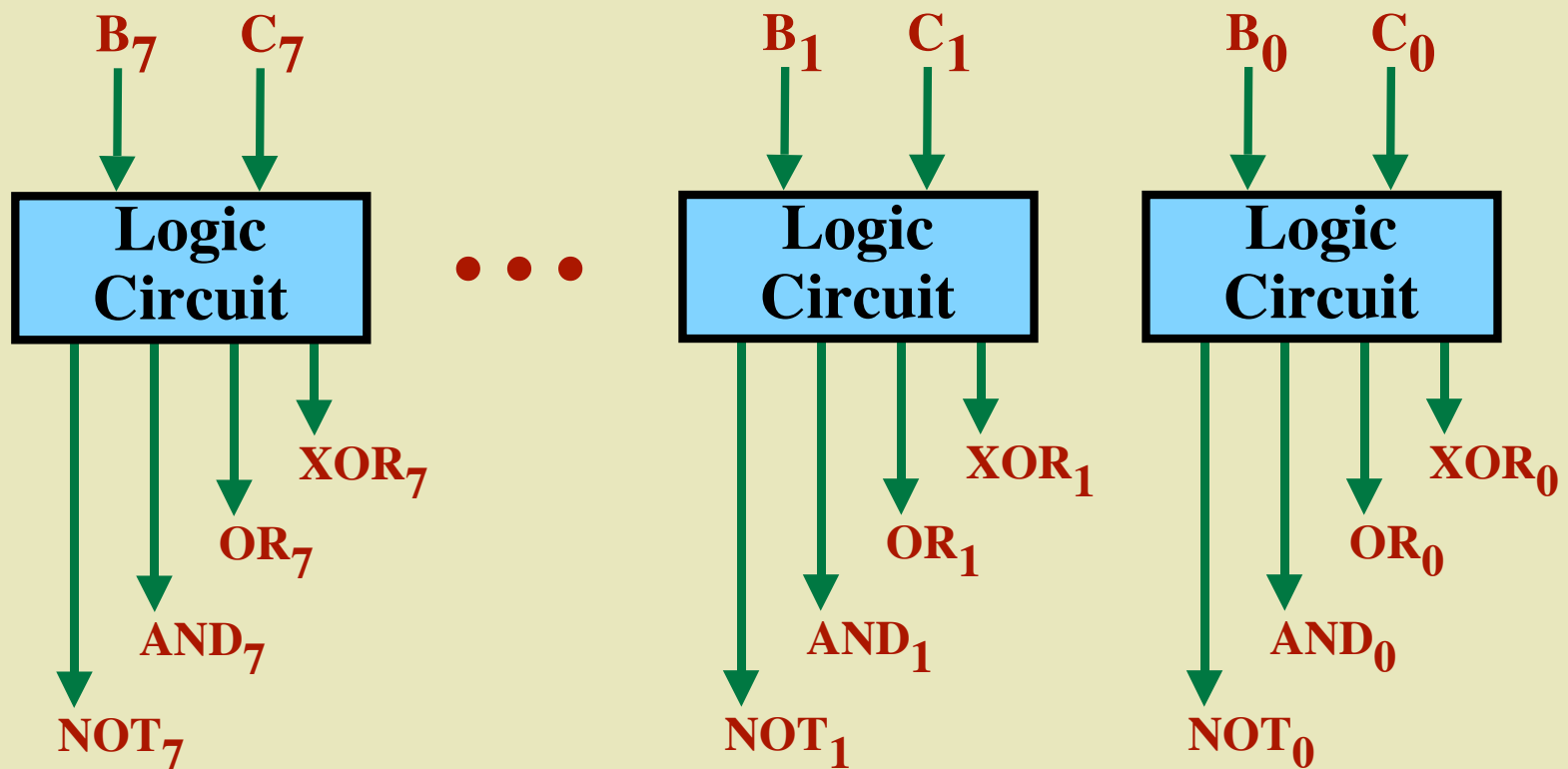


# The “Full Adder” Circuit

$Cy_{in}$	B	C	$Cy_{out}$	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

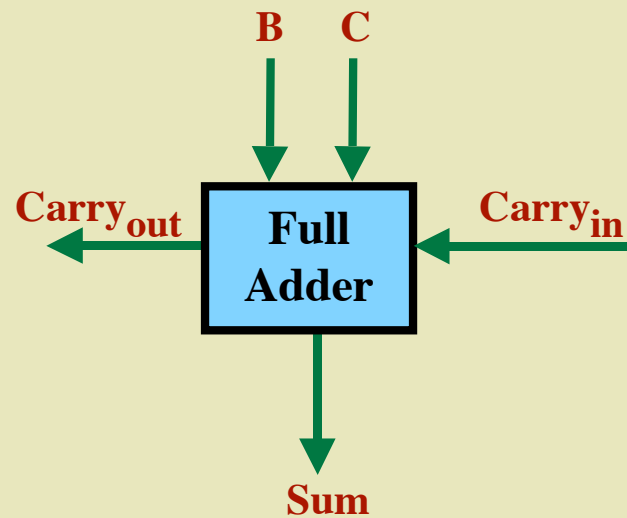


*8 full-adders can be combined to build an...*

## 8-Bit Adder

 

*8 full-adders can be combined to build an...*



## 8-Bit Adder

 




*8 full-adders can be combined to build an...*


## 8-Bit Adder

  


# The Zero-Detect Circuit

 


# The Zero-Detect Circuit

 


# Enable Circuit

 


# Enable Circuit

 

# Enable Circuit

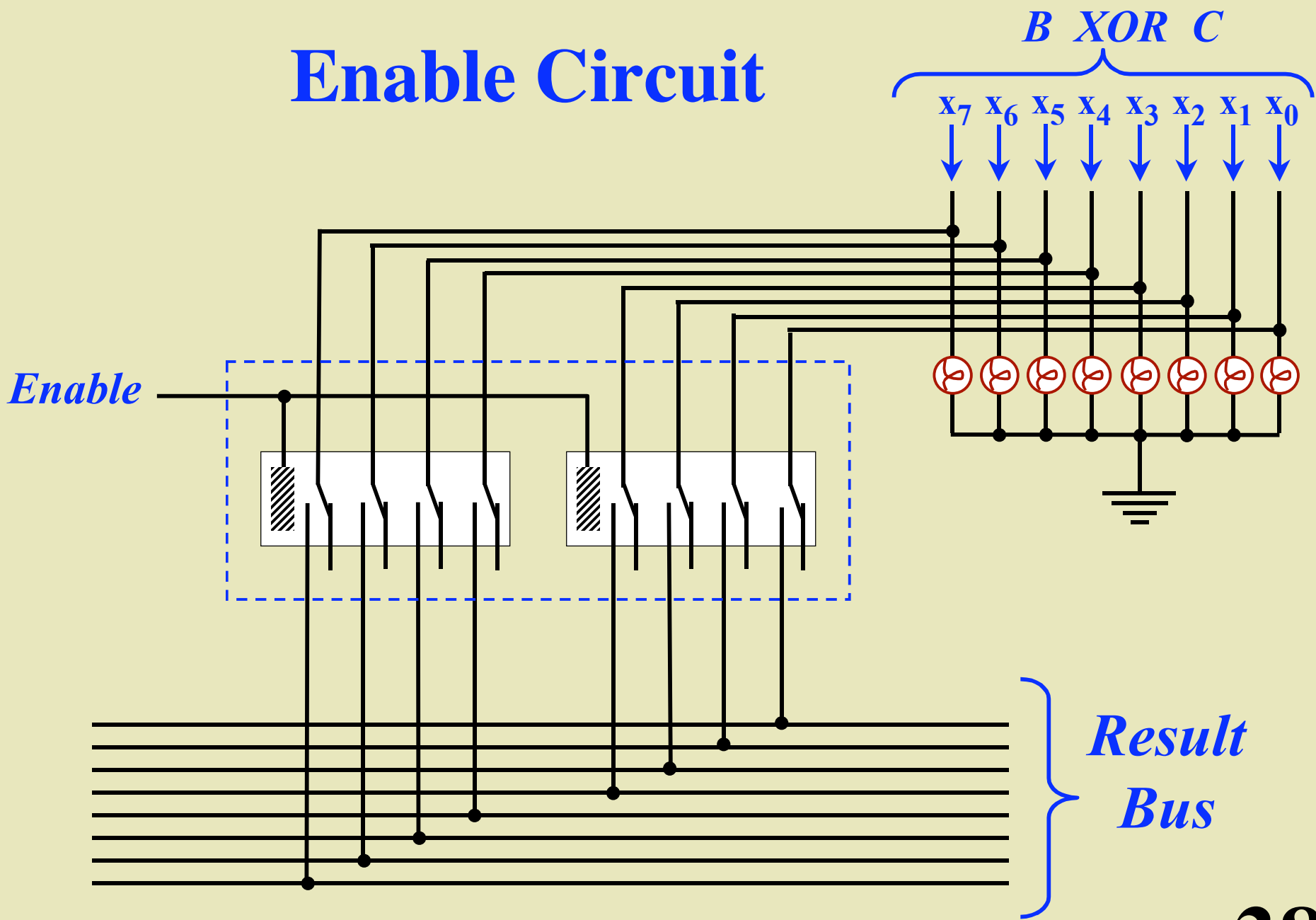

# Shift Left Circular (SHL)

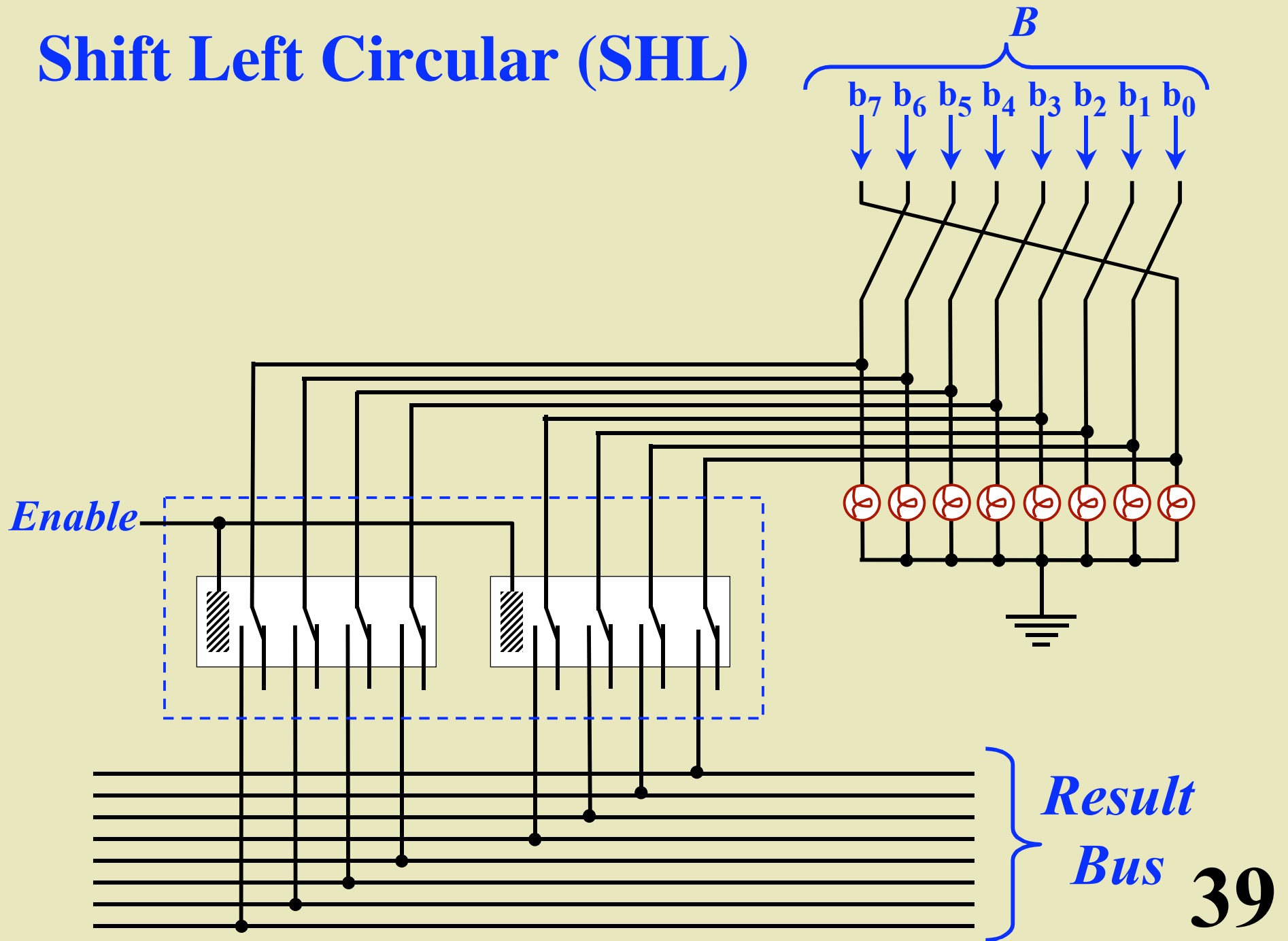


# 3-to-8 Decoder

$f_0$	$f_1$	$f_2$	OUTPUT							
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1




# 3-to-8 Decoder

$f_0$	$f_1$	$f_2$	OUTPUT							
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 

# 3-to-8 Decoder


$f_0$	$f_1$	$f_2$	OUTPUT								
0	0	0	1	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	0	1

 


21:46




# Arithmetic Logic Unit (ALU)

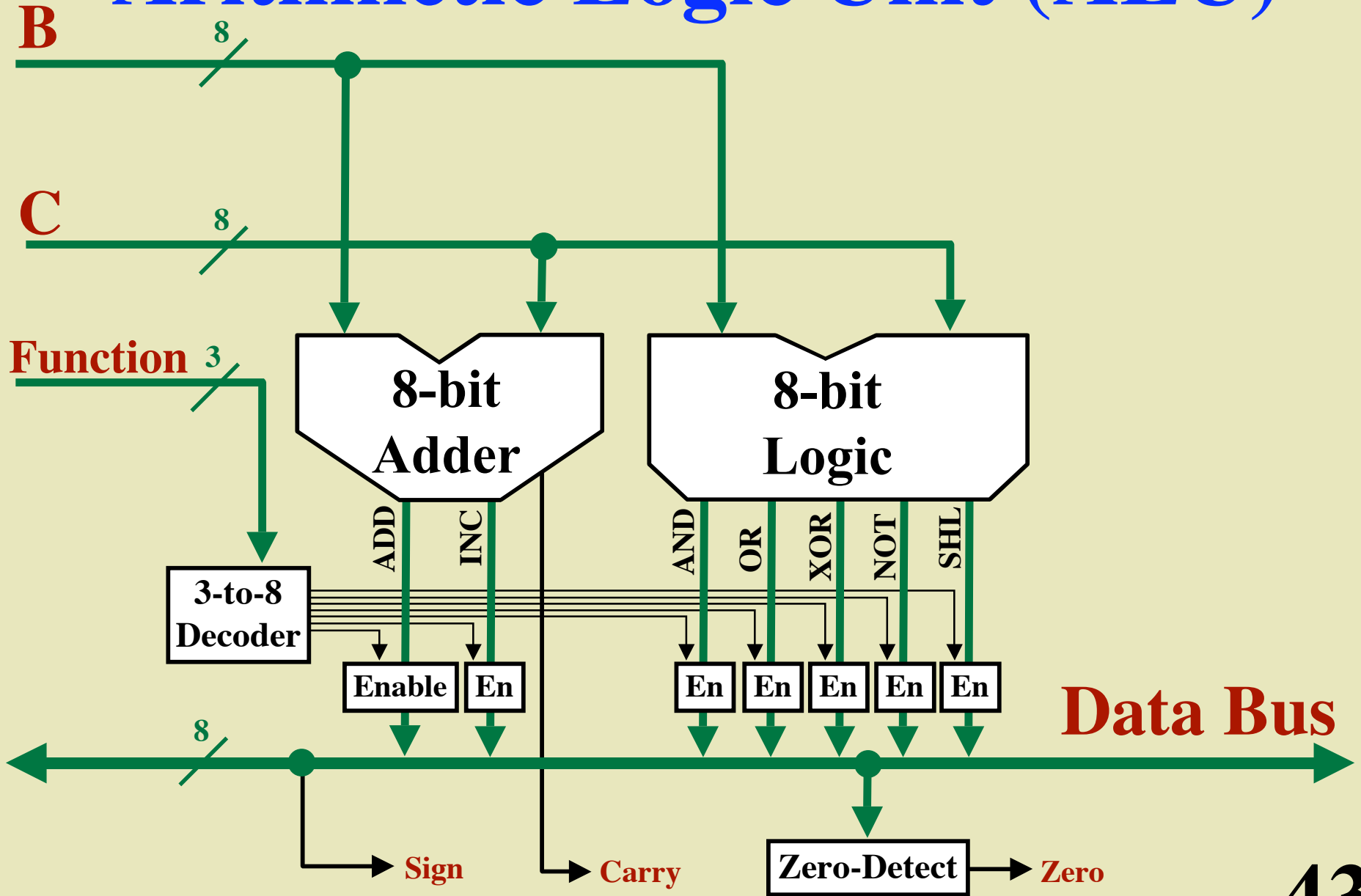


# An 8-Bit ALU

 


# Register Storage

 


# Register Storage

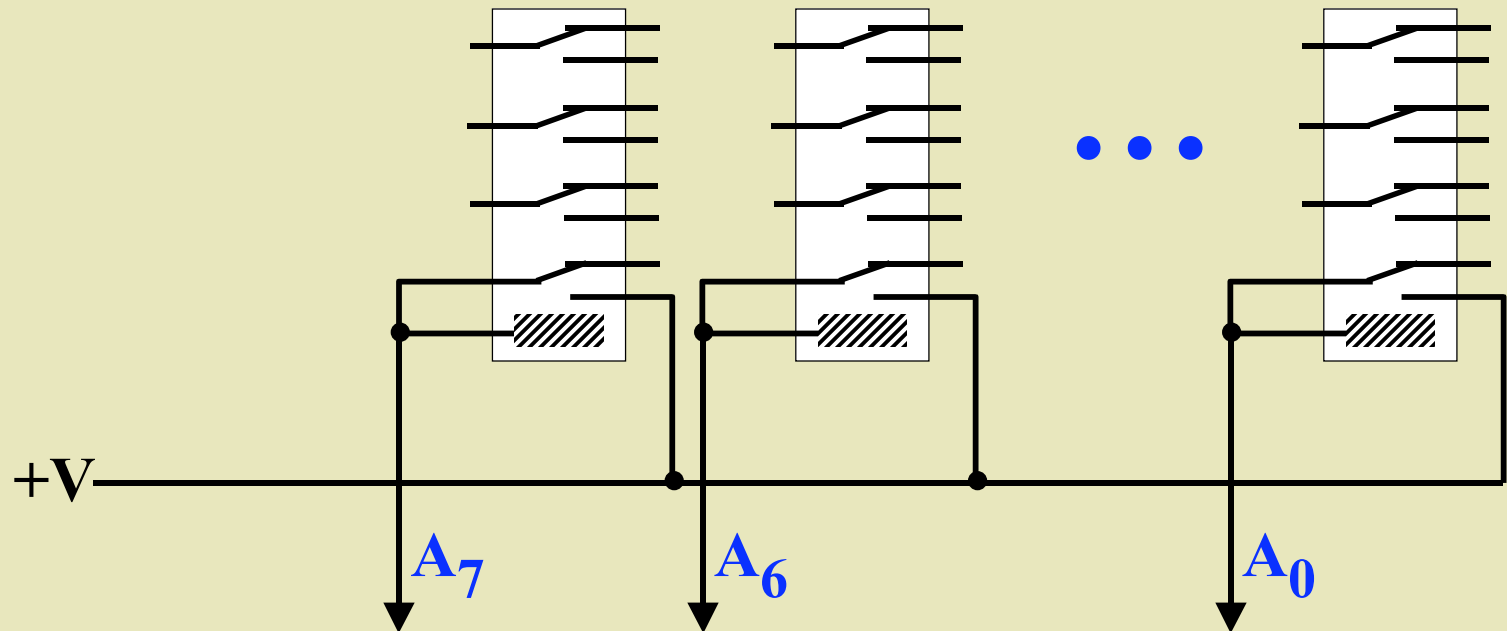

# Register Storage

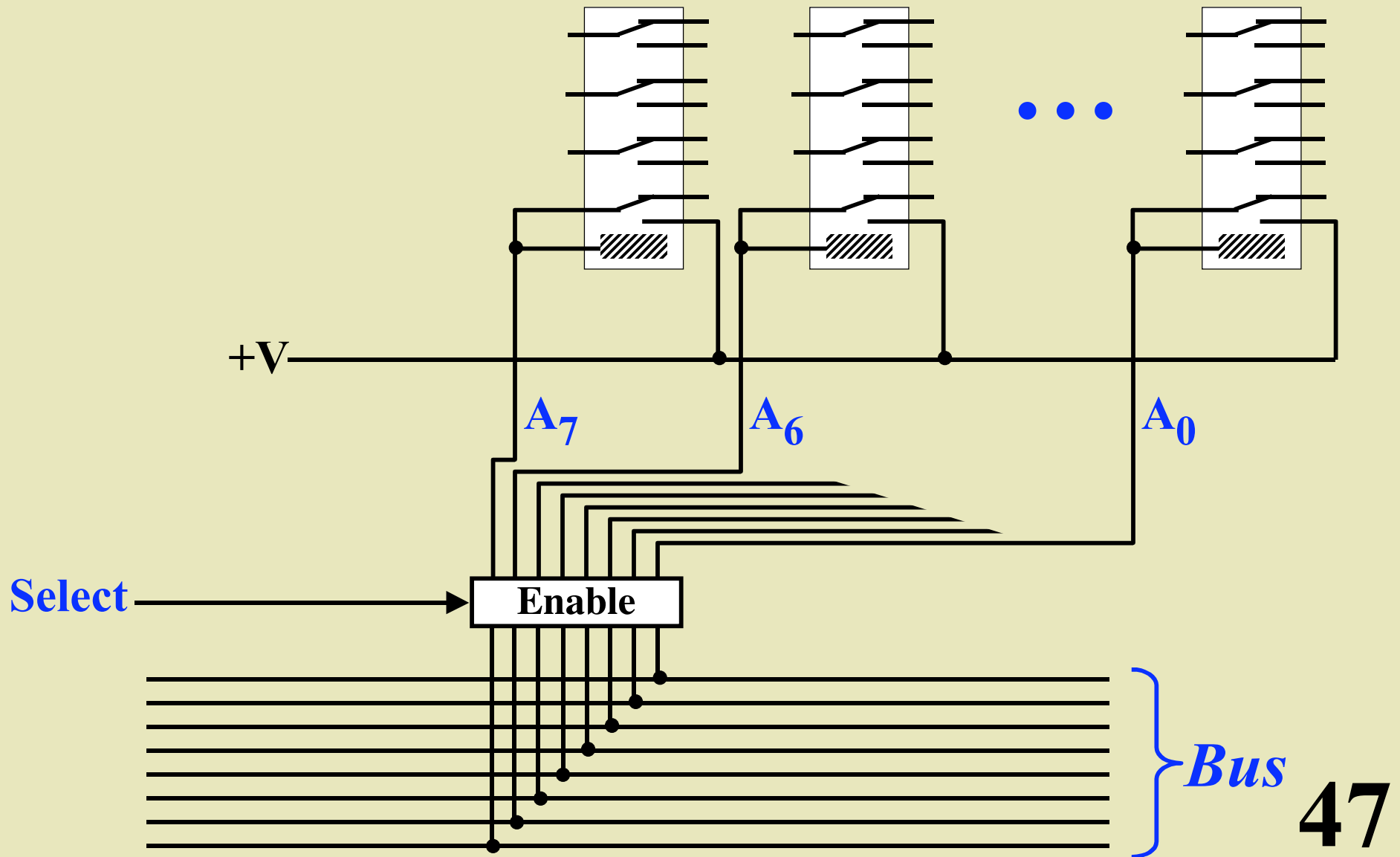


# Register Storage

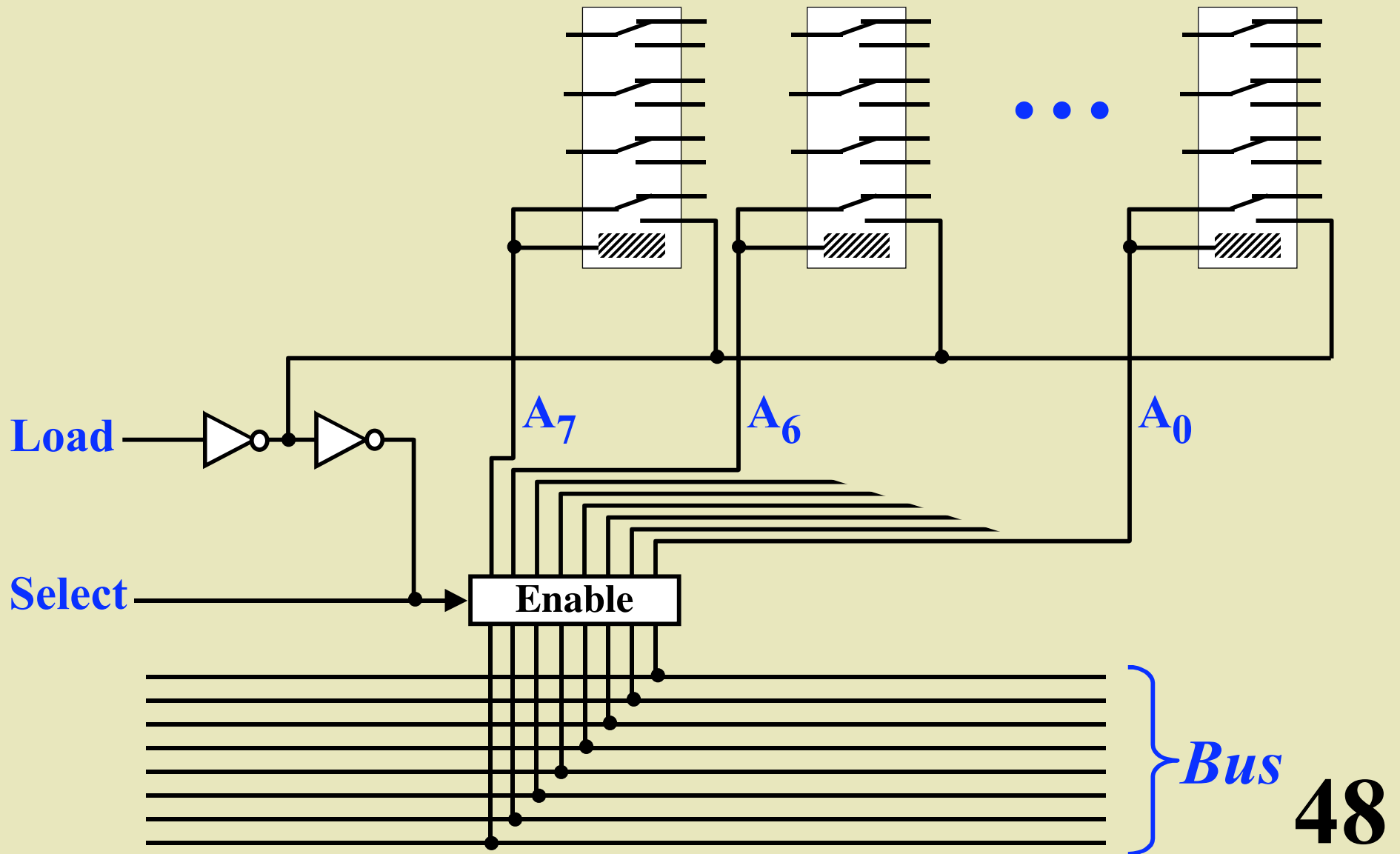






# 8-Bit Registers

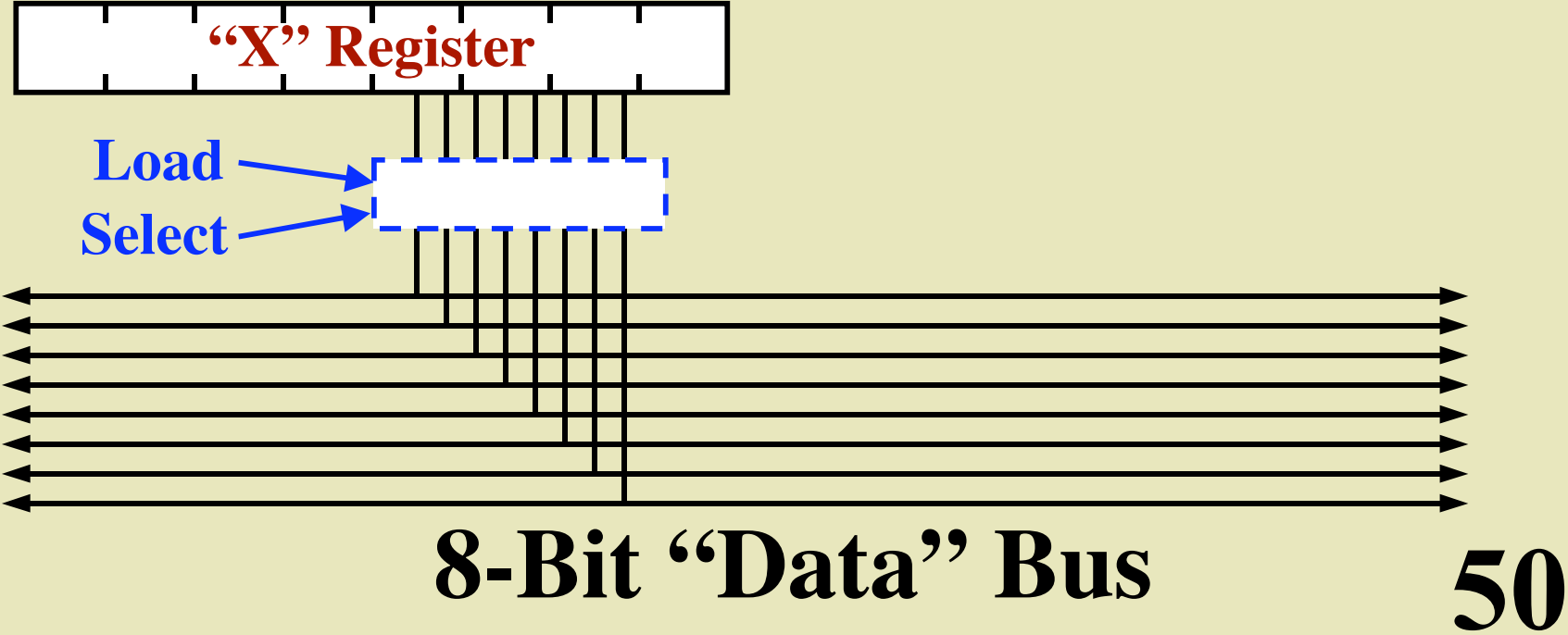


# 8-Bit Registers

 


8-Bit "Data" Bus

# 16-Bit "Address" Bus

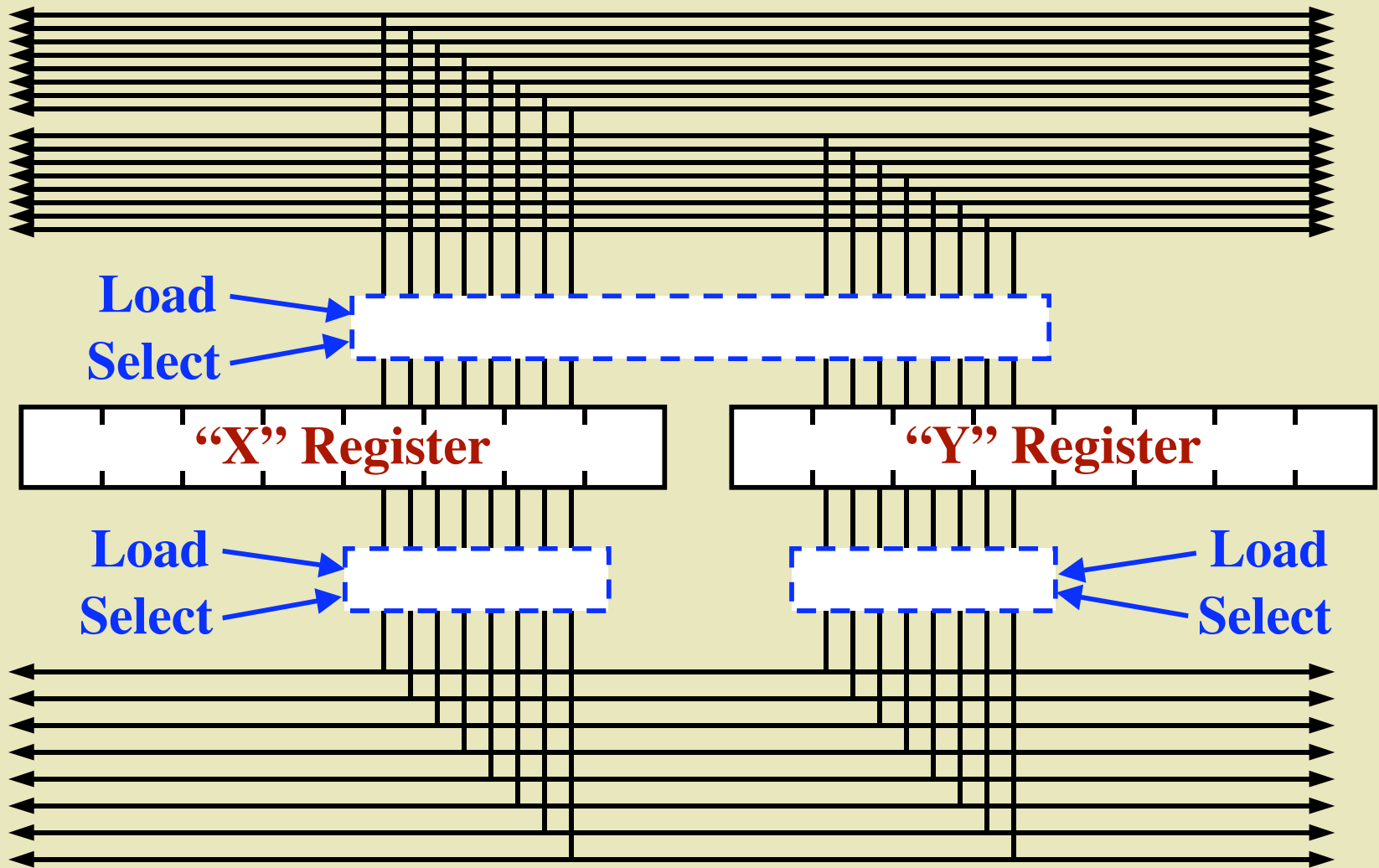


8-Bit "Data" Bus


8-bit Data Bus

 


# System Architecture

8-bit Data Bus

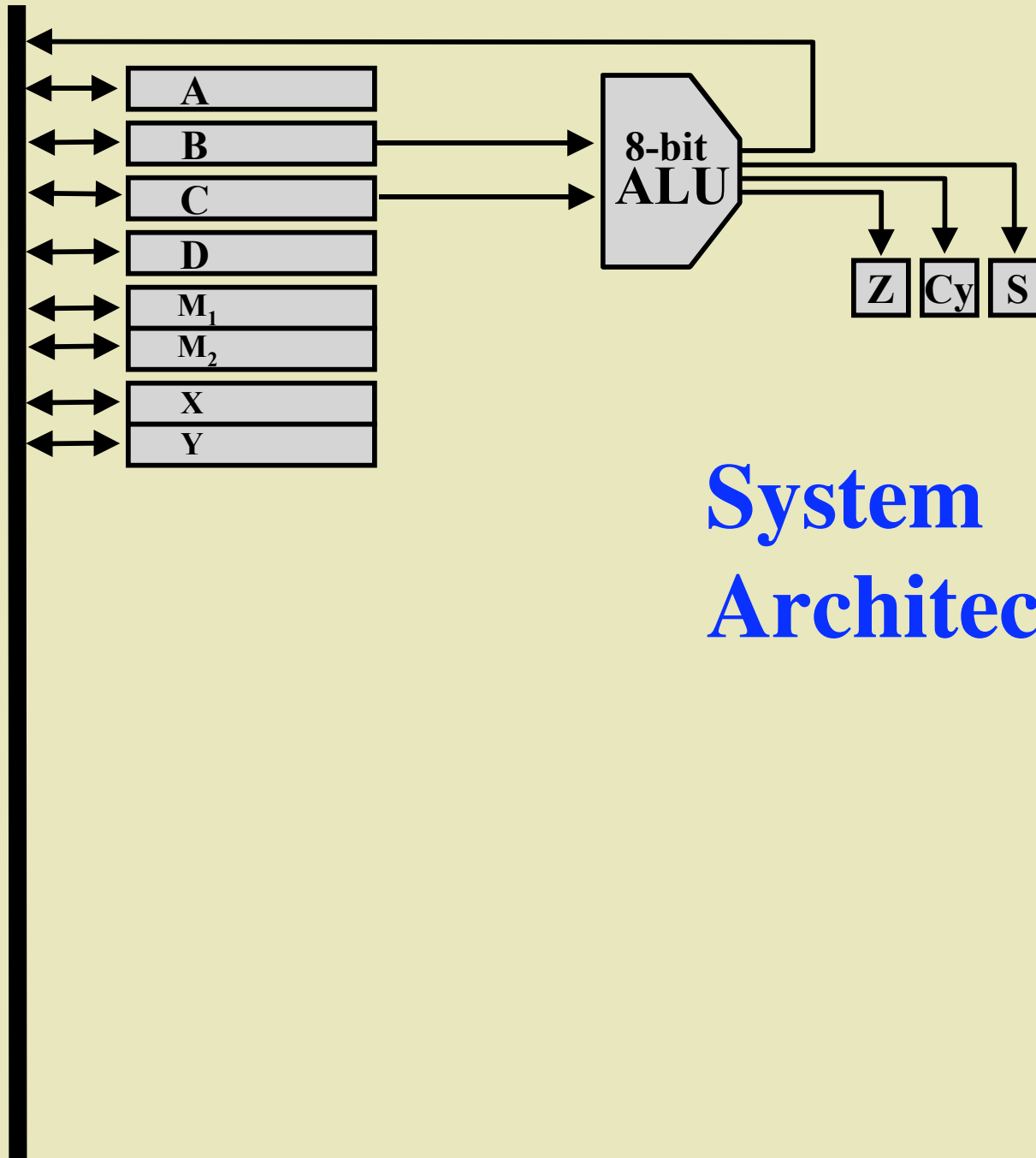

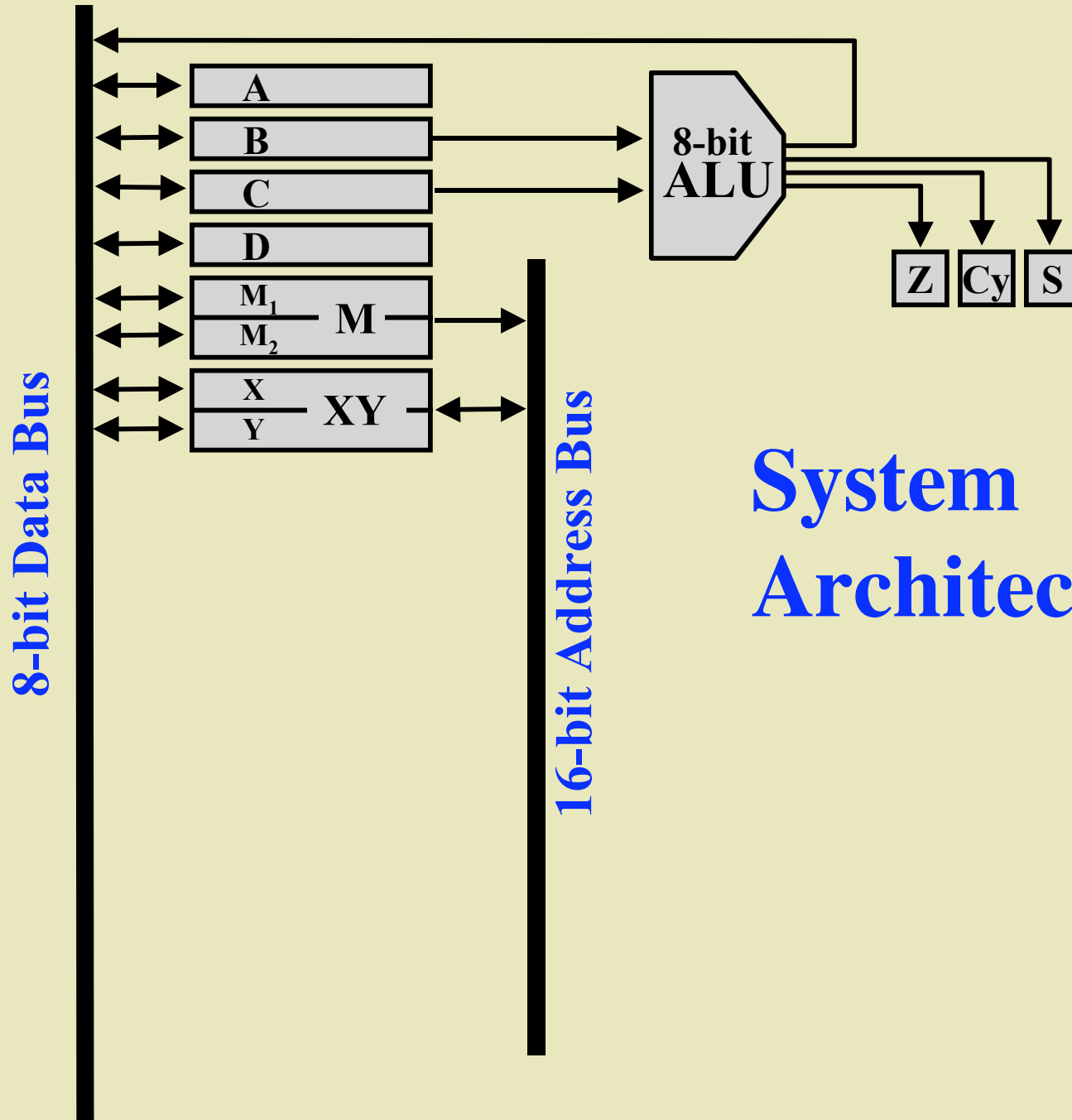


# System Architecture

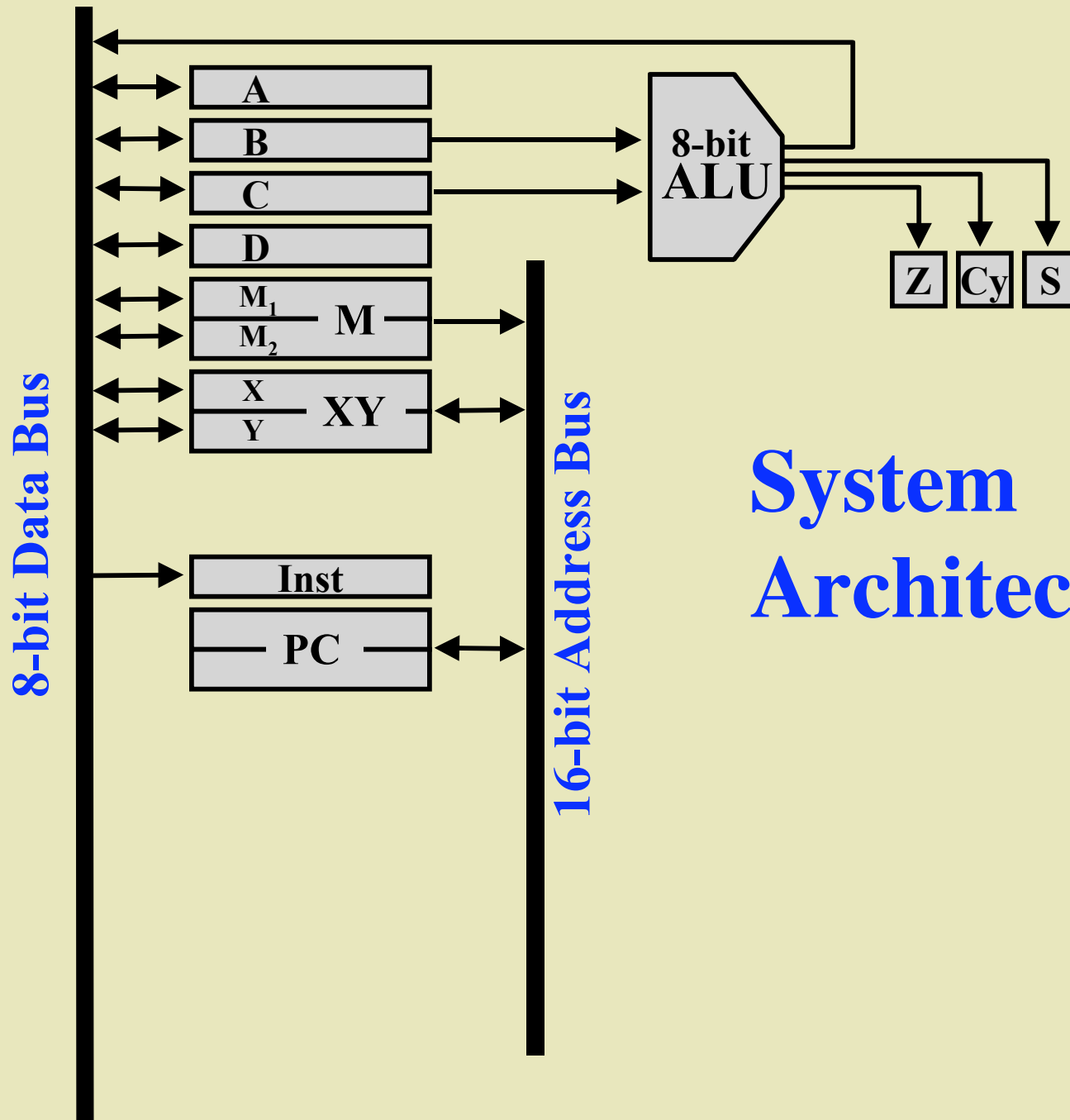


# System Architecture




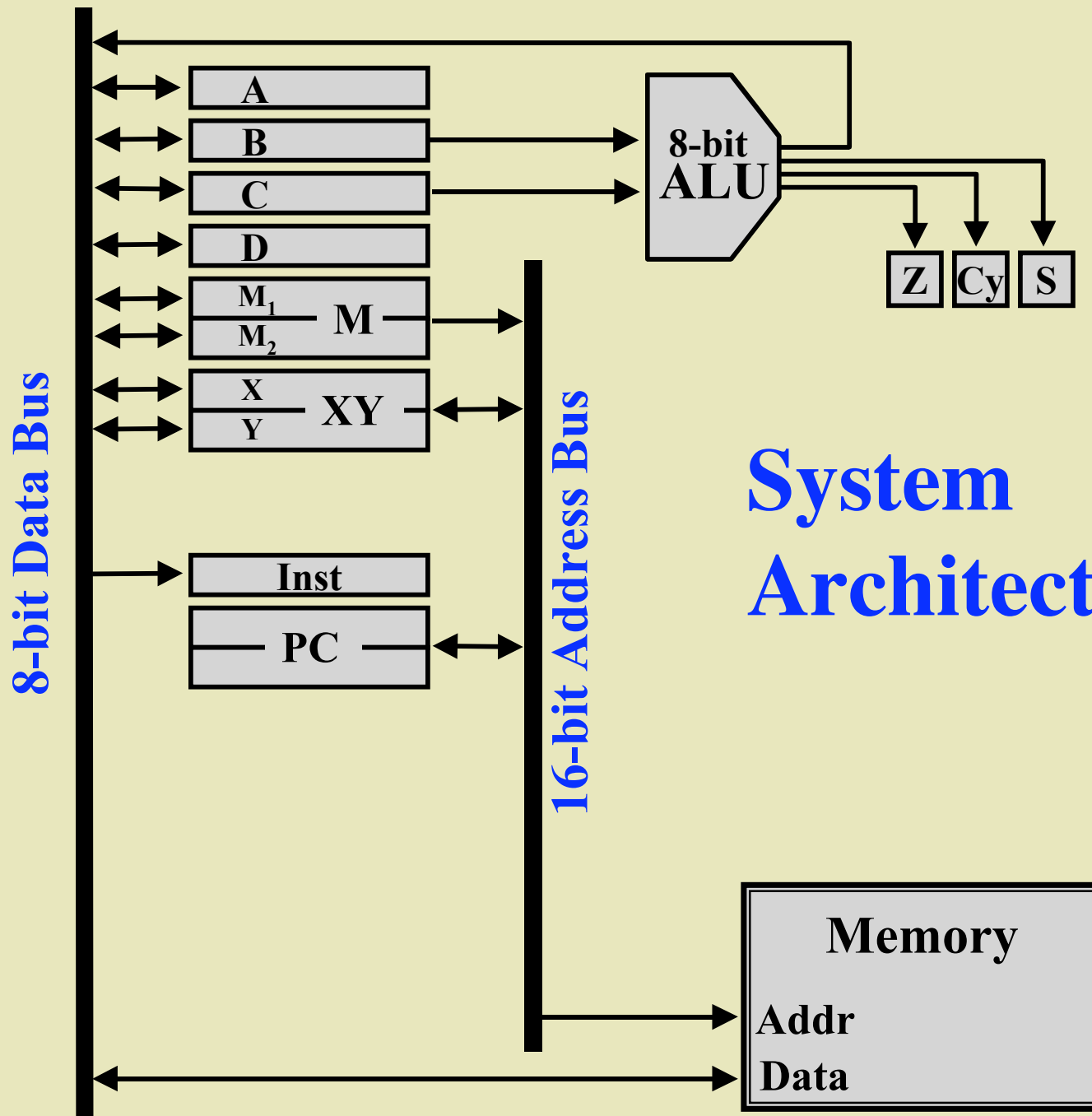


# System Architecture

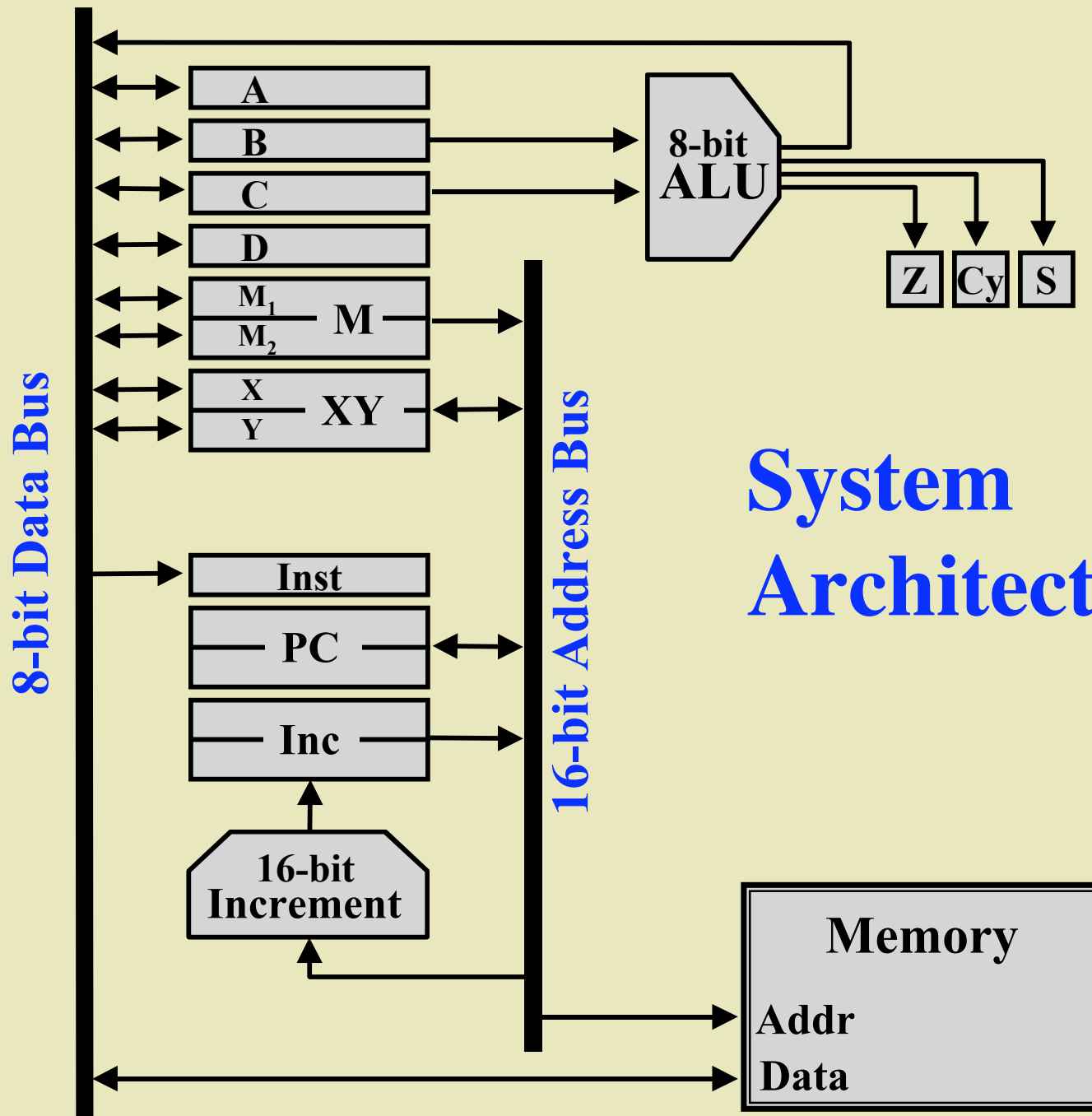

# System Architecture

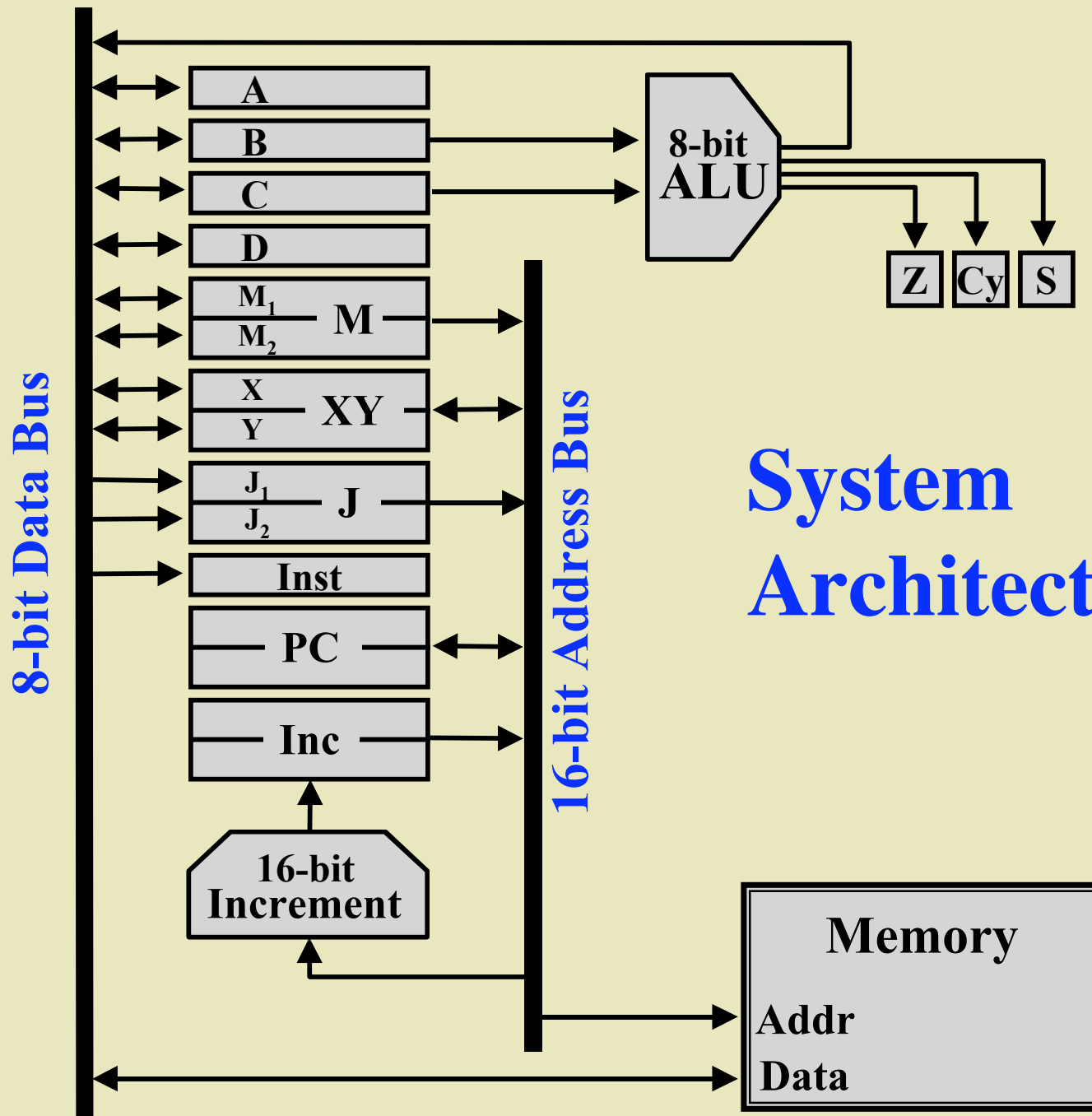

# System Architecture

 

**32K Byte Static  
RAM Chip**


**LEDs**

**8 FET Power Transistors  
(to drive relays during  
a memory-read operation)**


Mem  
Read

Mem  
Write


Bus to  
Mem

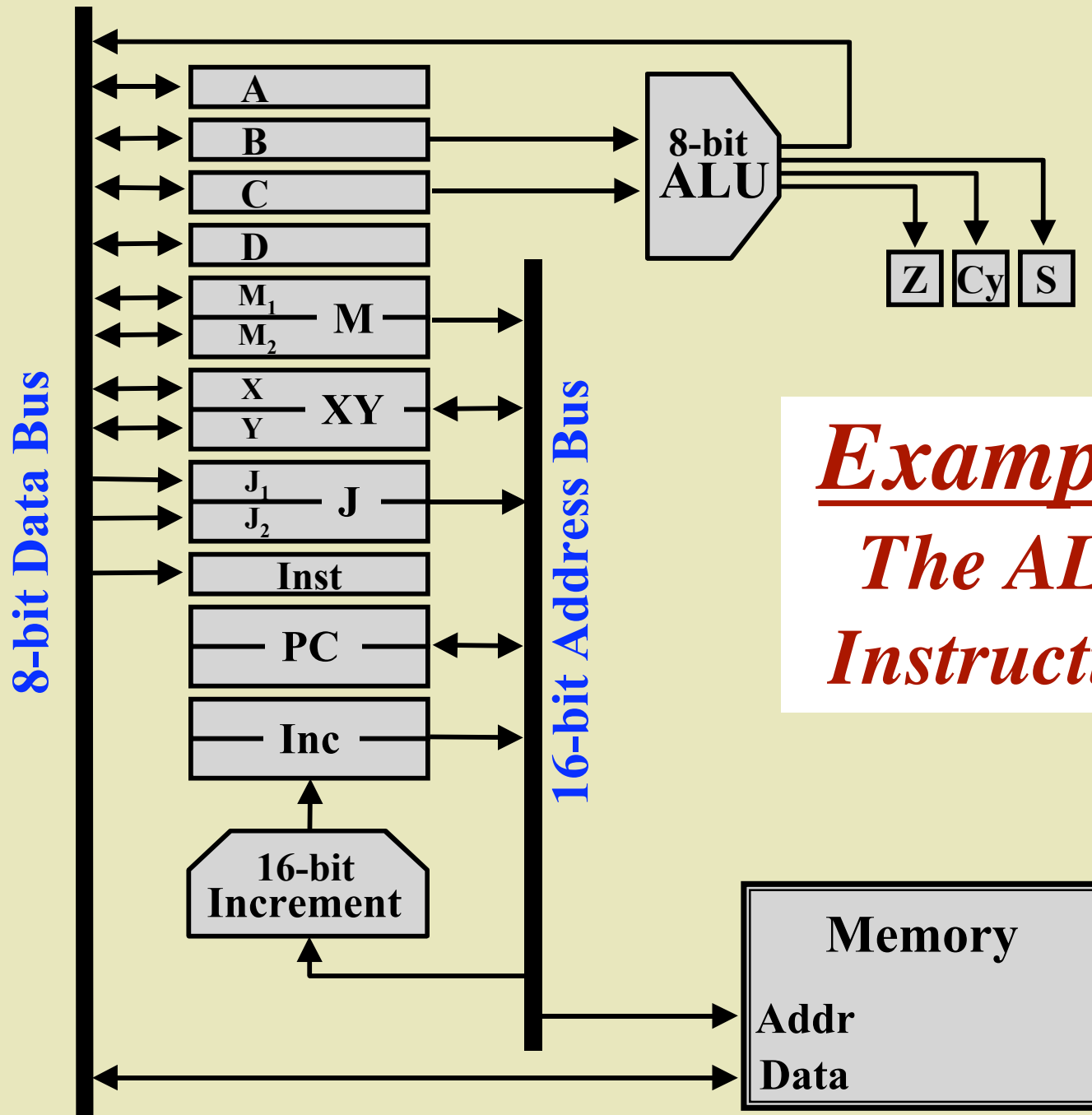


*Example:*  
*The ALU*  
*Instruction*

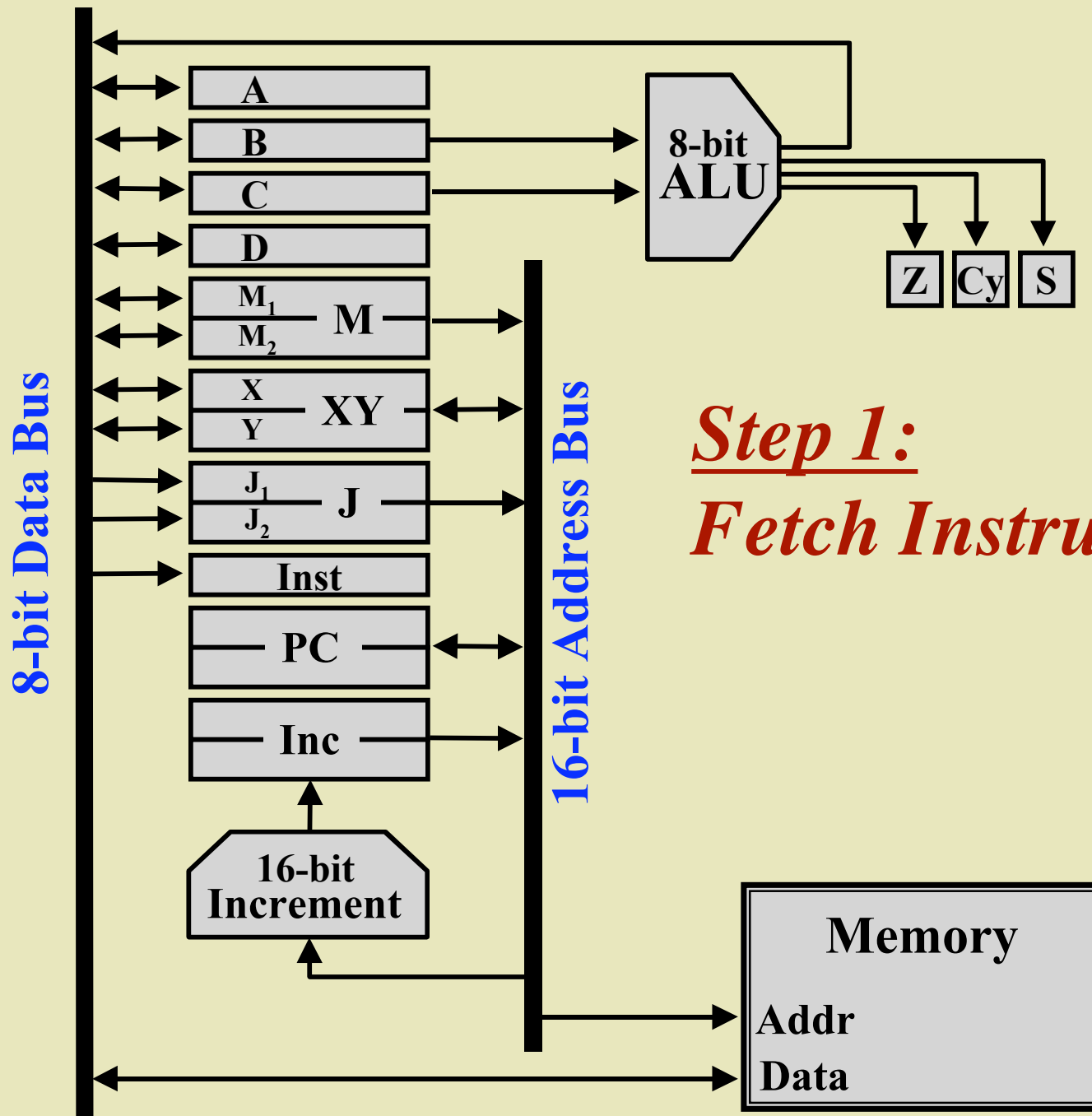

***Step 1:  
Fetch Instruction***

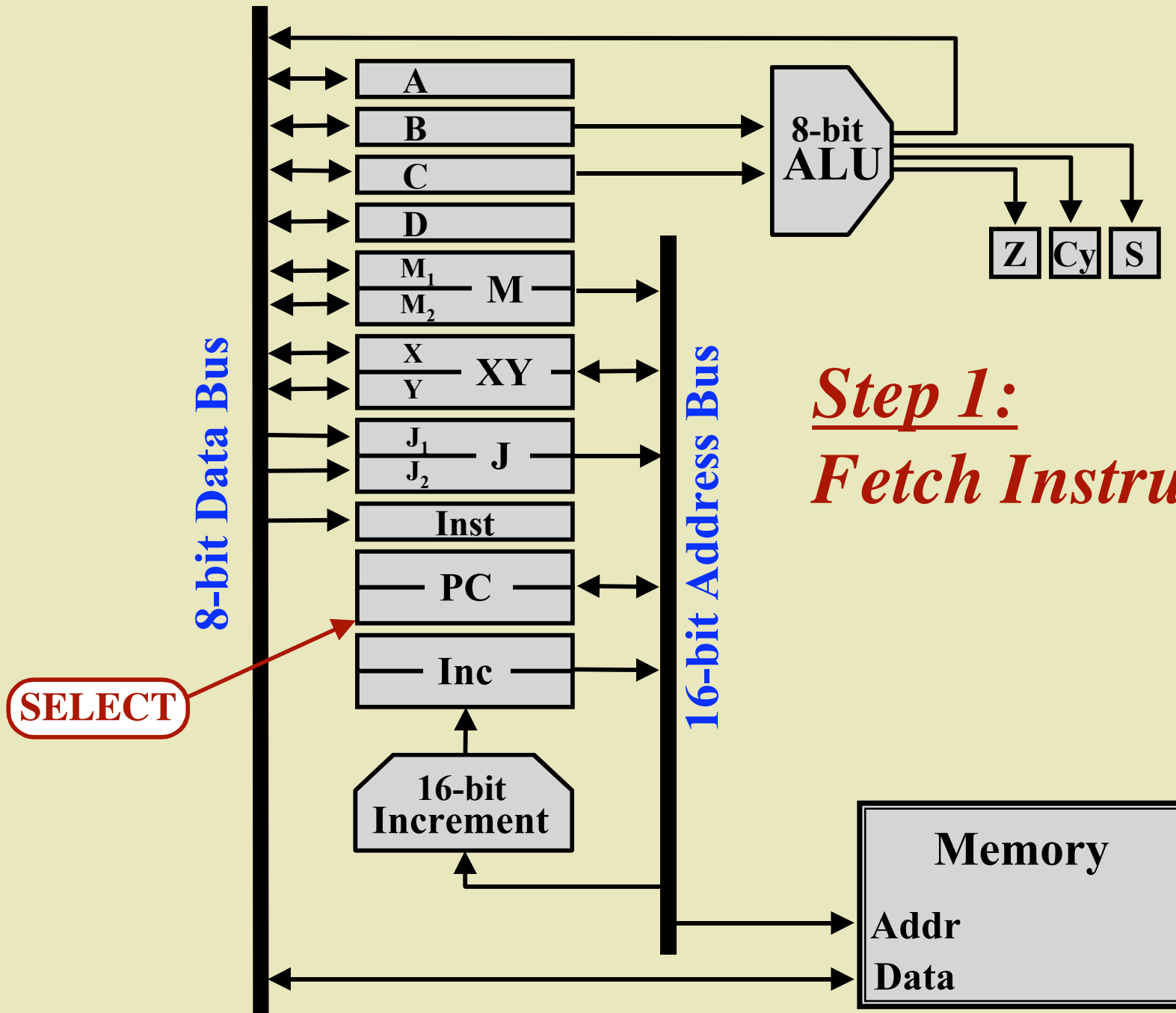


***Step 1:  
Fetch Instruction***

 



***Step 1:  
Fetch Instruction***




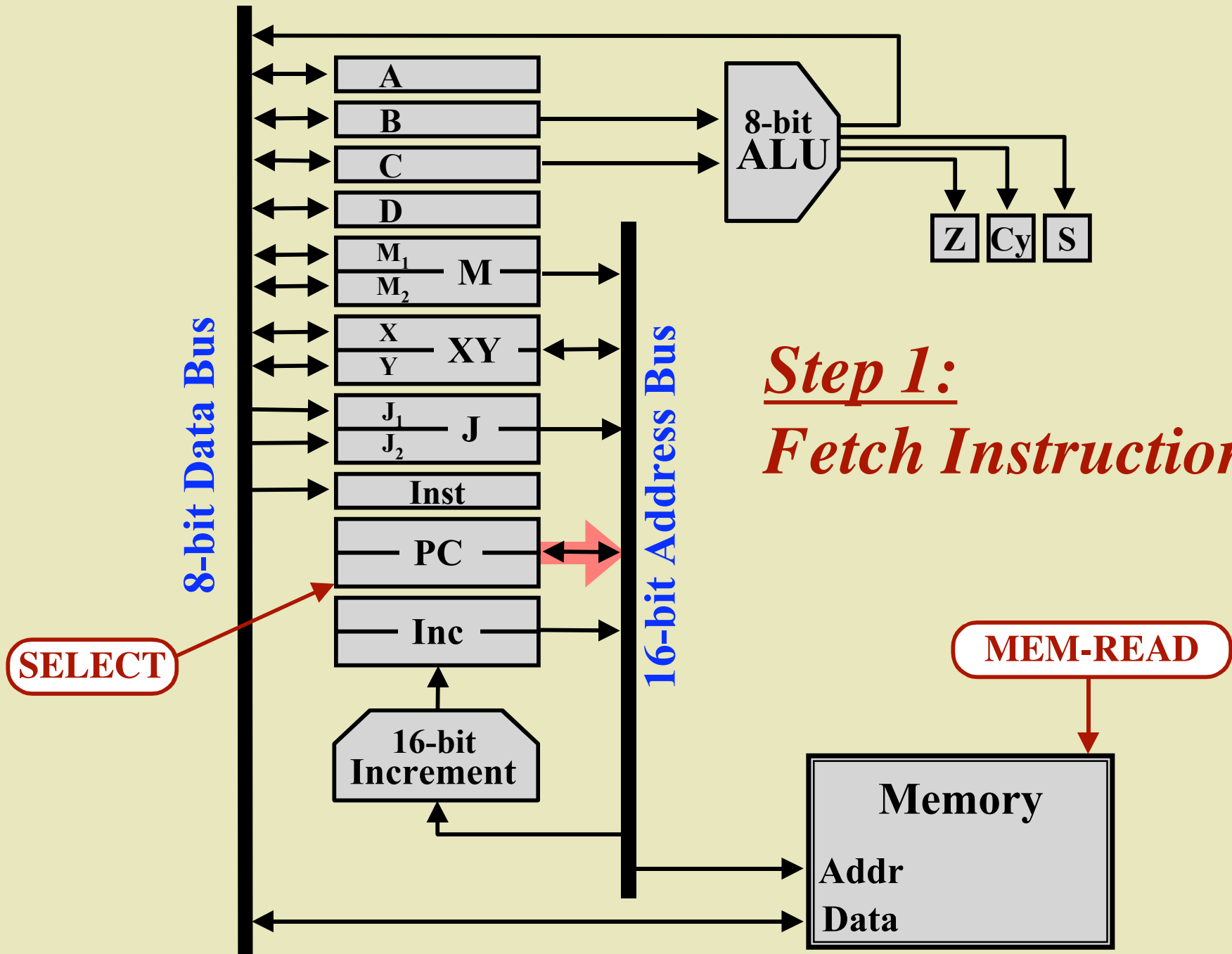

*Step 1:  
Fetch Instruction*

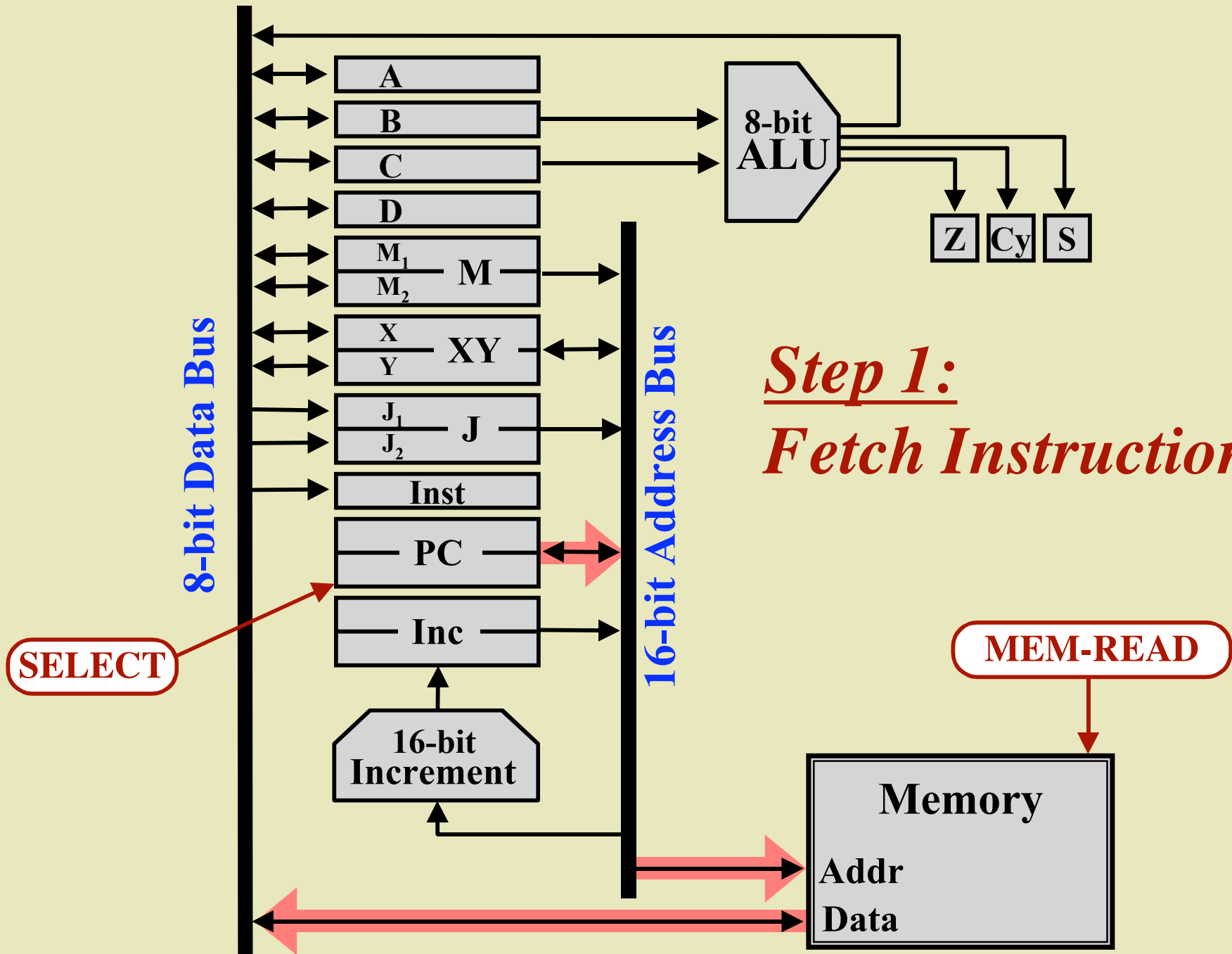


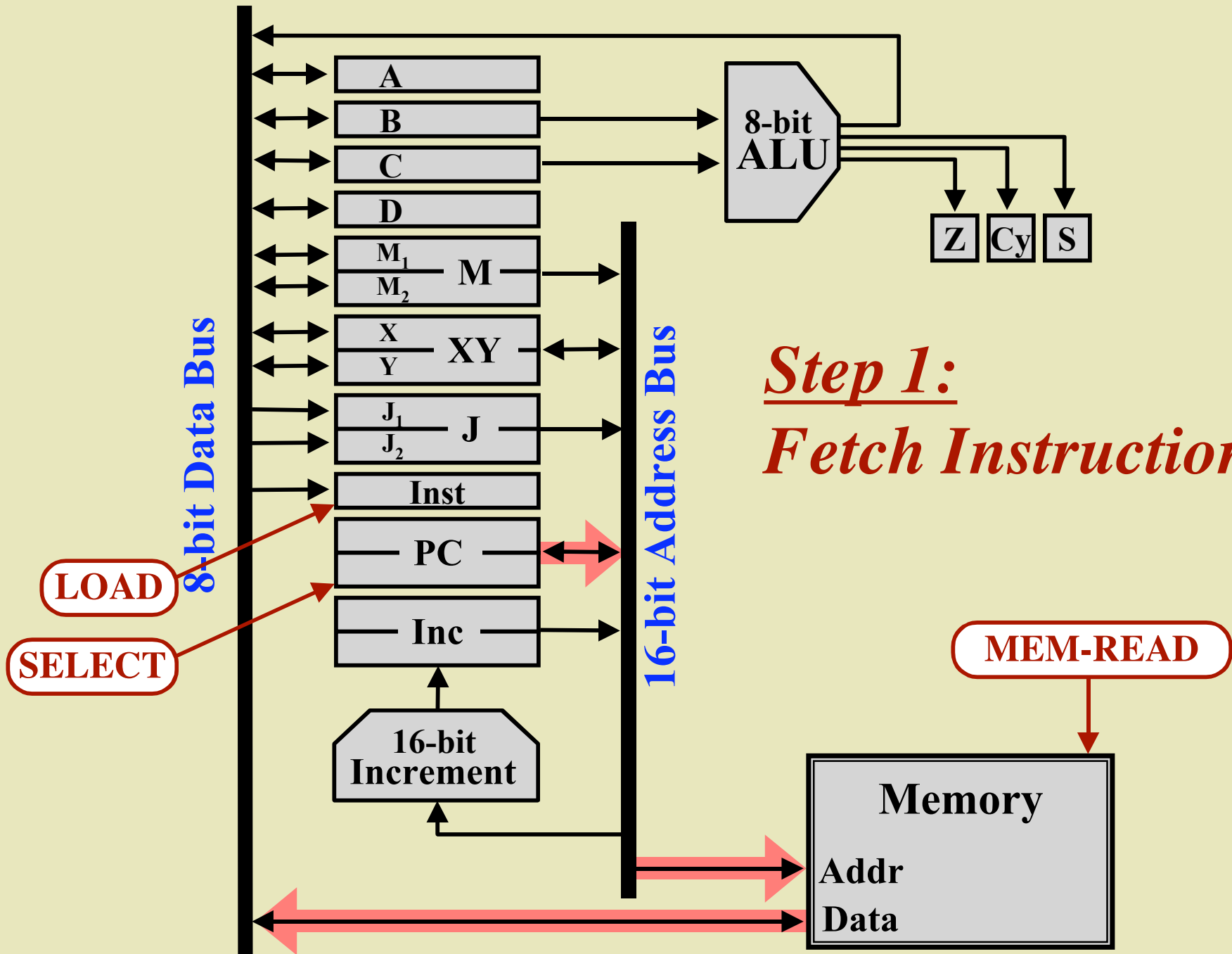

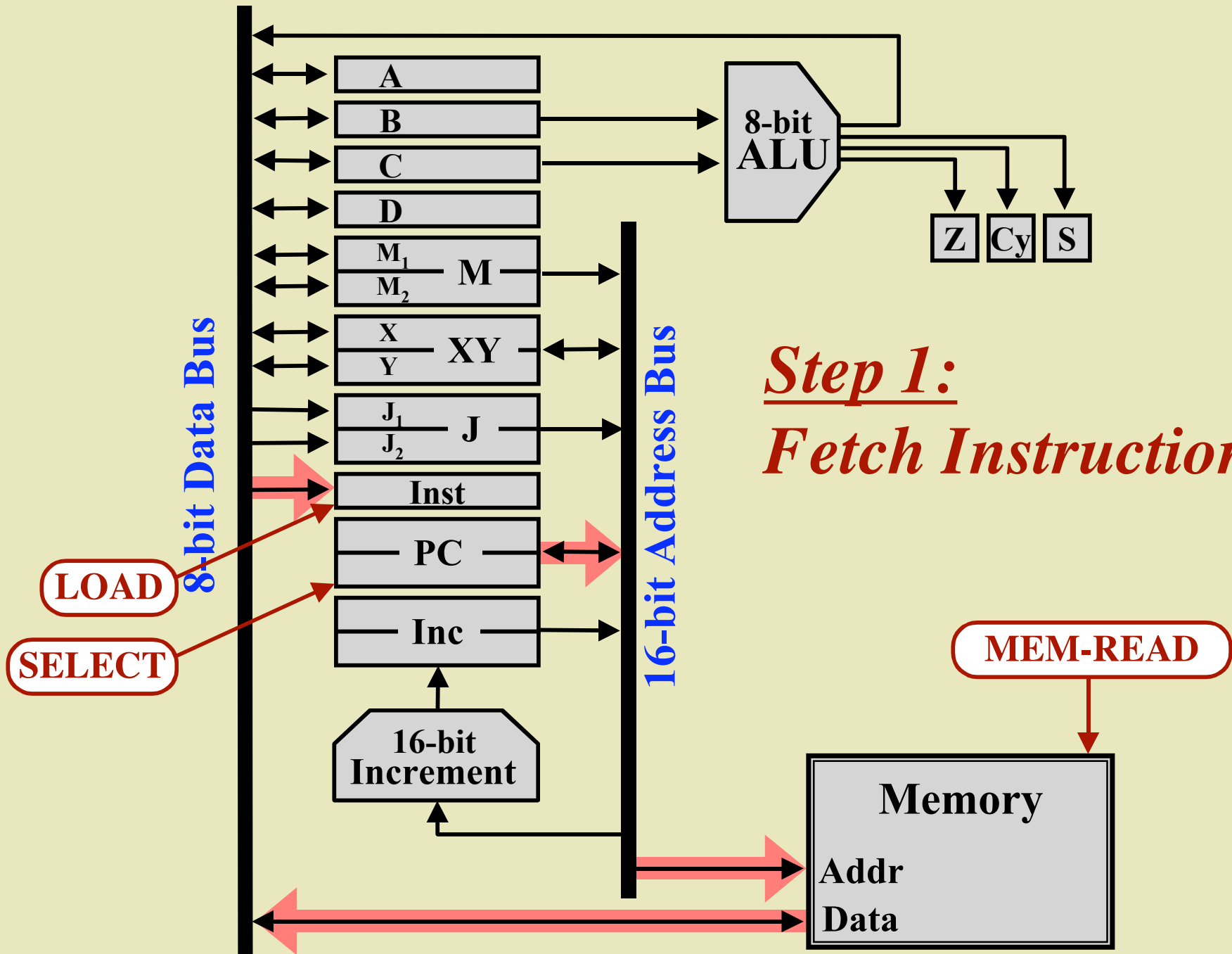


*Step 1:  
Fetch Instruction*


MEM-READ

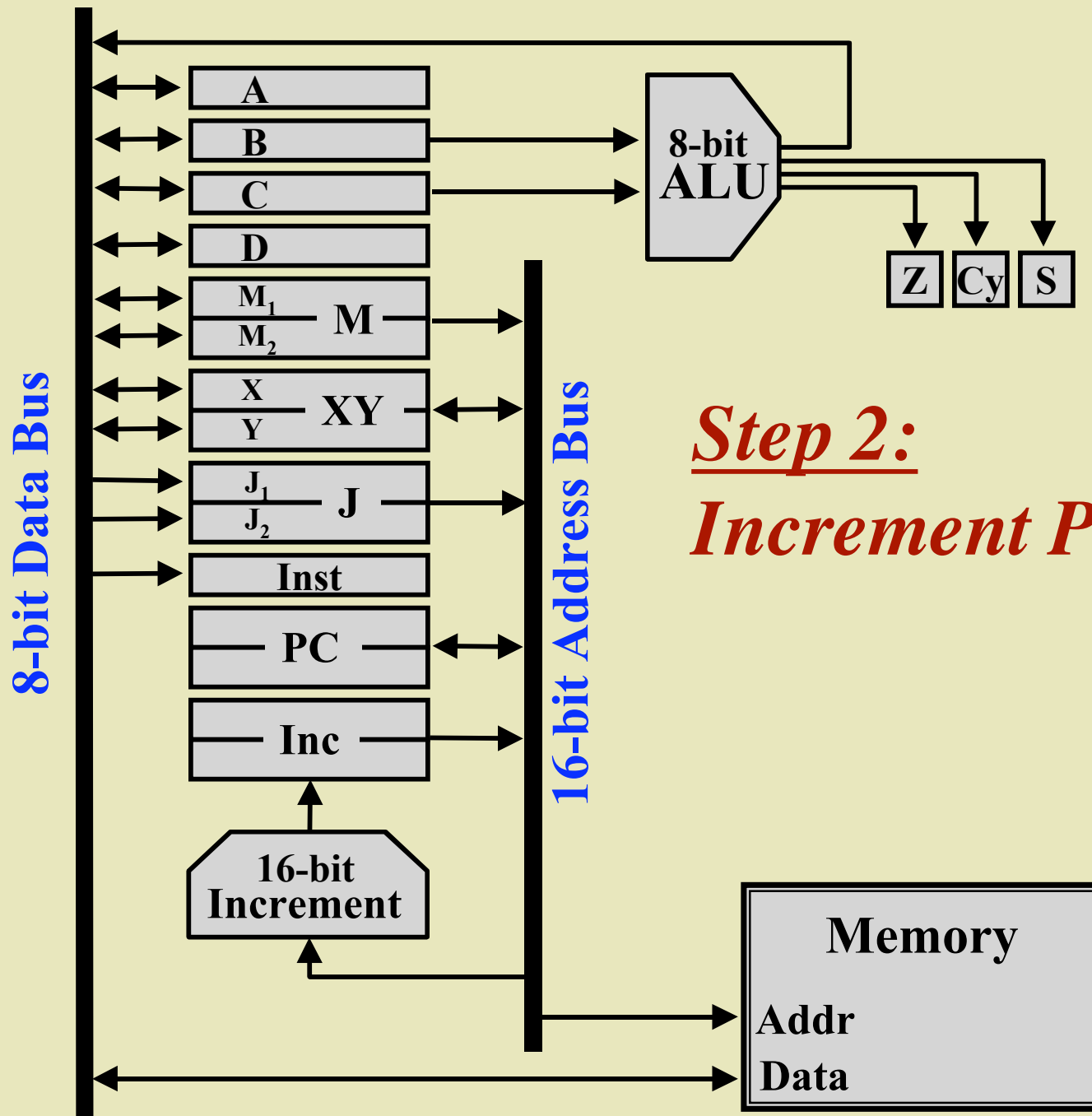


*Step 2:*  
*Increment PC*

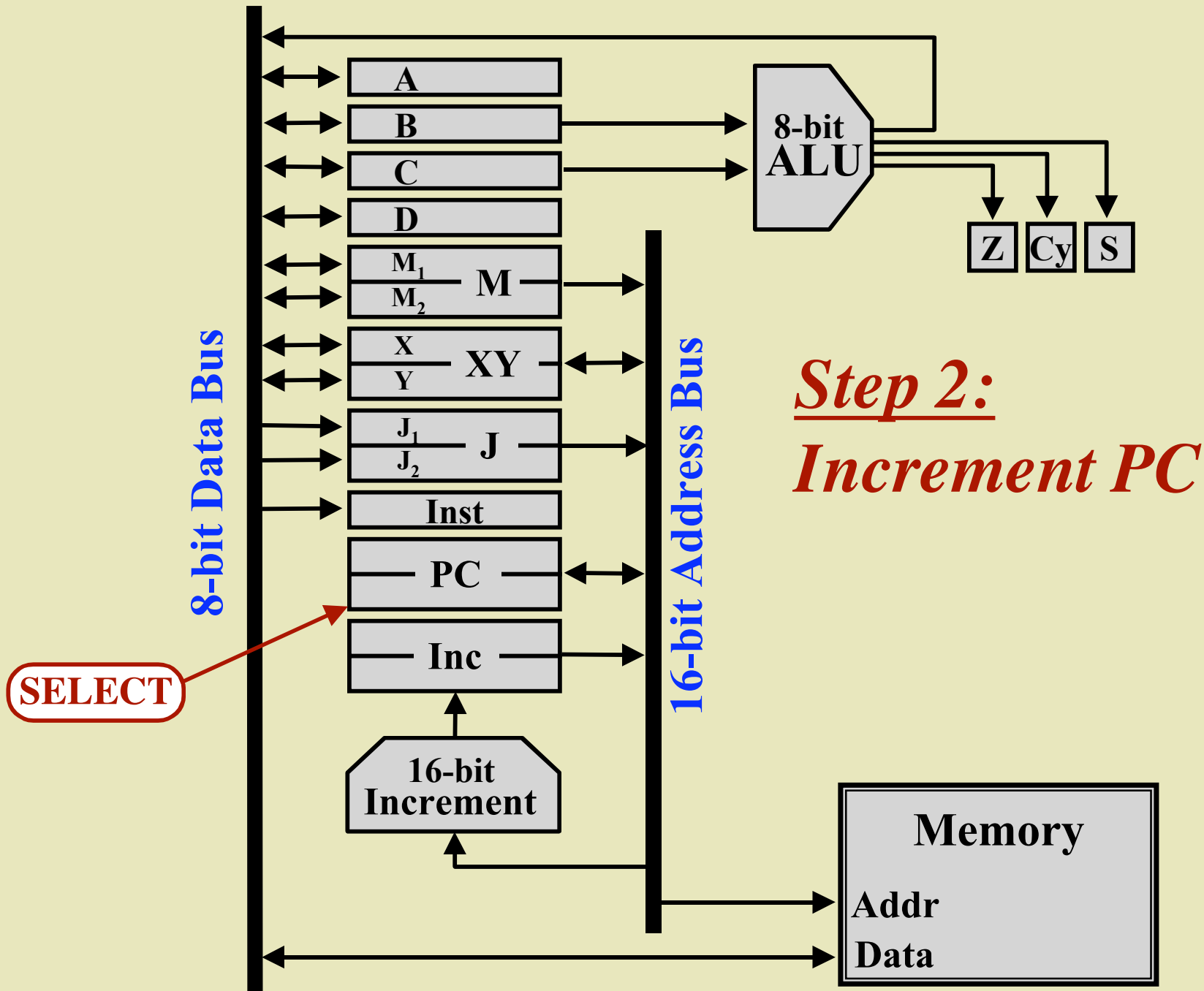

***Step 2:  
Increment PC***

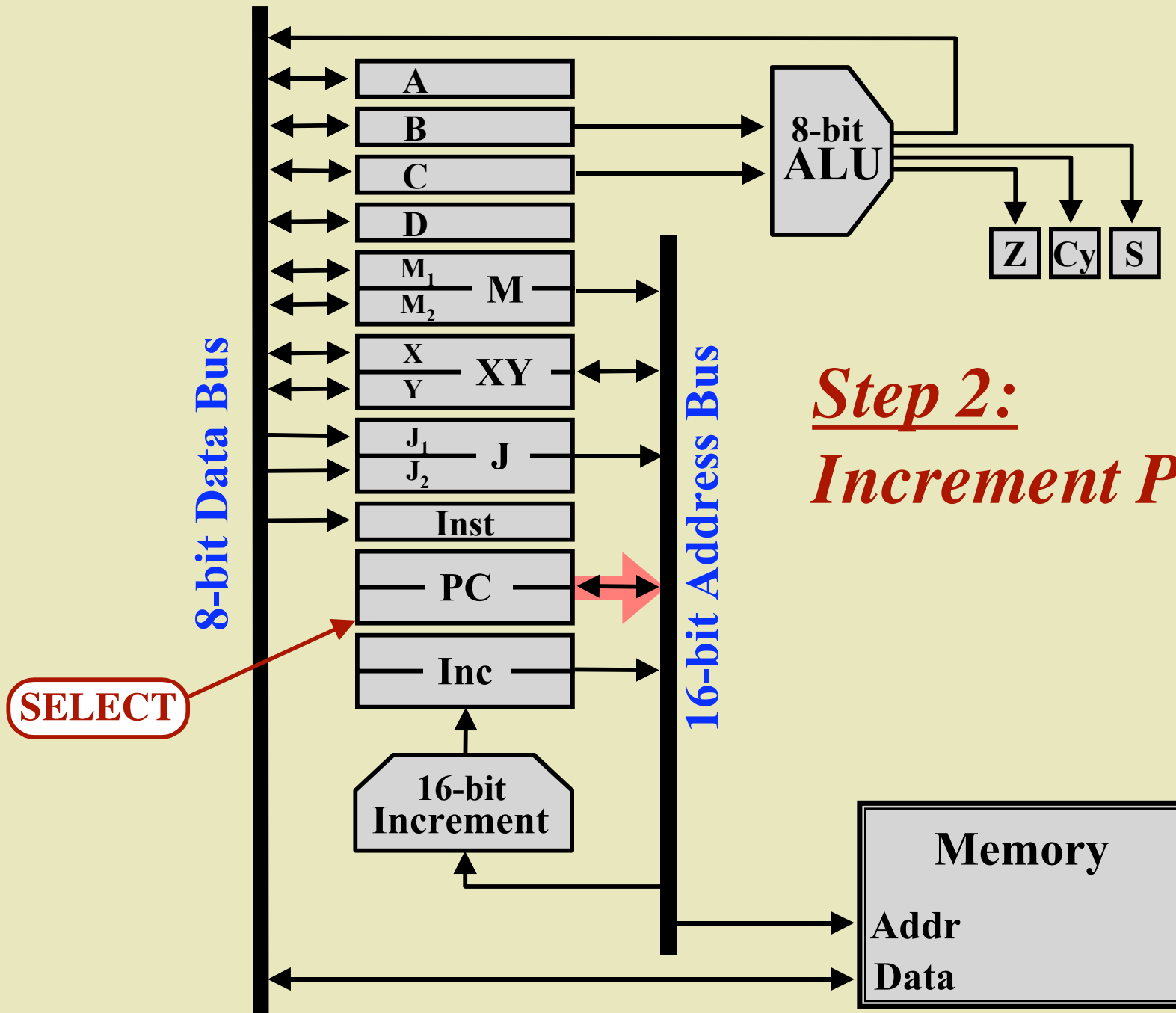


*Step 2:*  
*Increment PC*

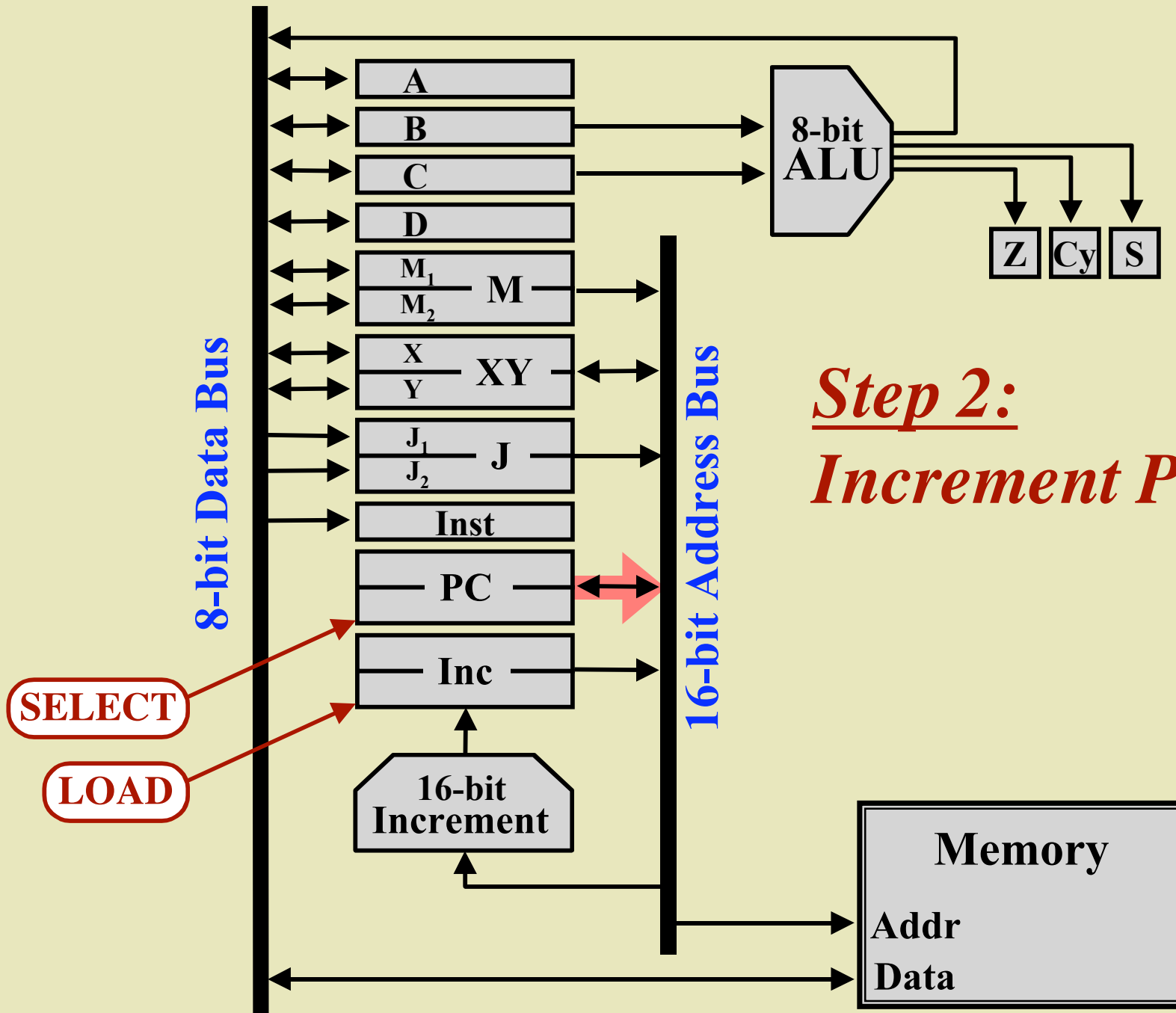


*Step 2:*  
*Increment PC*




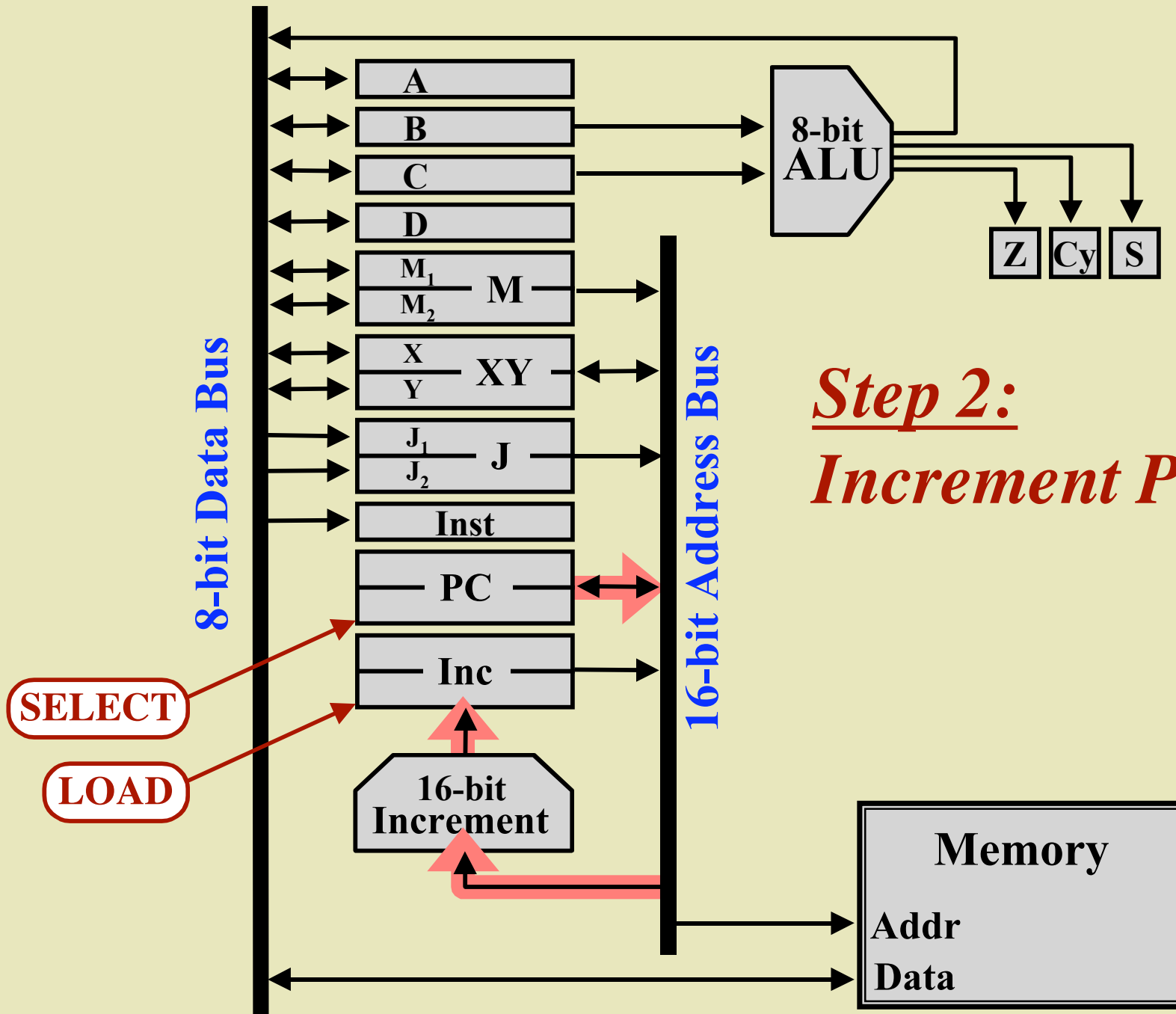



***Step 2:  
Increment PC***

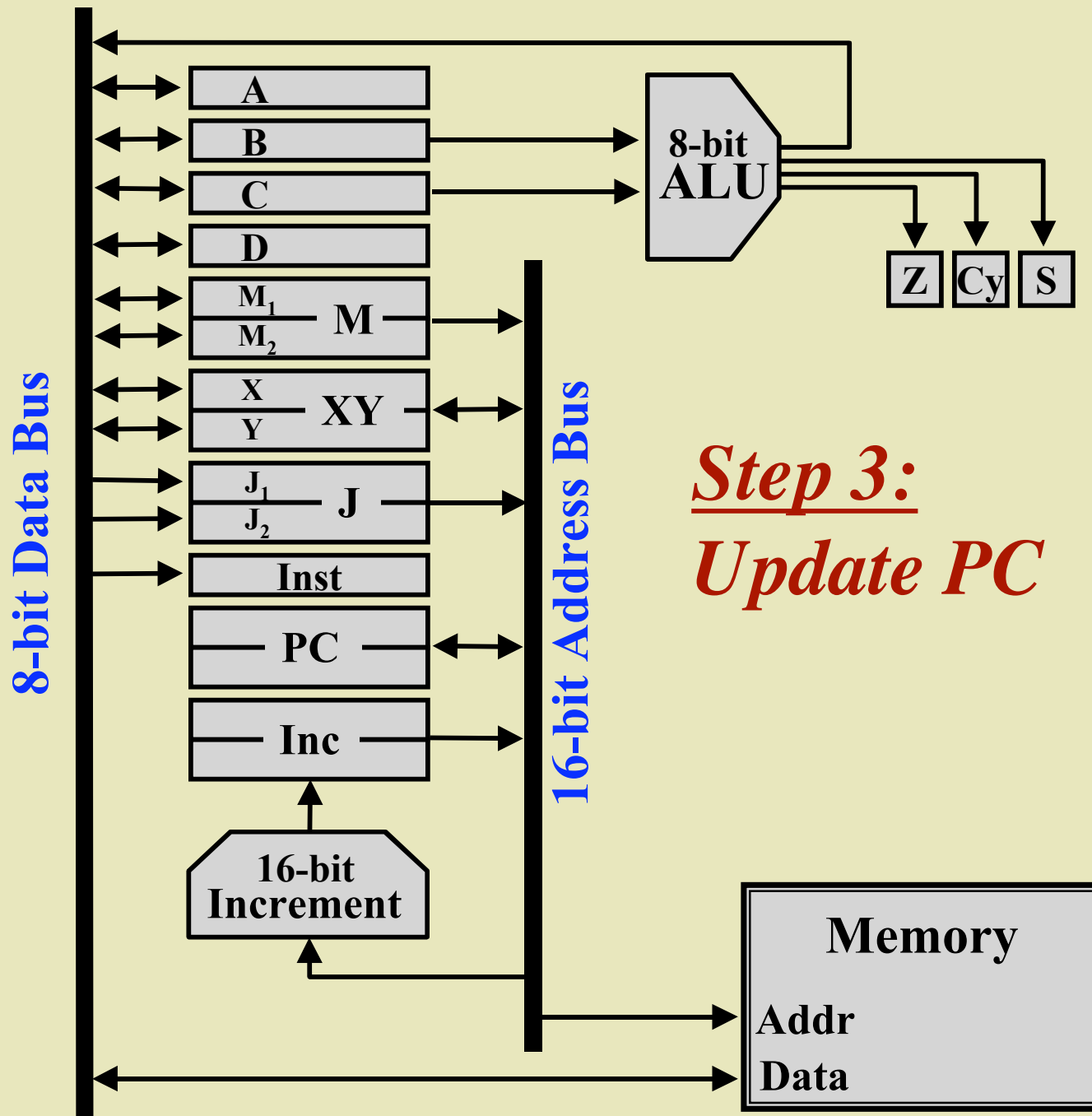


*Step 3:  
Update PC*

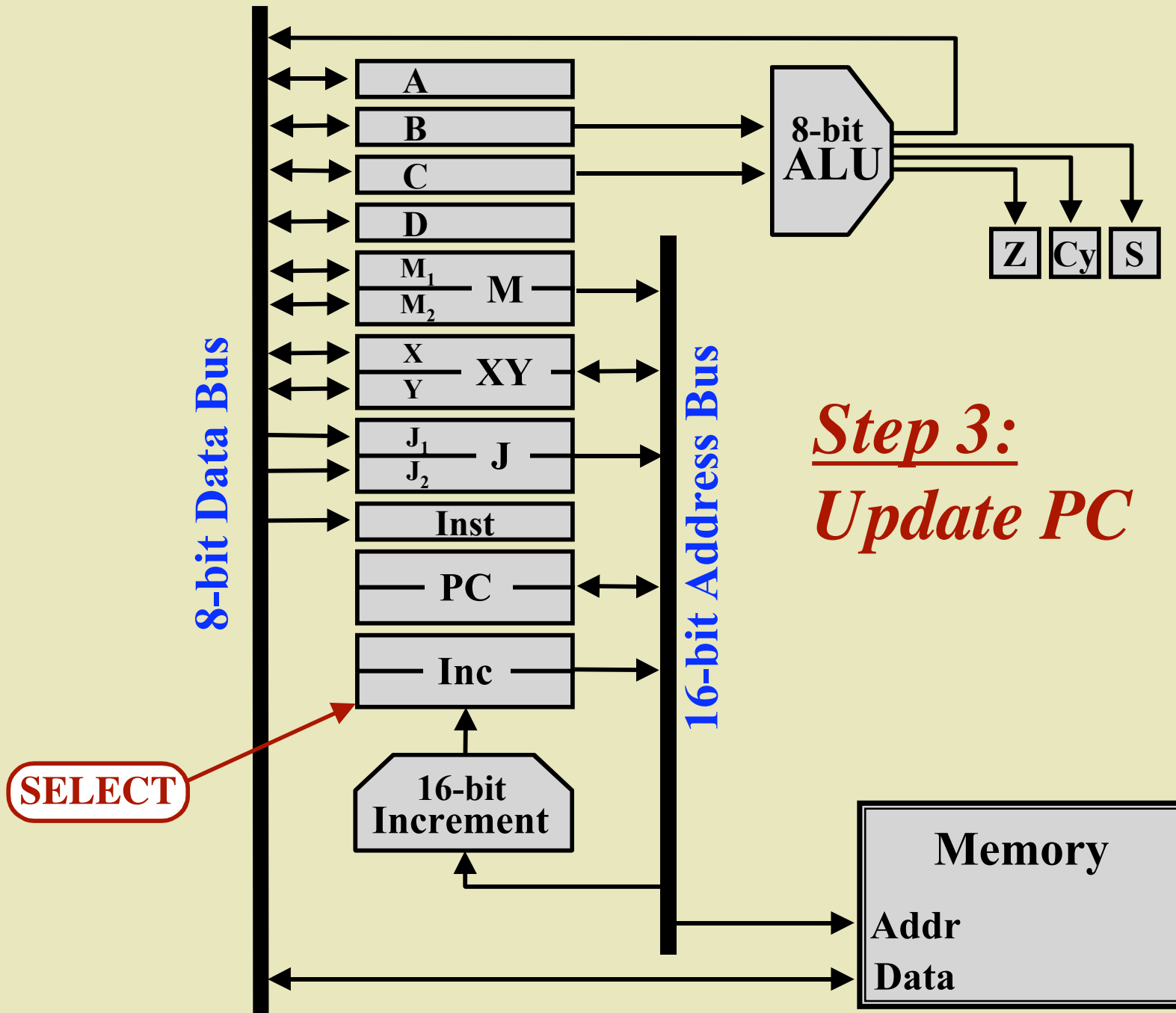


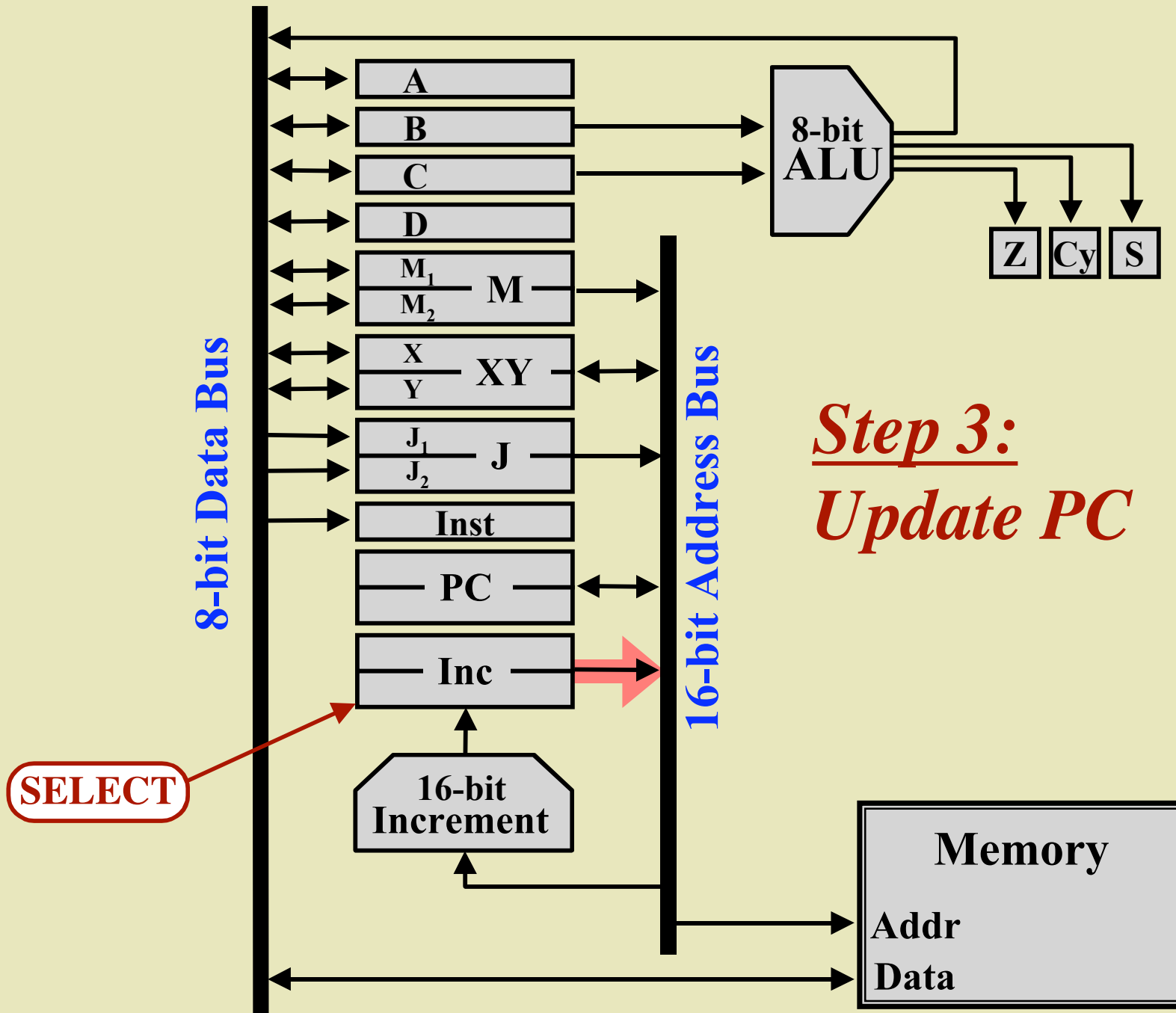

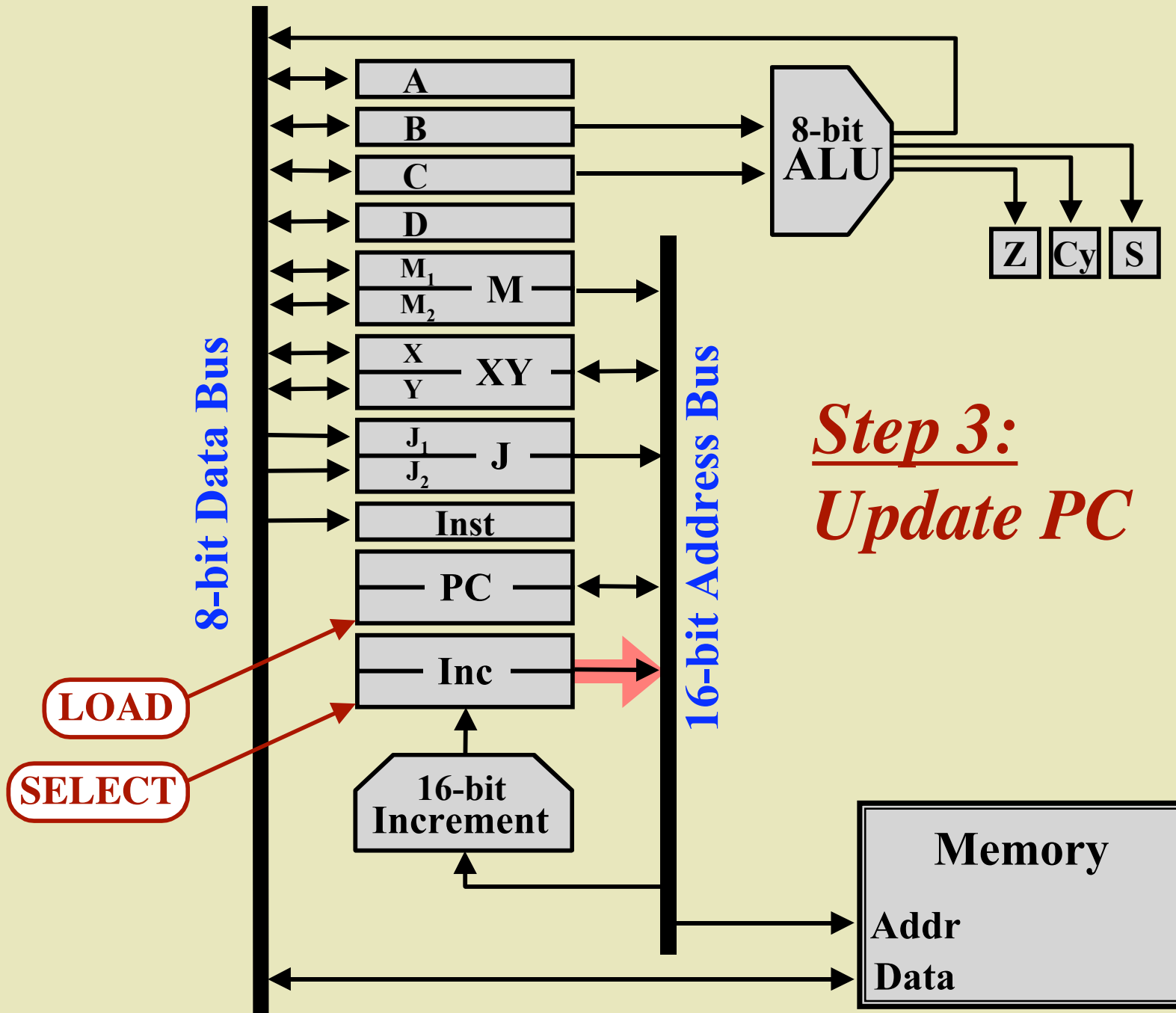


*Step 3:  
Update PC*

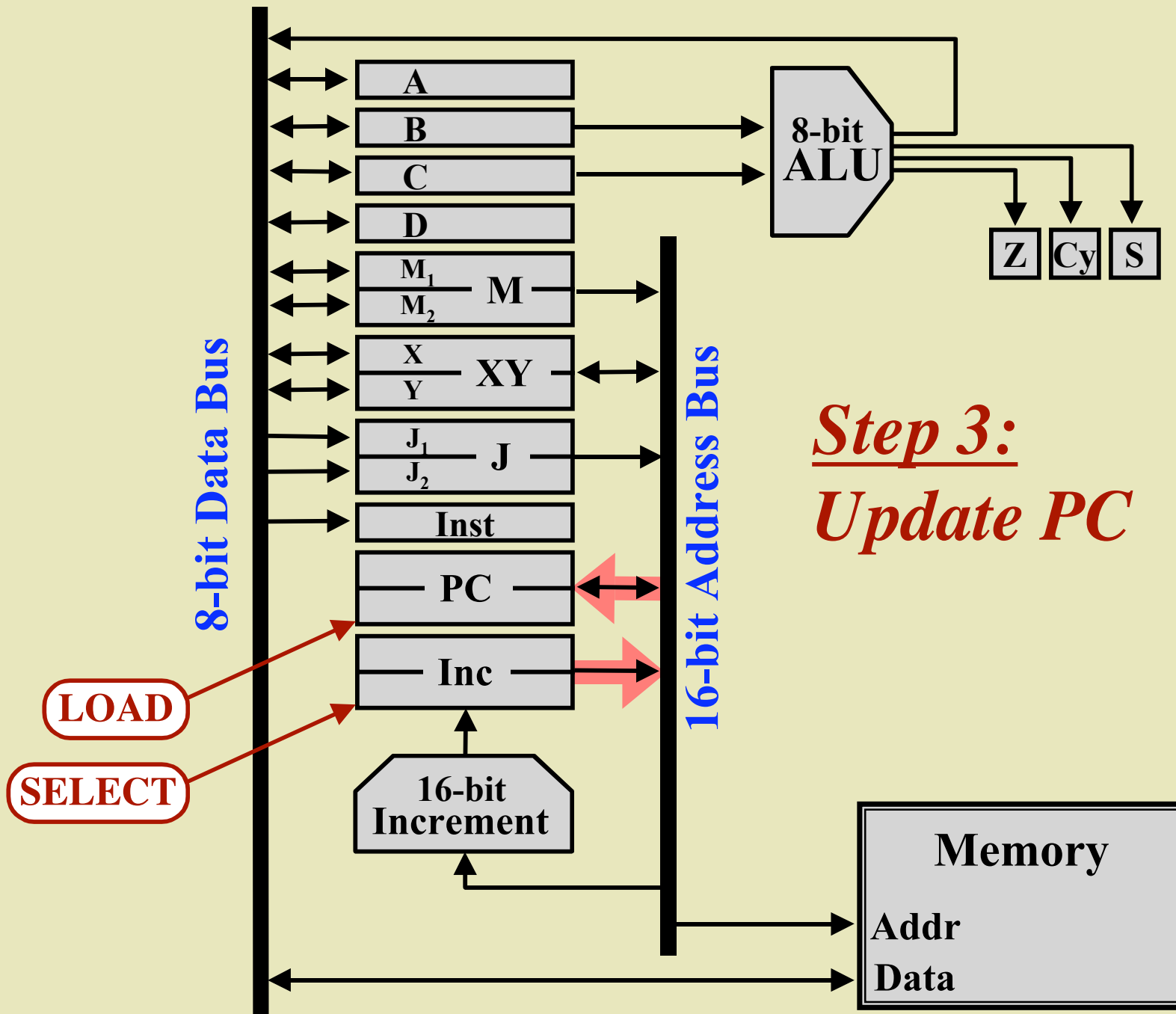

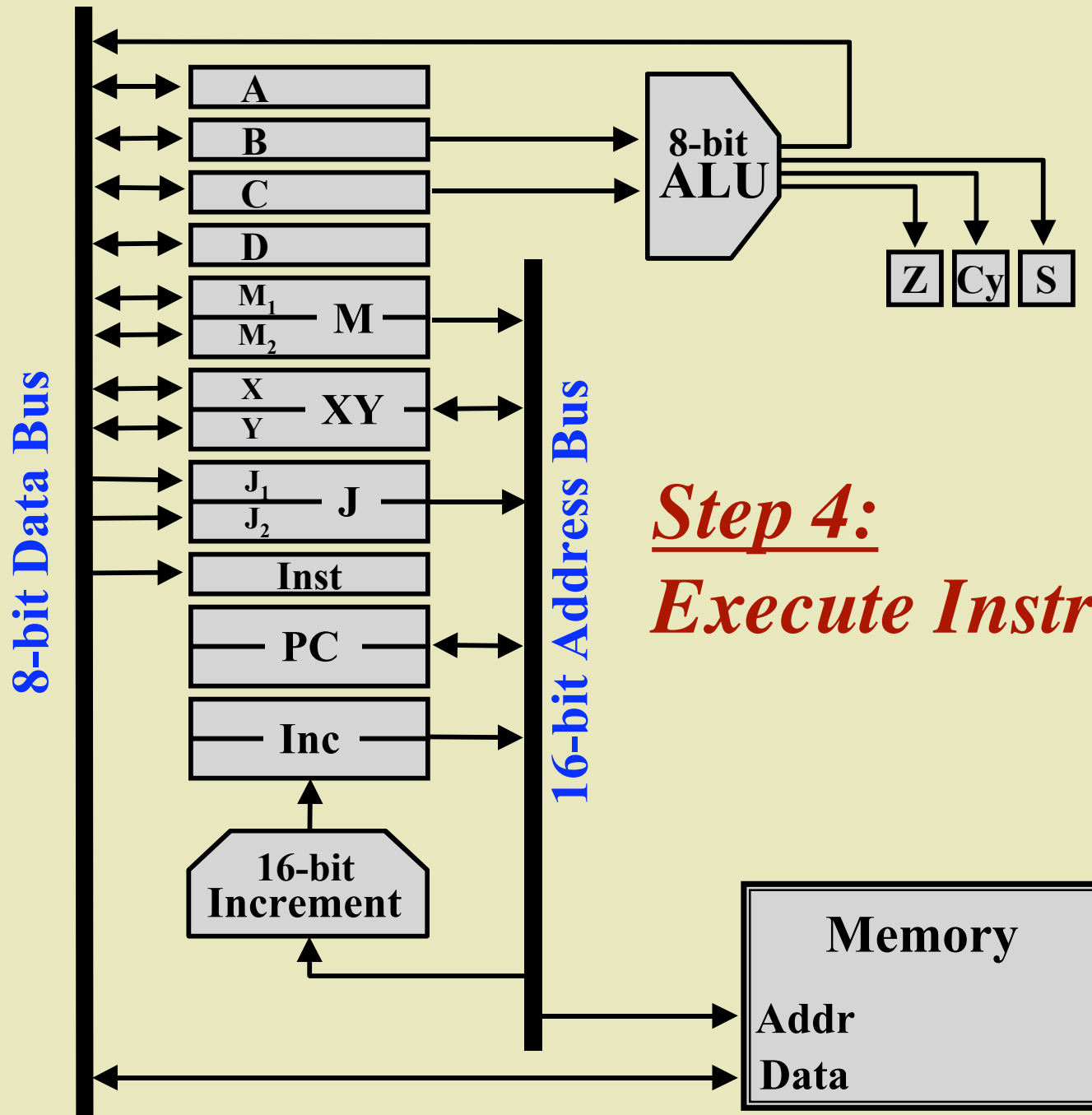


***Step 4:  
Execute Instruction***

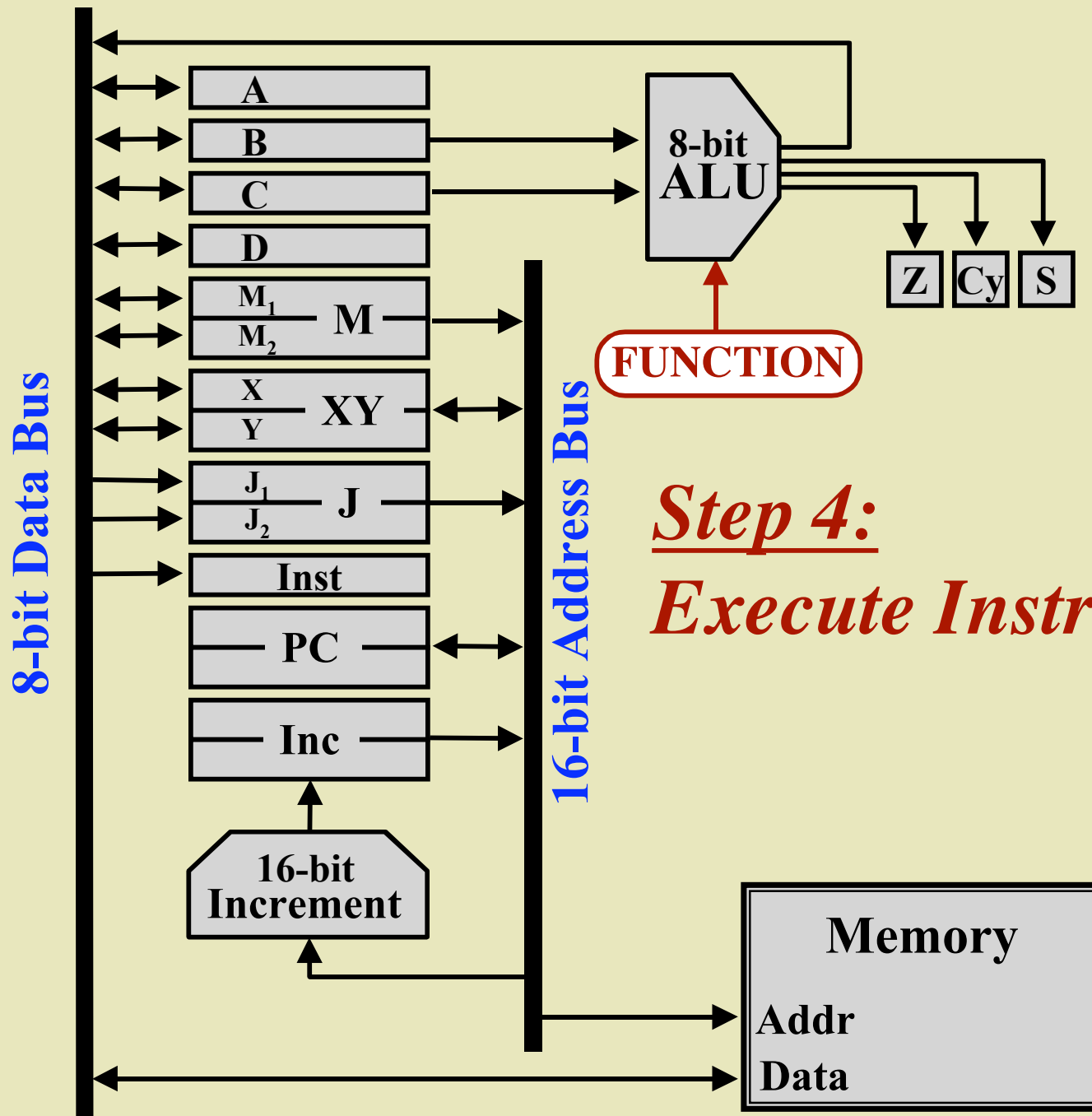


***Step 4:  
Execute Instruction***



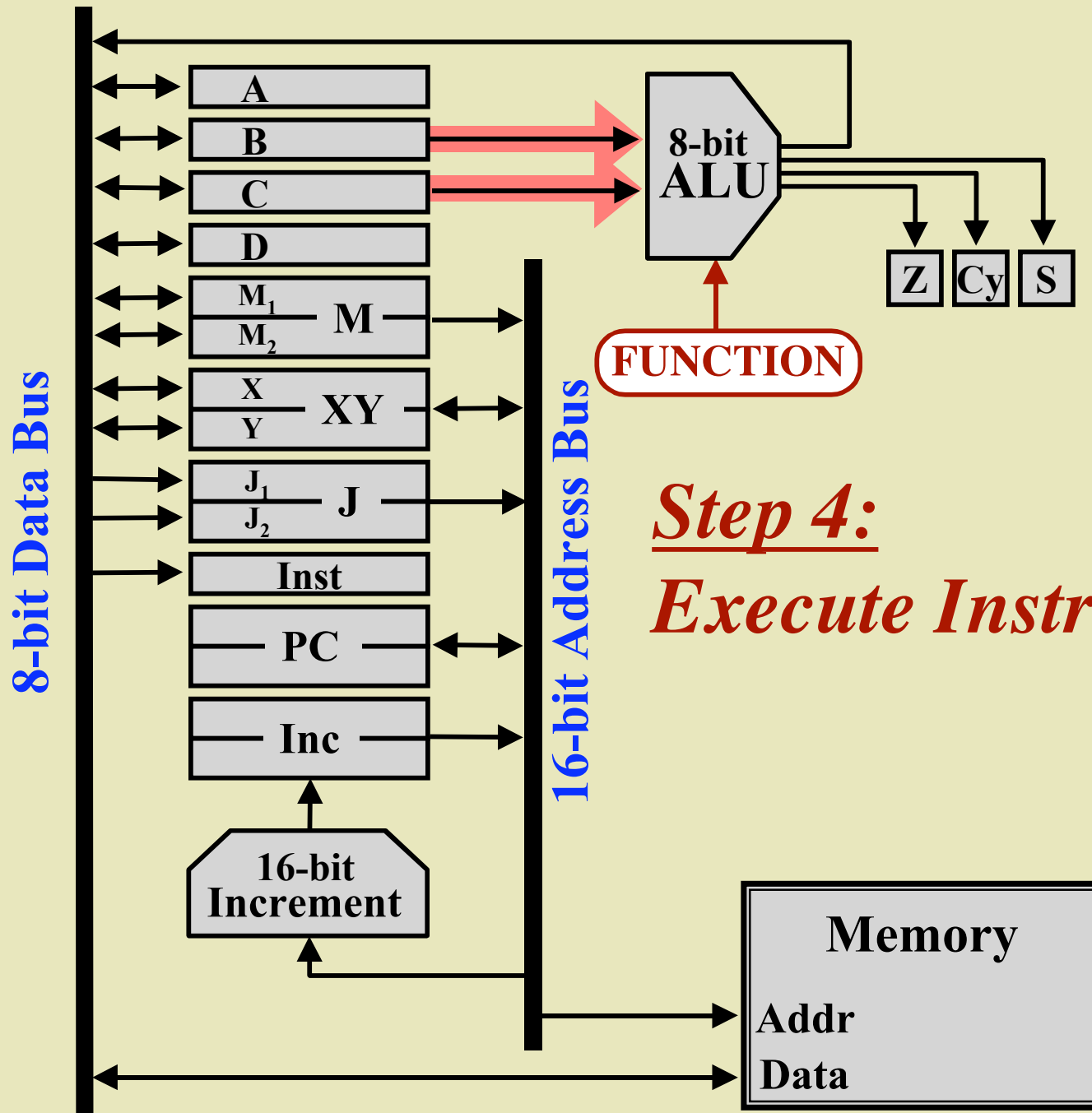



***Step 4:  
Execute Instruction***

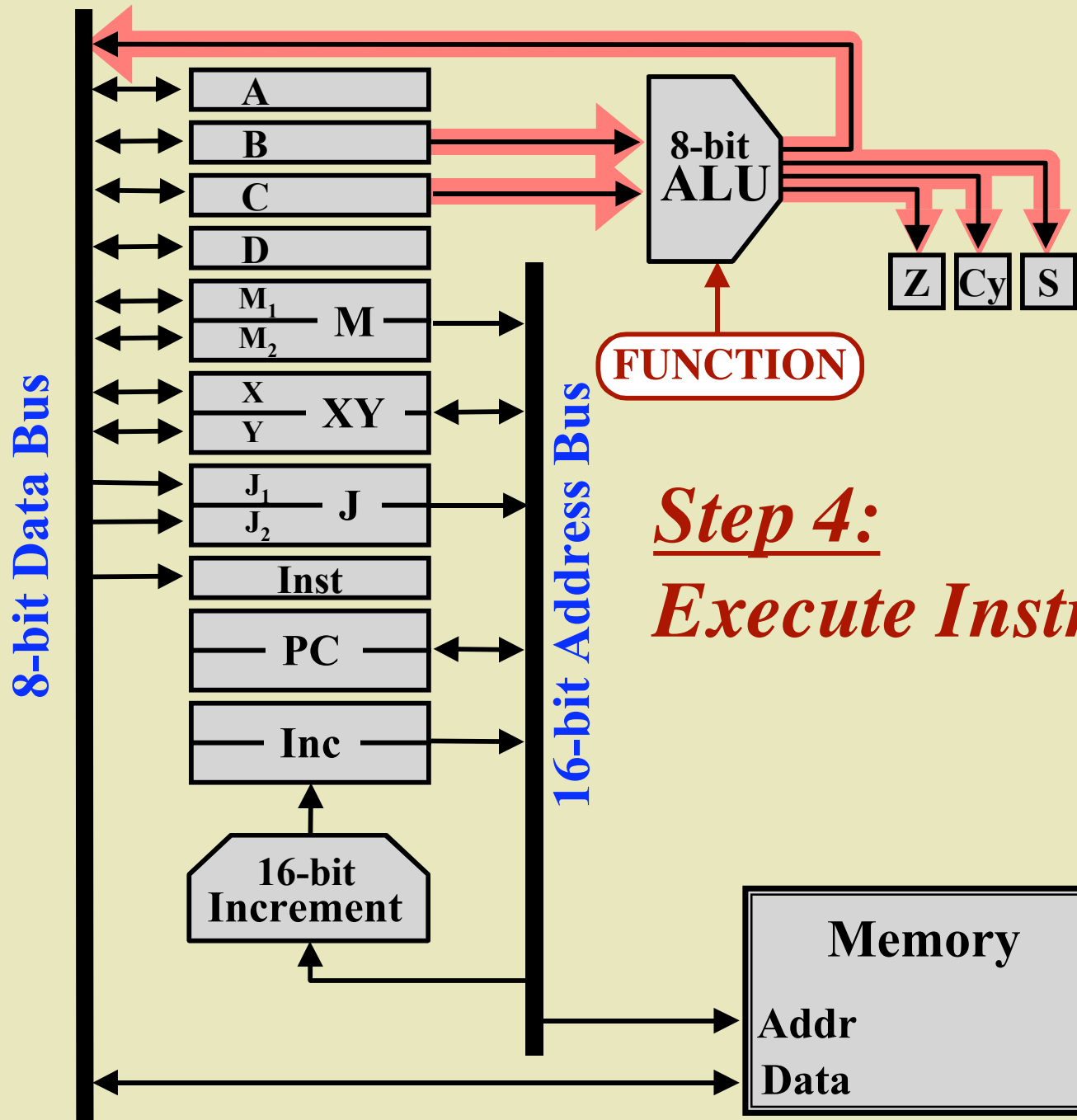


**FUNCTION**

*Step 4:  
Execute Instruction*

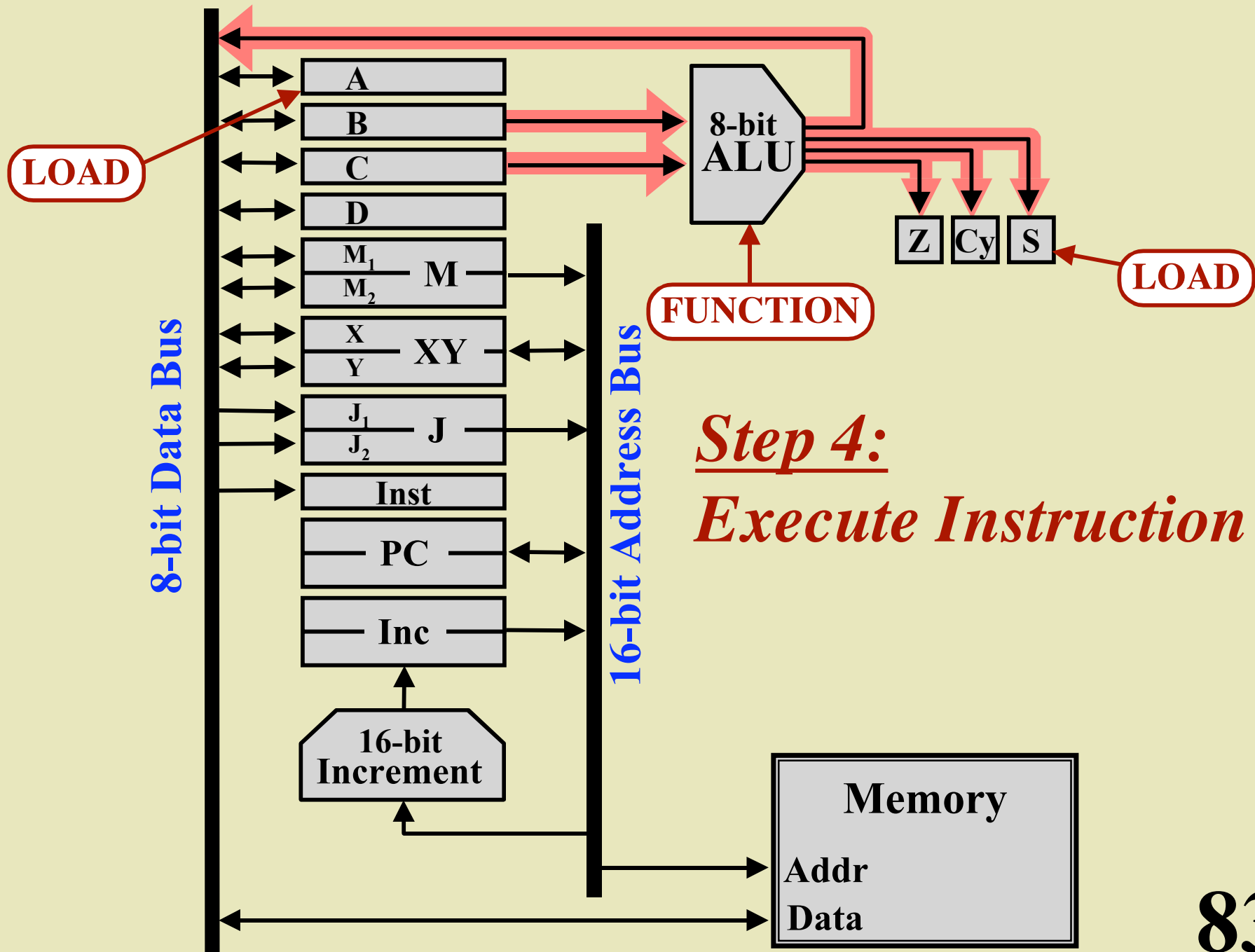


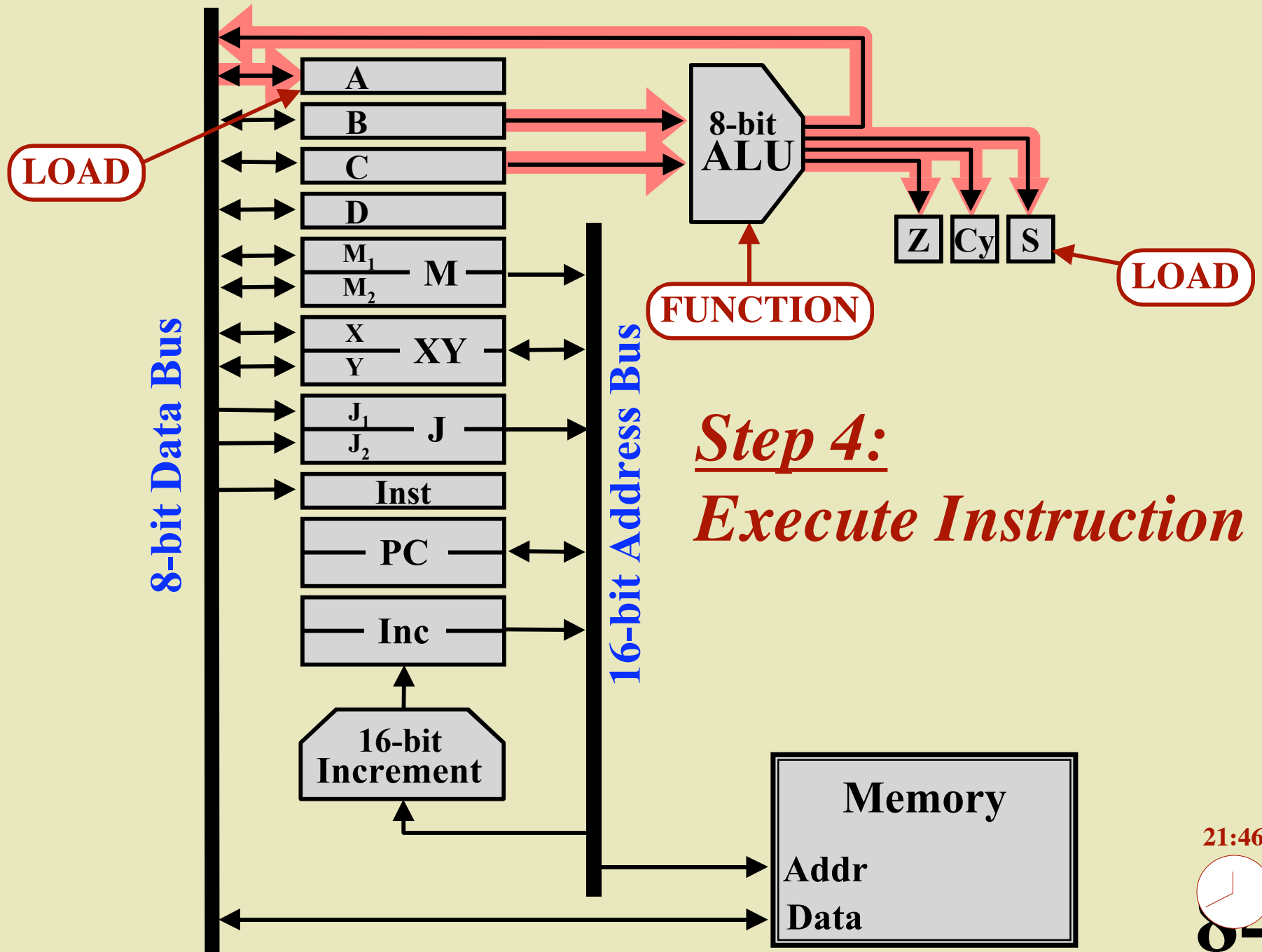


# Clock

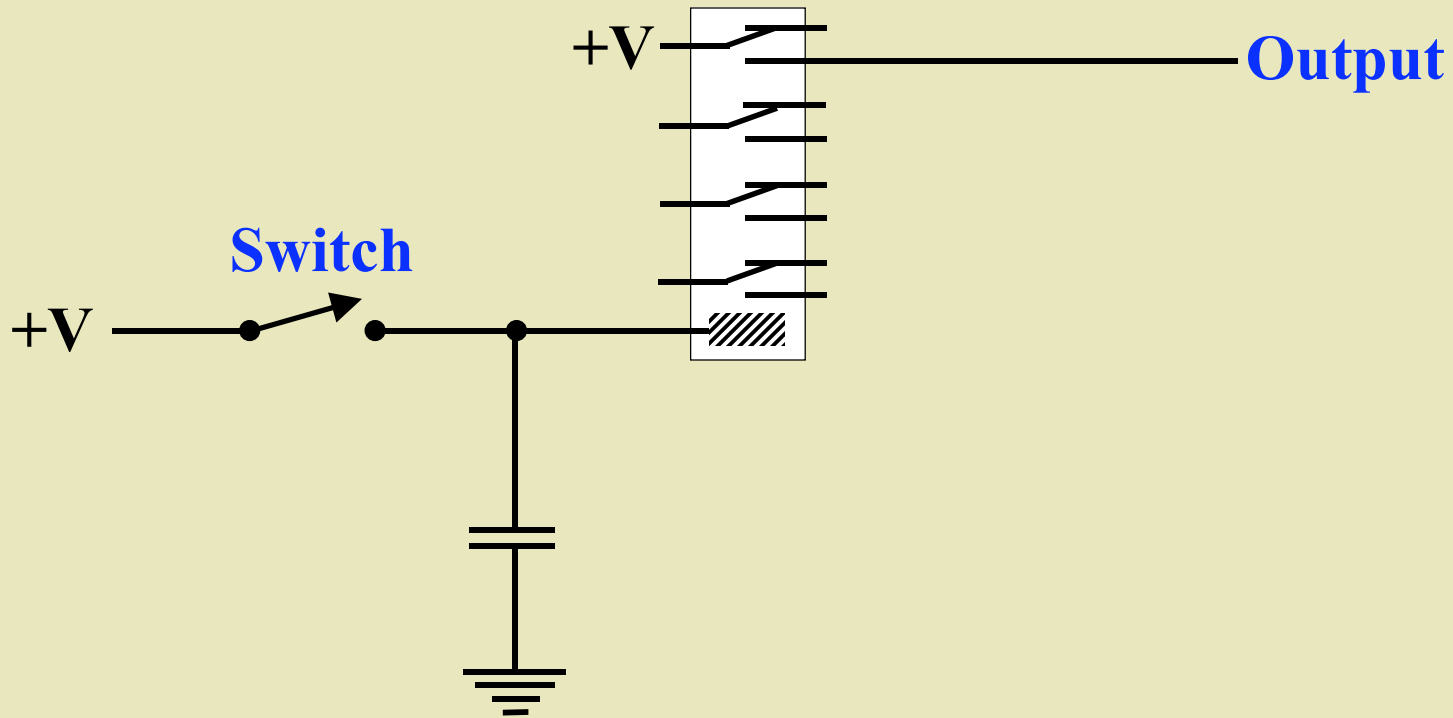


# Clock

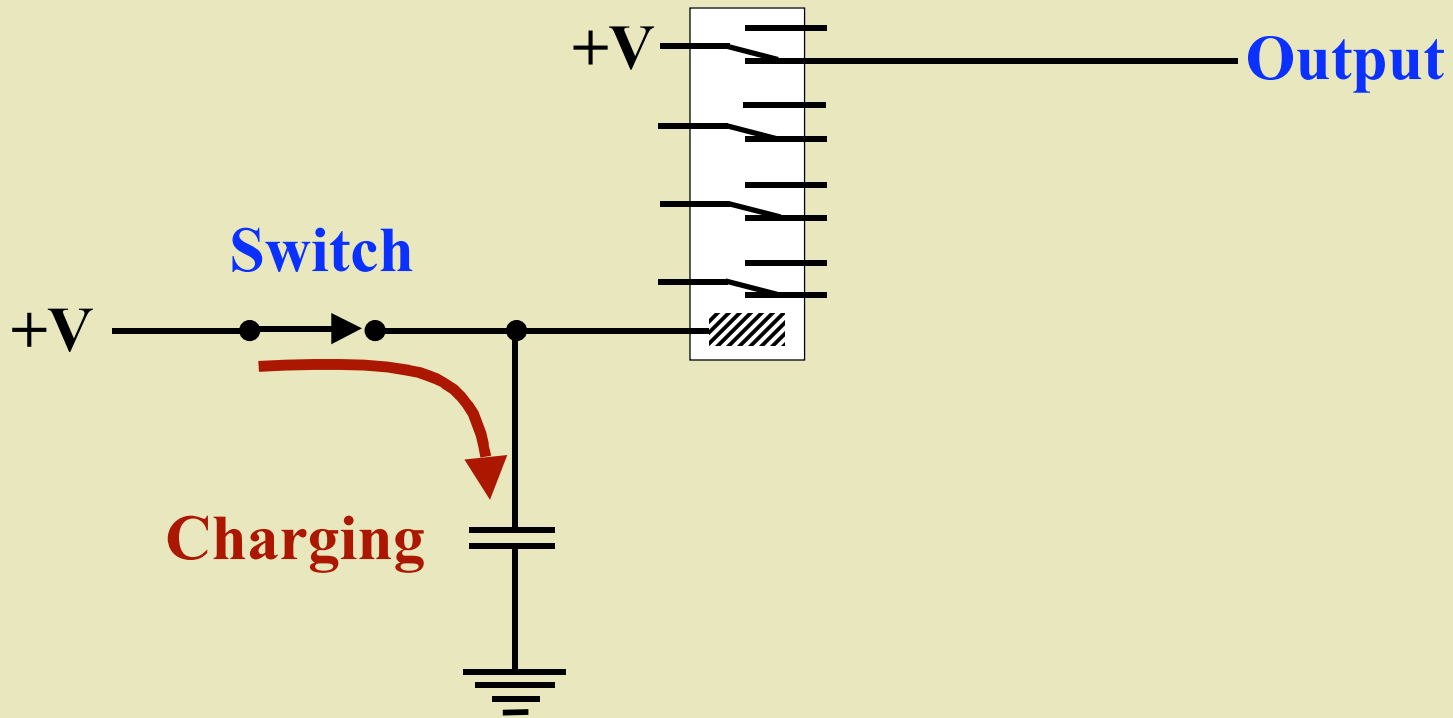

# Clock

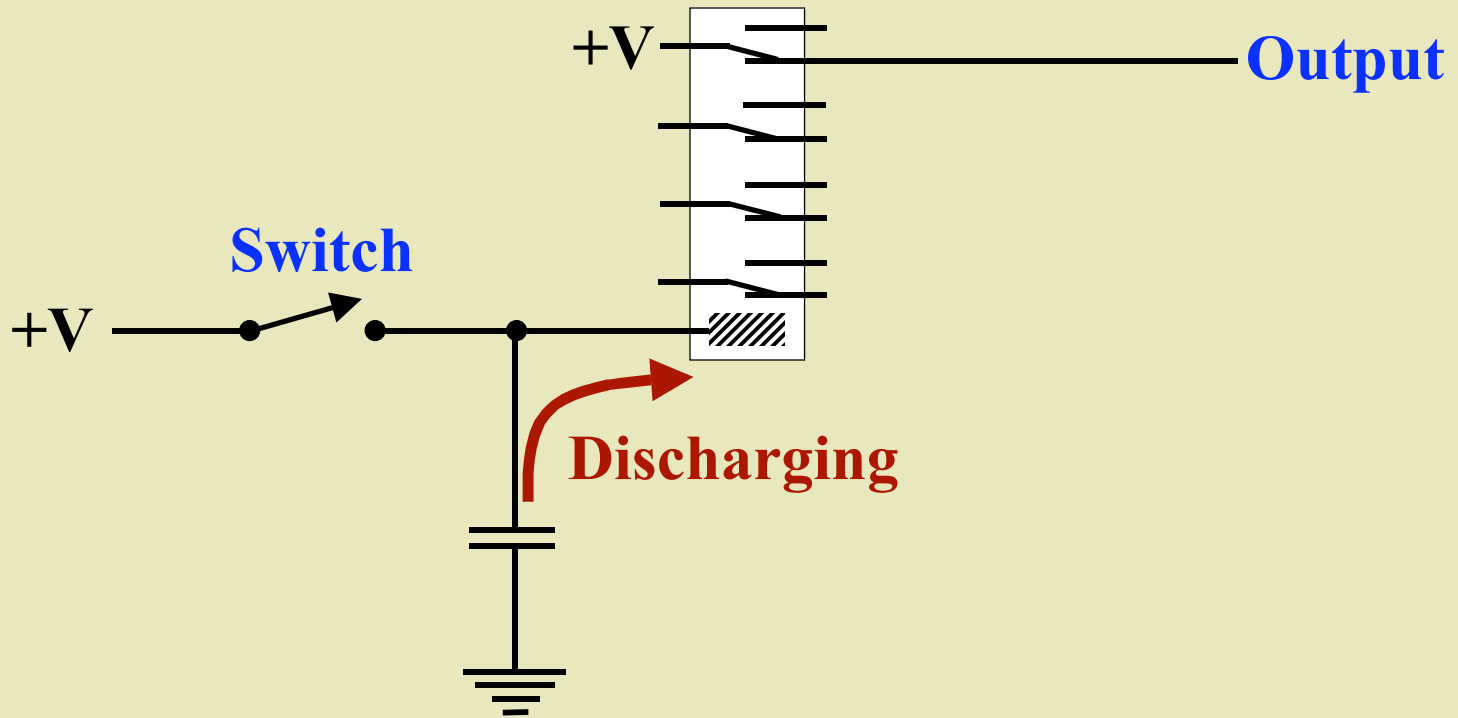


# Clock

 





# Clock

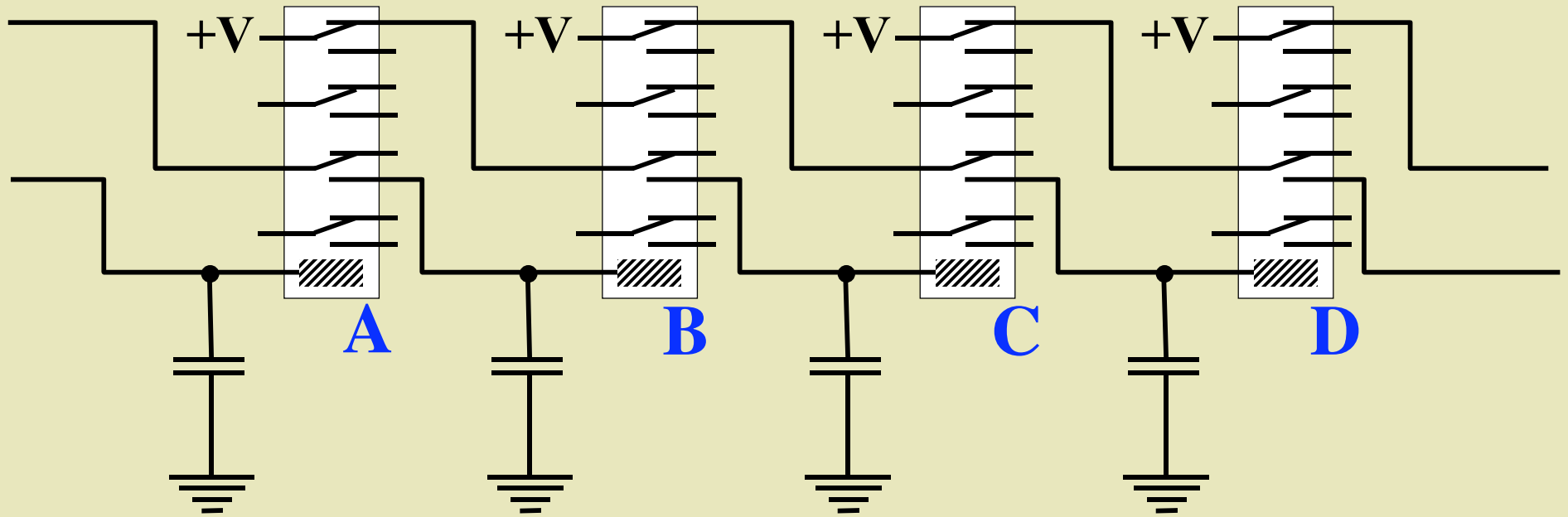


# Clock

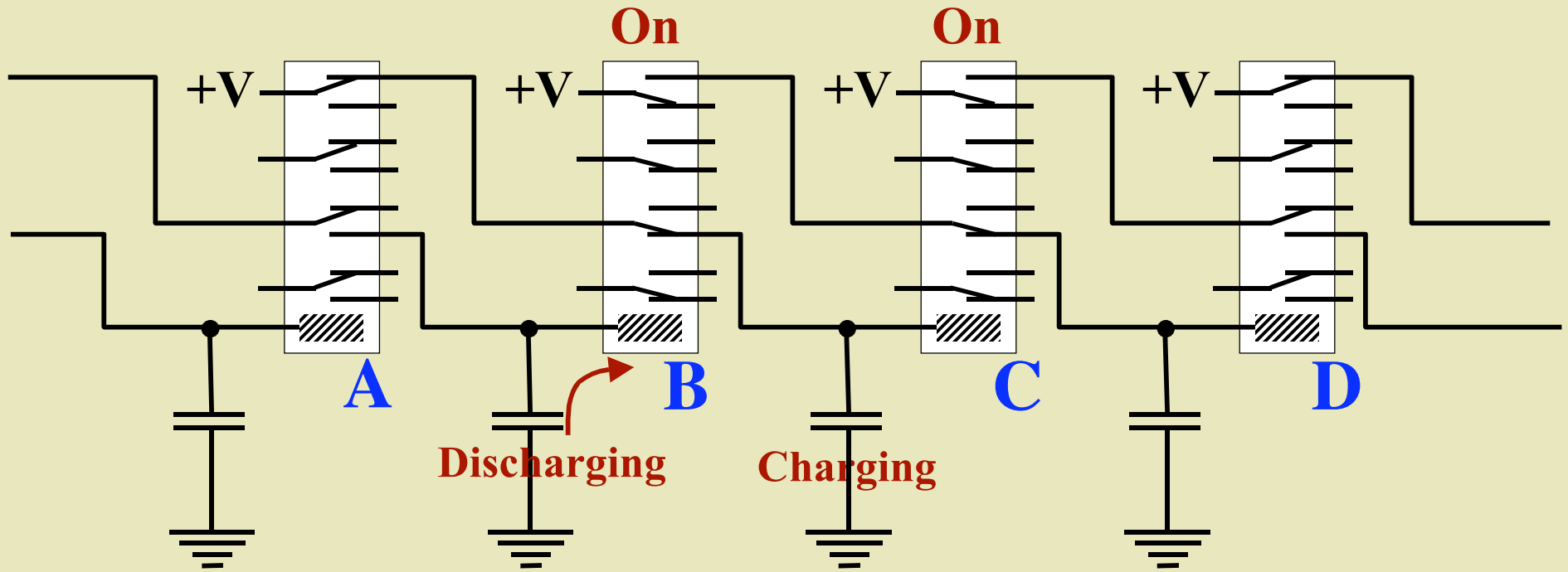


# Clock

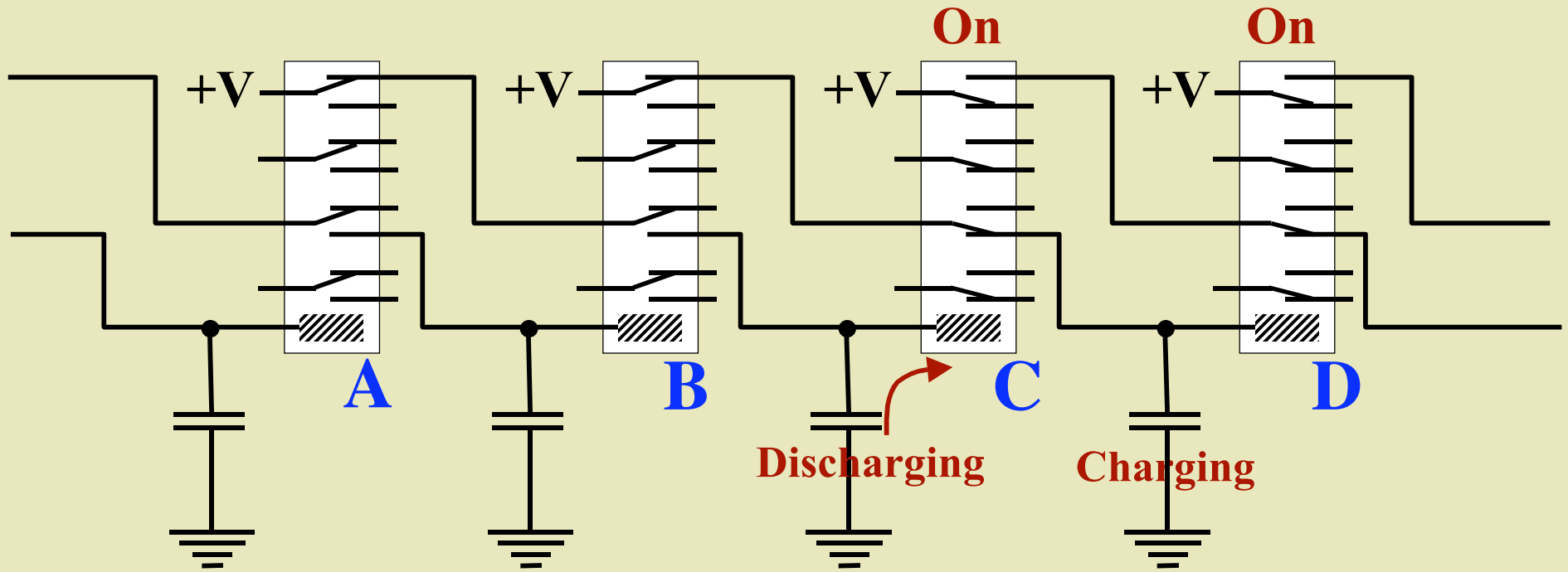

# Clock

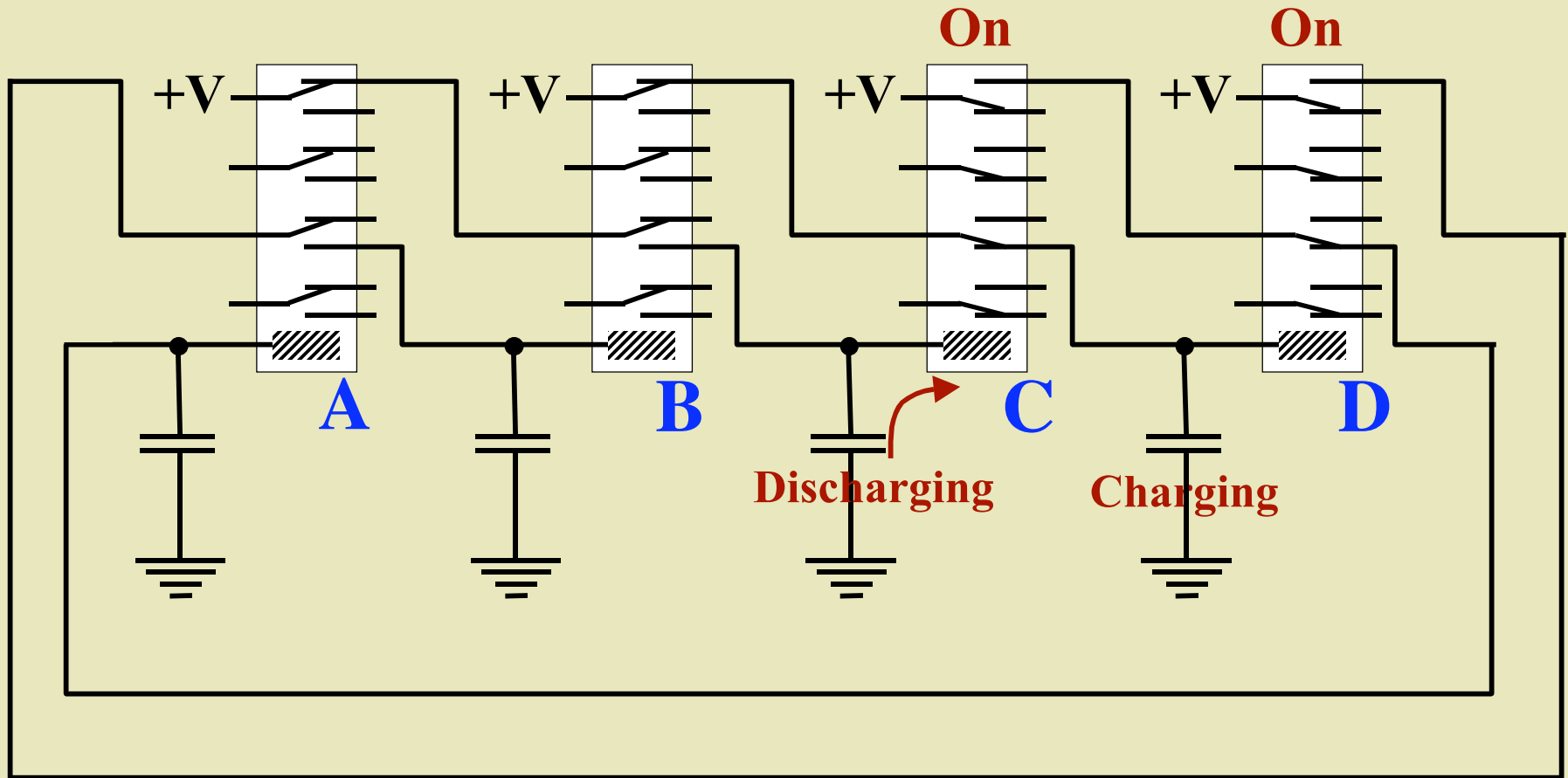


# Clock

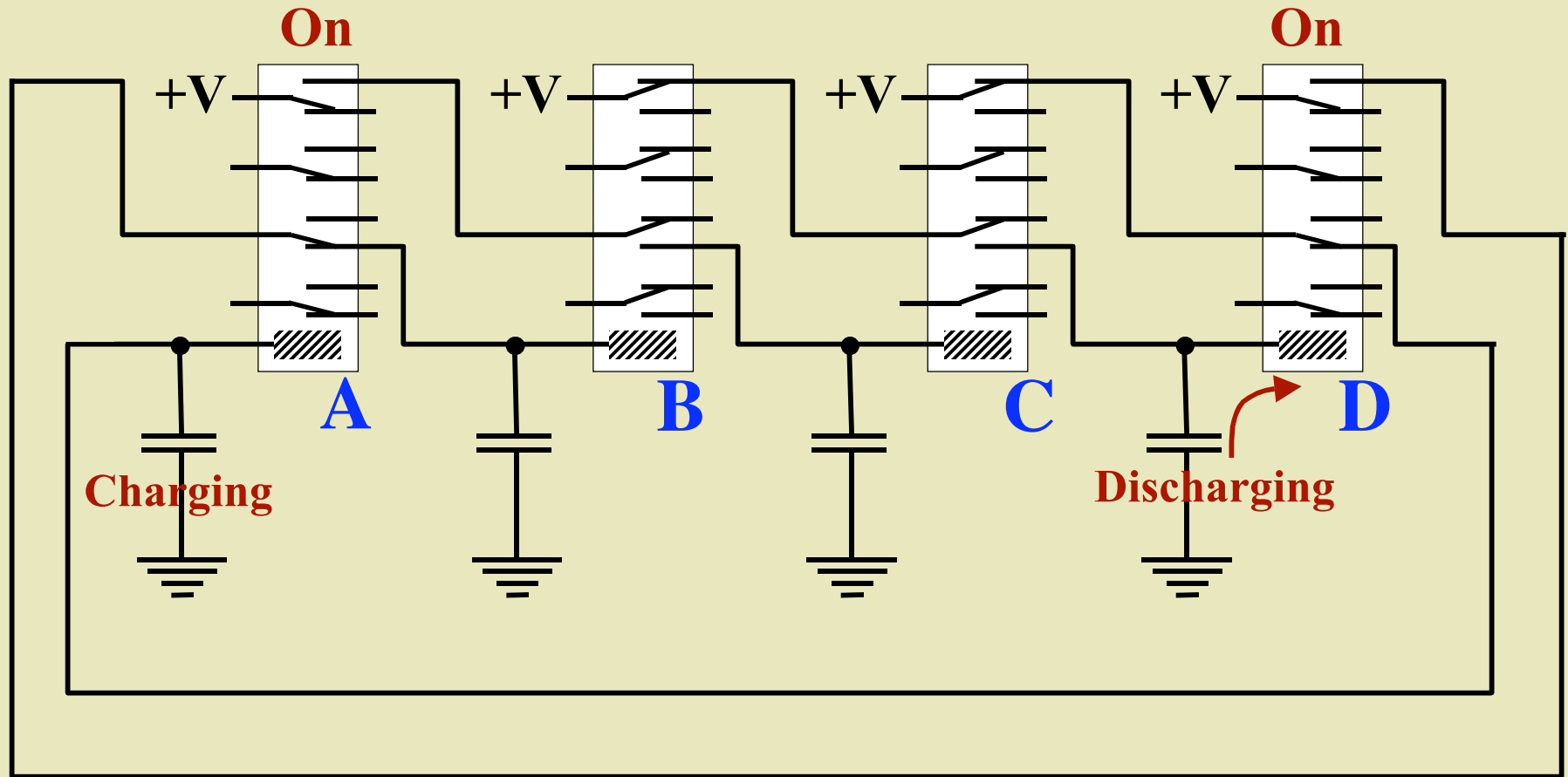




# Clock Timing Diagram

 


# Clock Timing Diagram

 




# Clock Timing Diagram

 


**Clock = (A and B) or (C and D)**


# Finite State Machine

 


# Finite State Machine

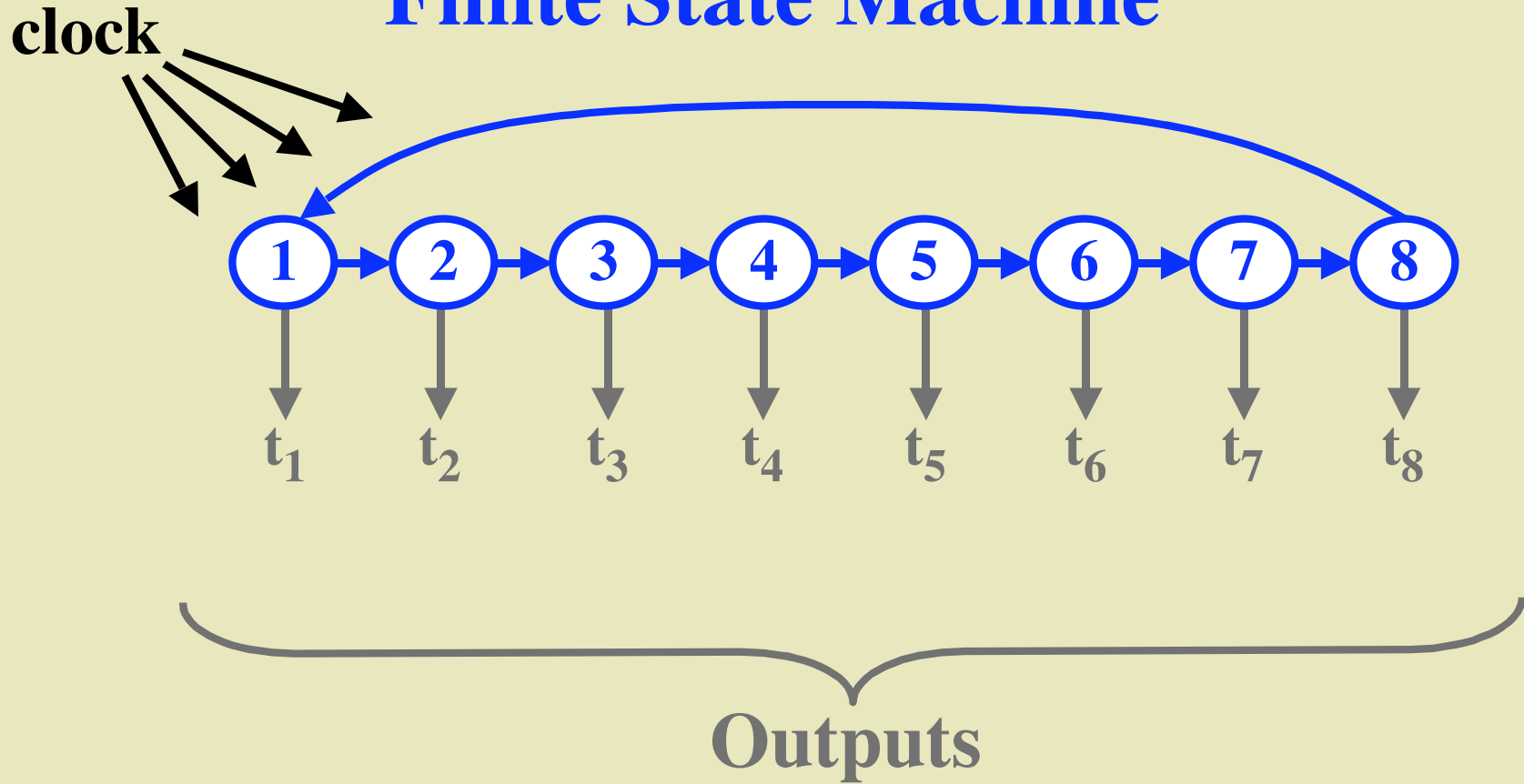


# Finite State Machine

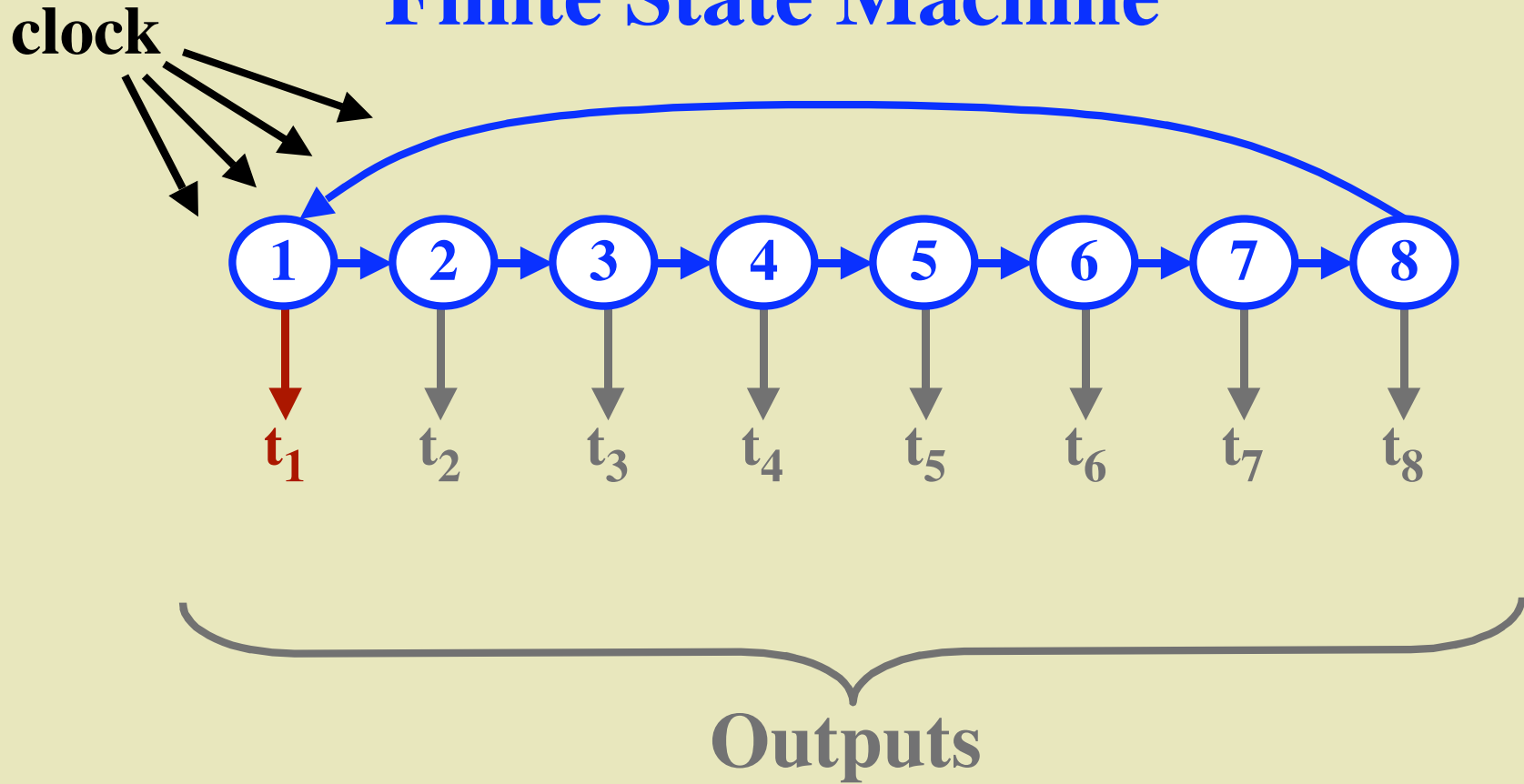


# Finite State Machine

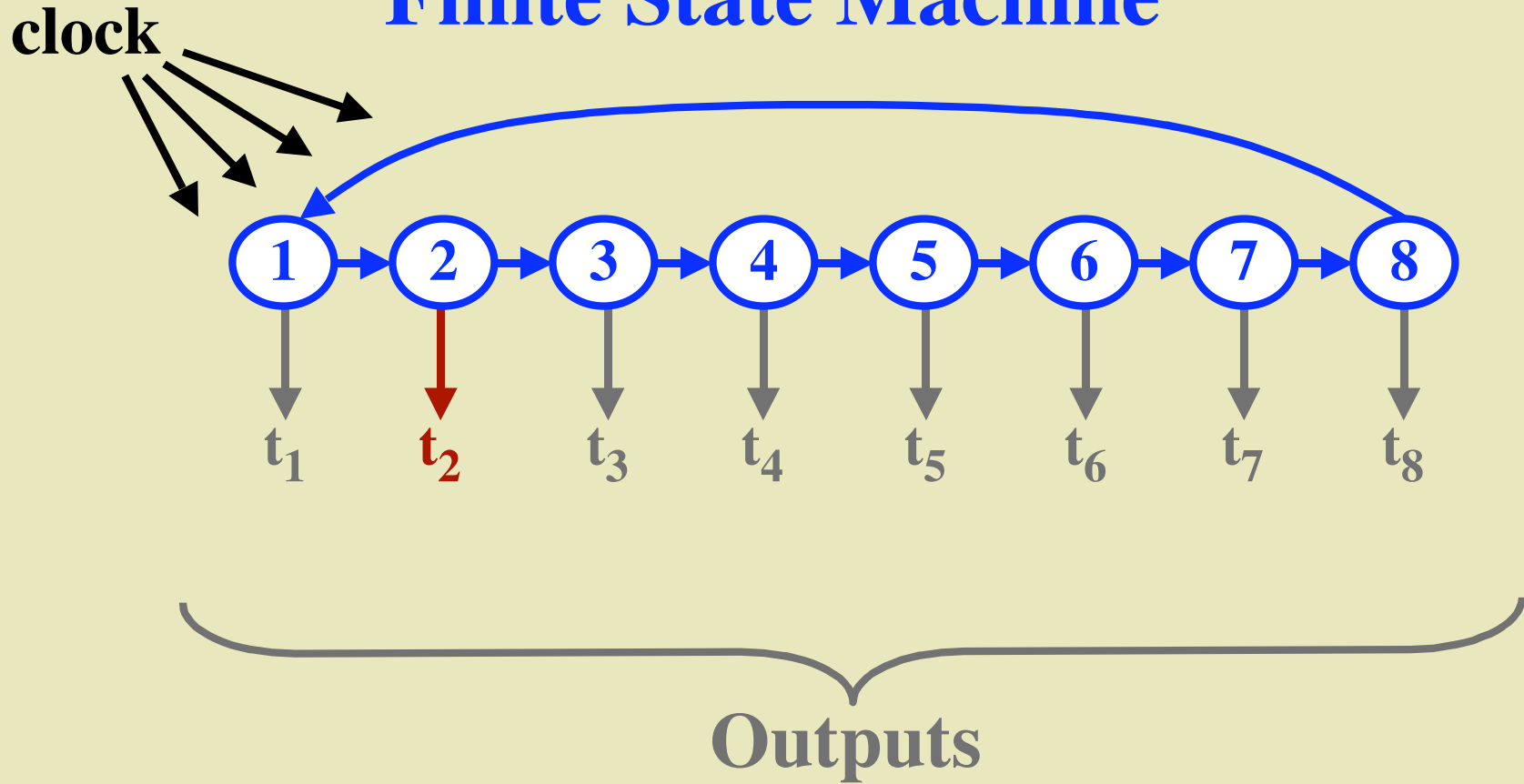


# Finite State Machine

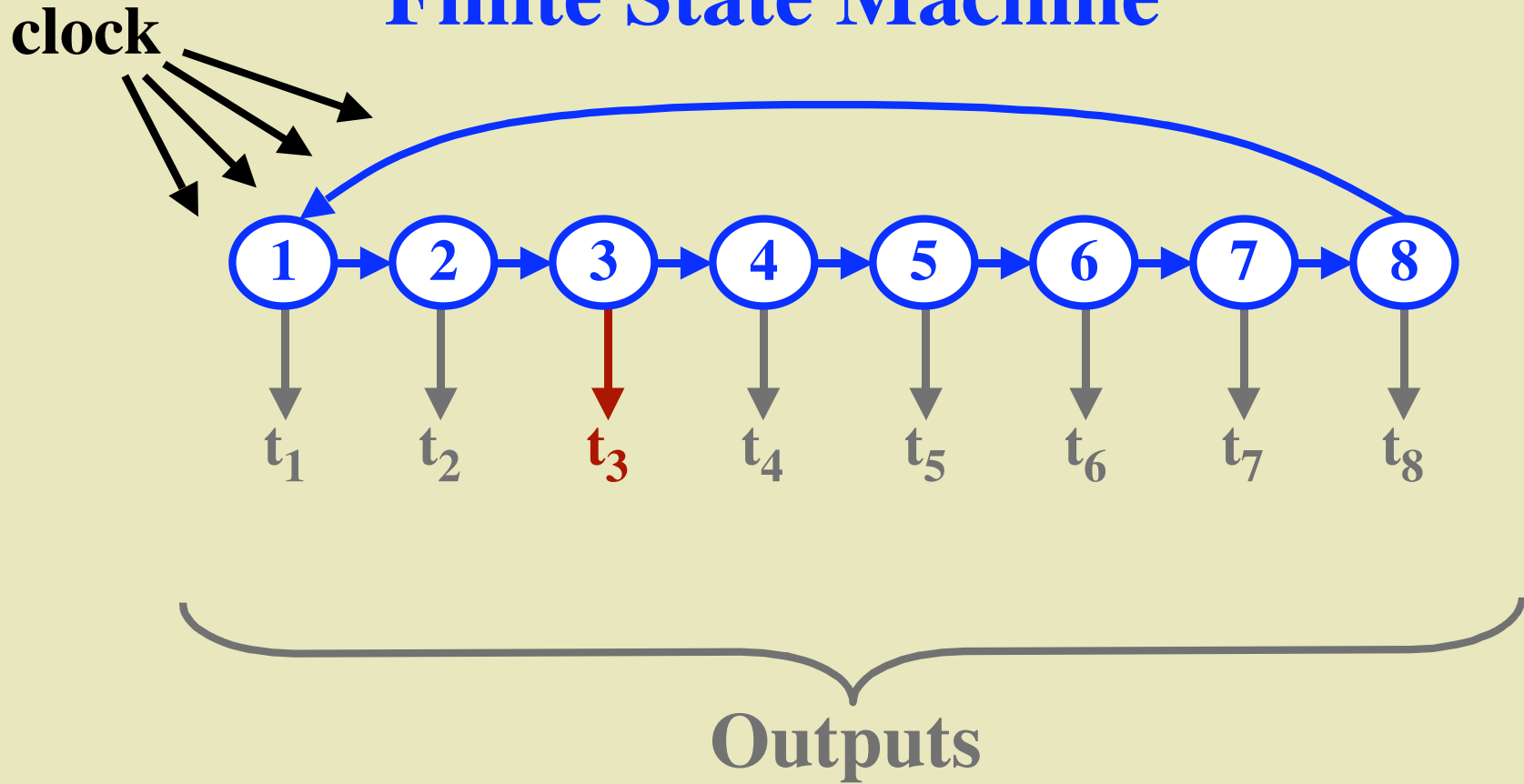

# Finite State Machine

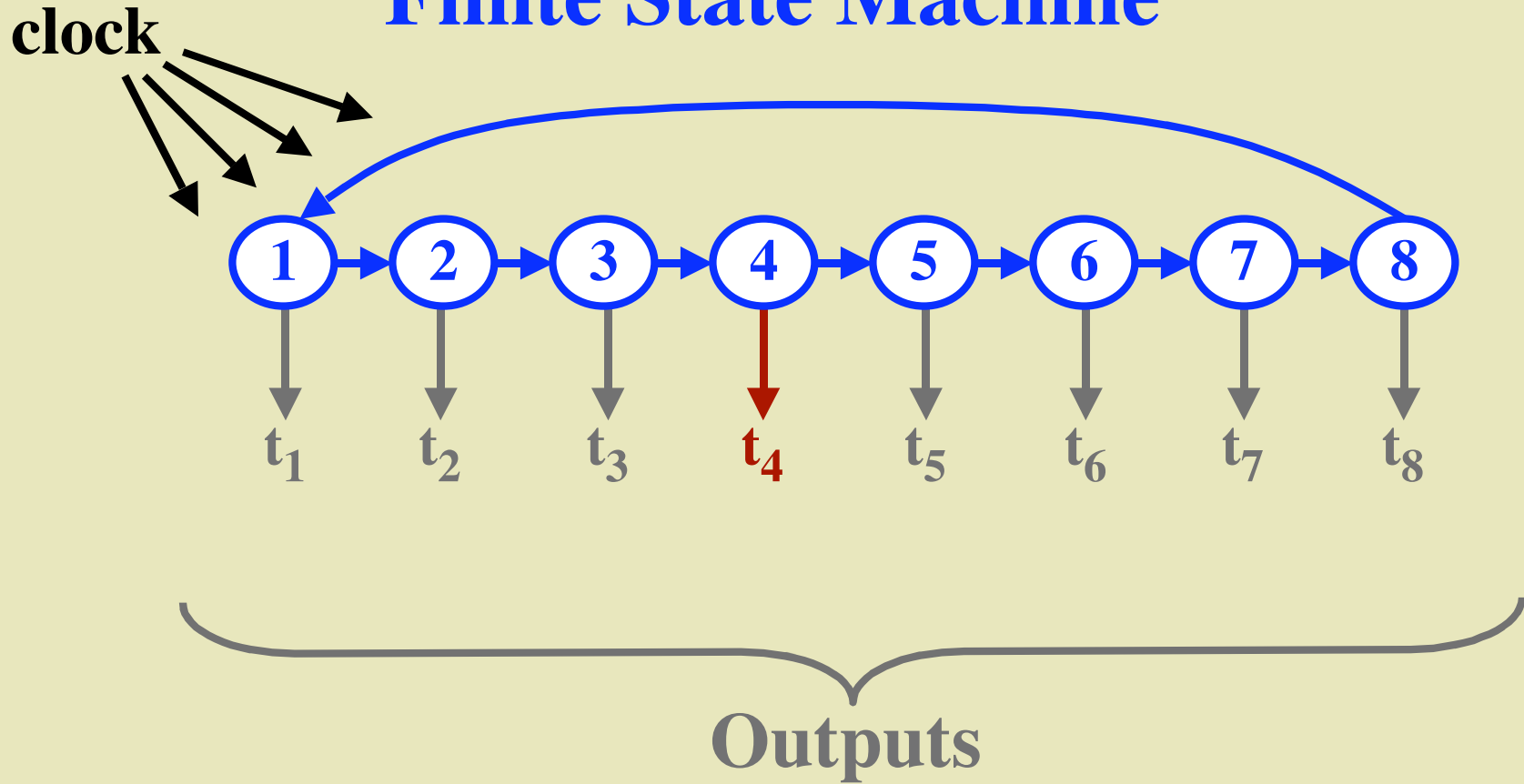


# Finite State Machine

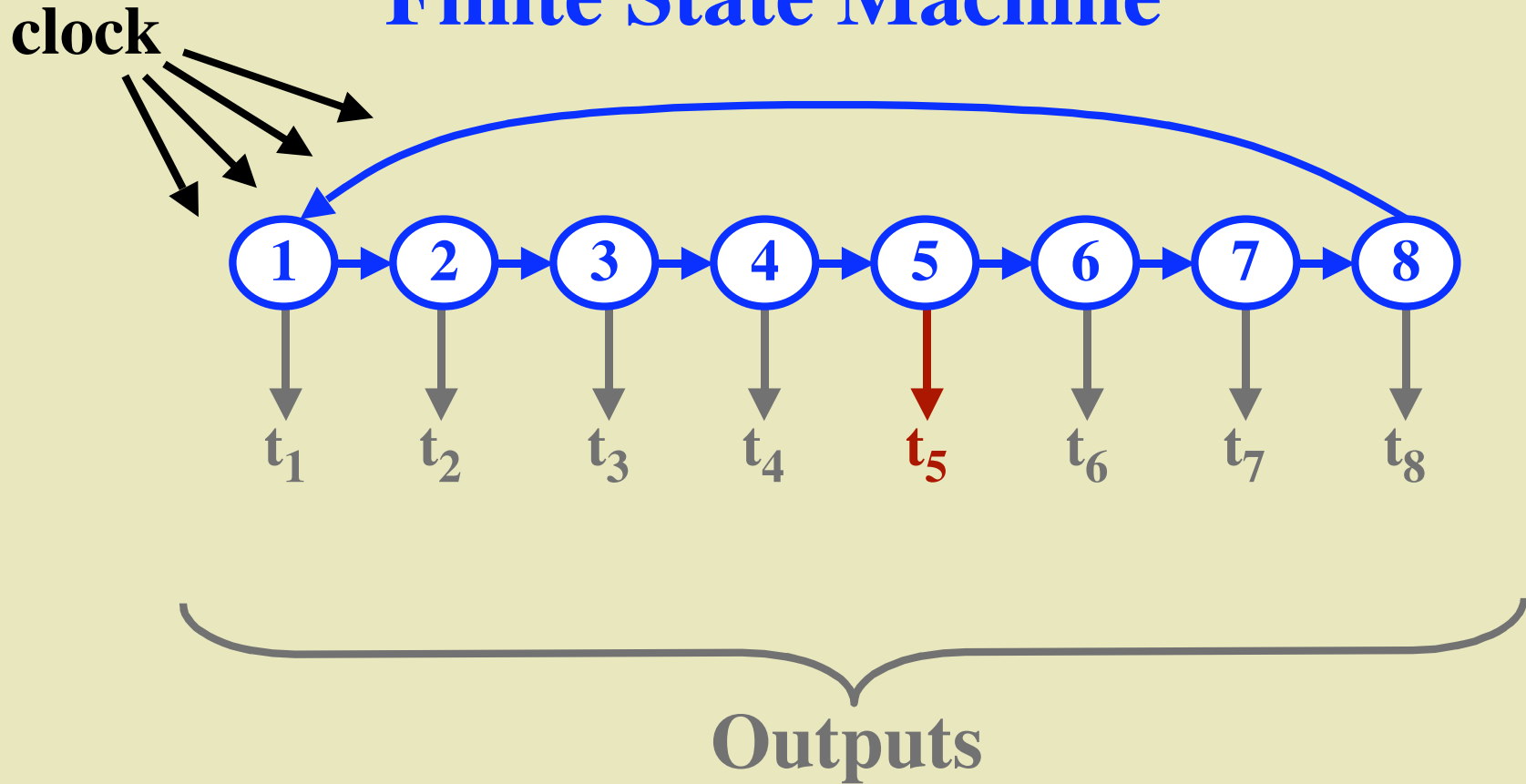





# Finite State Machine

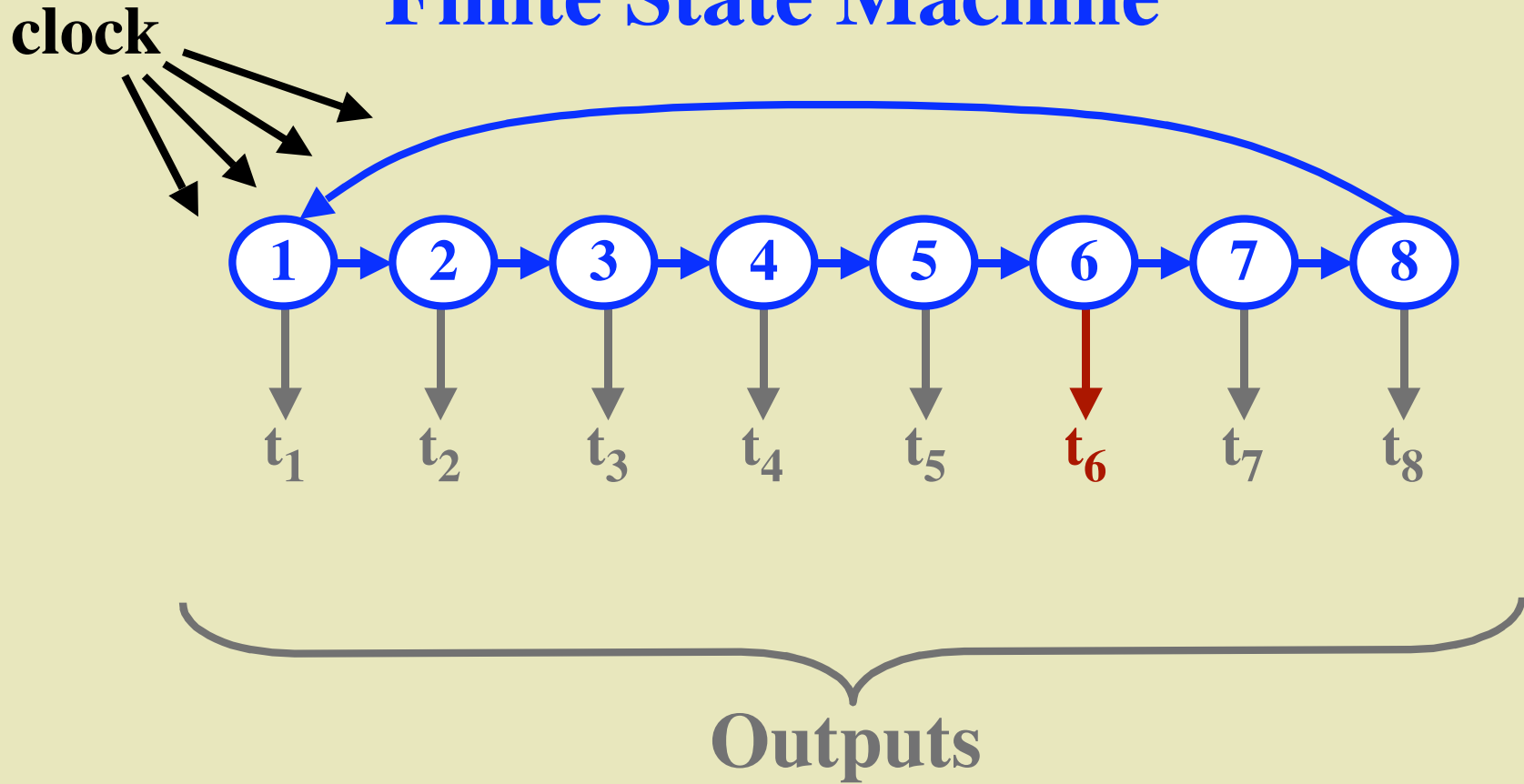


# Finite State Machine

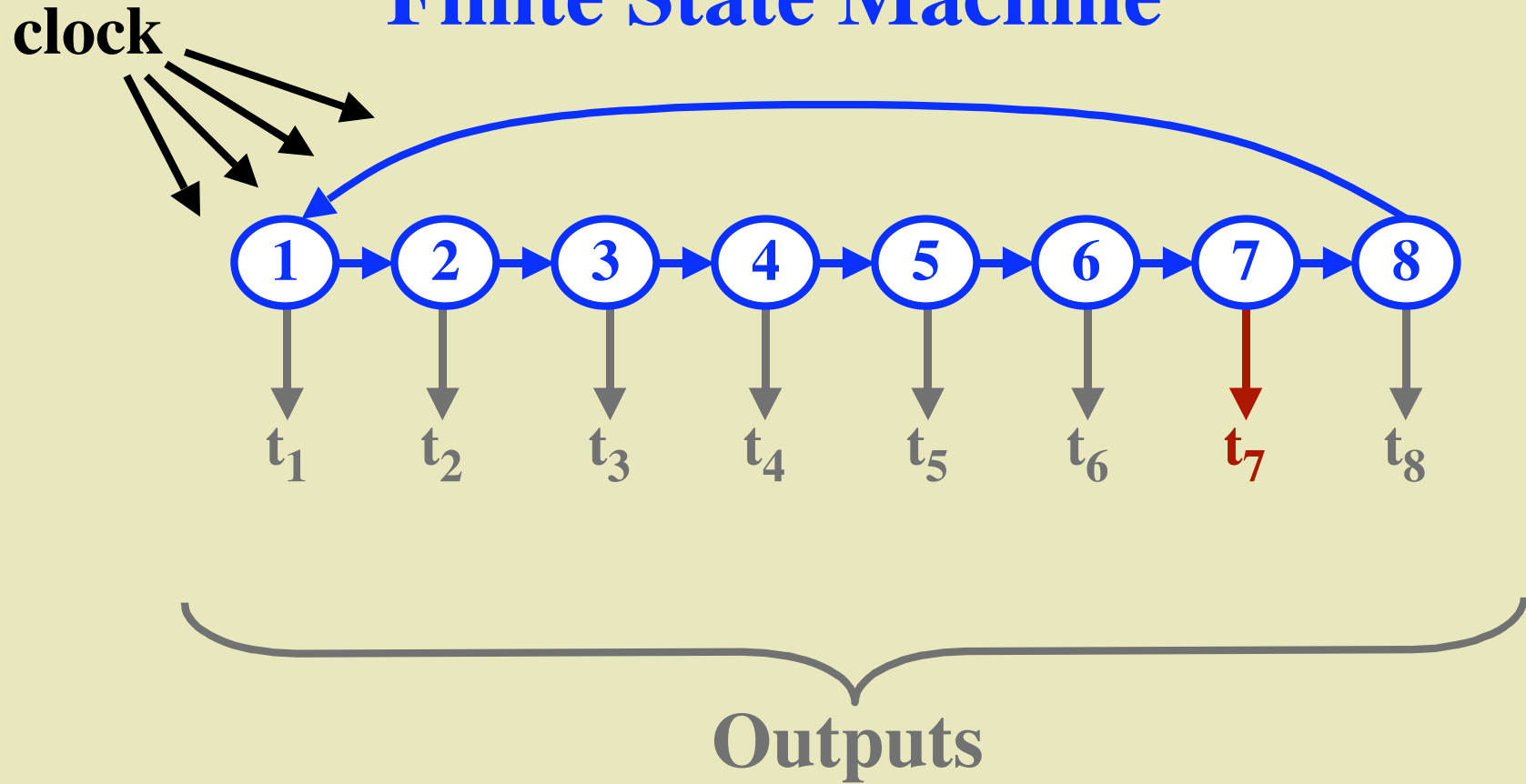


# Finite State Machine

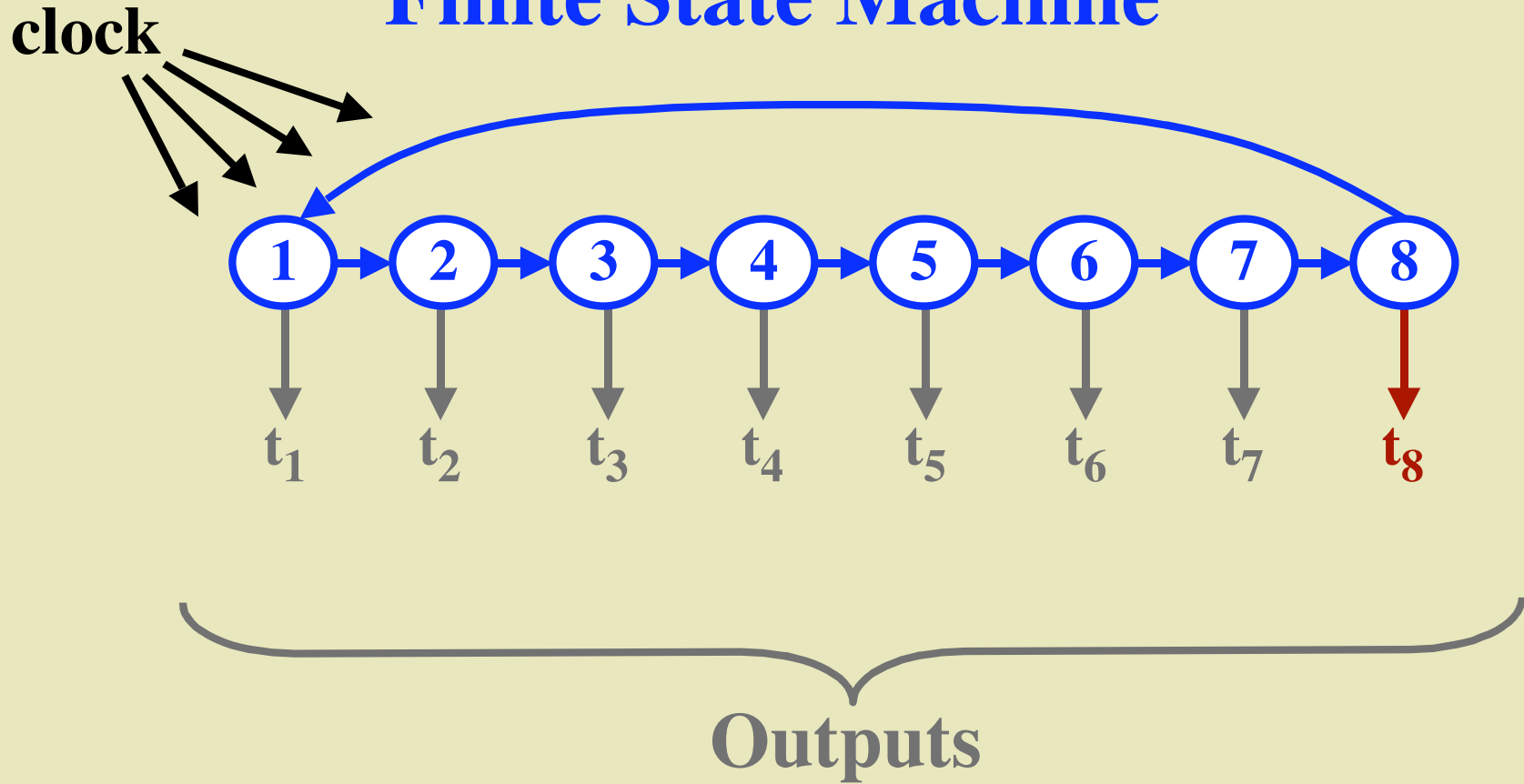


# Finite State Machine

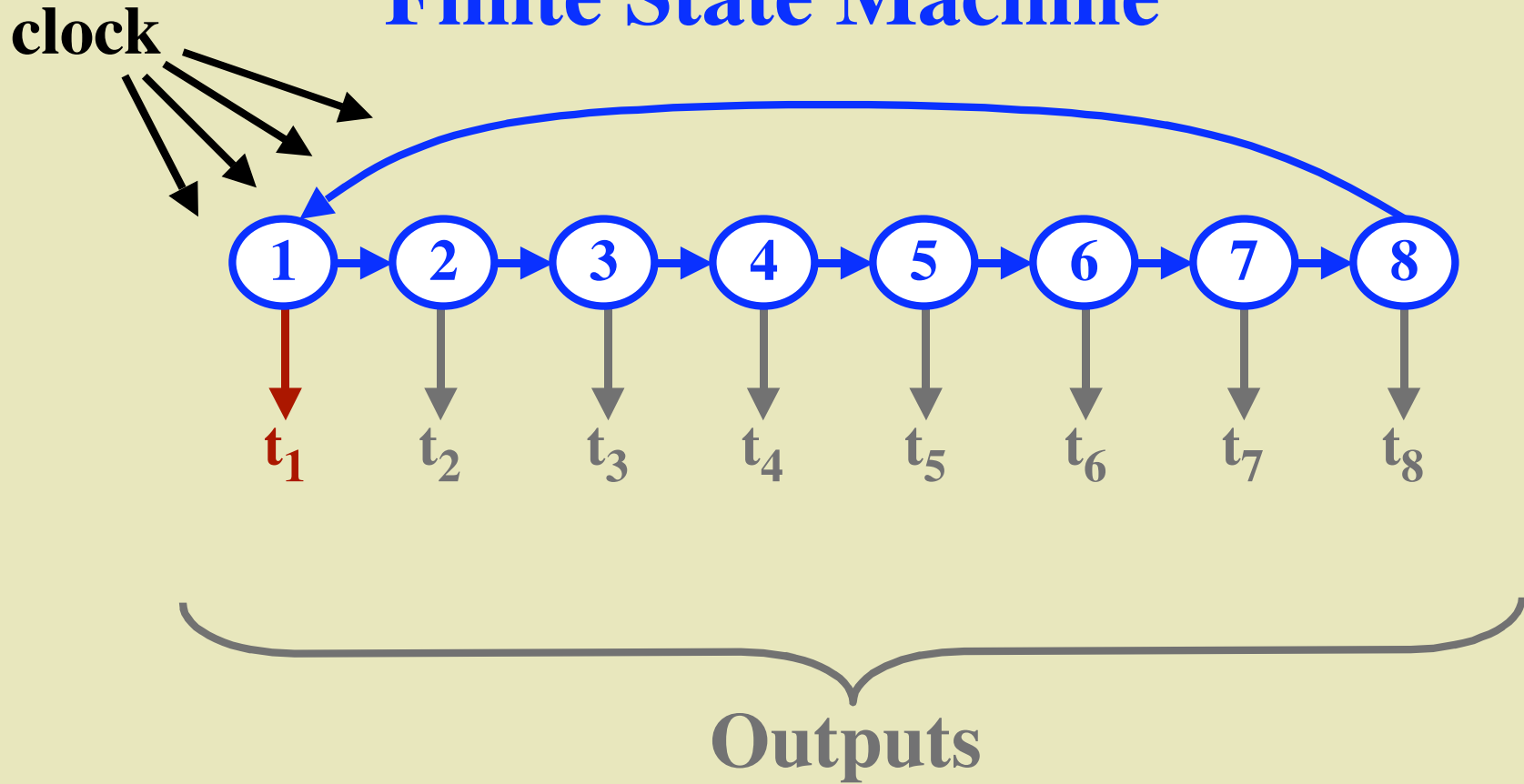


# Output from FSA

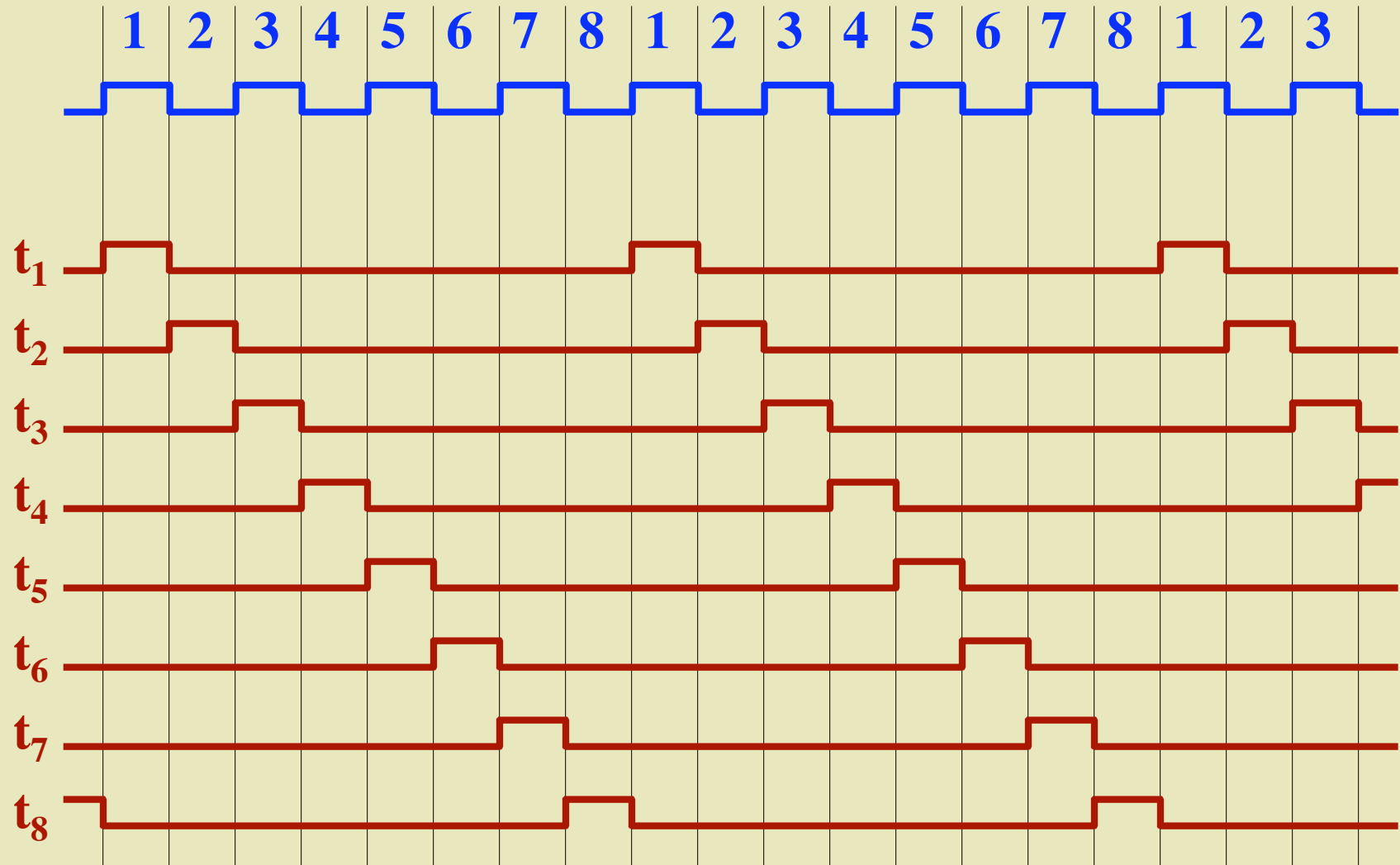


# Instruction Timing - ALU Instruction

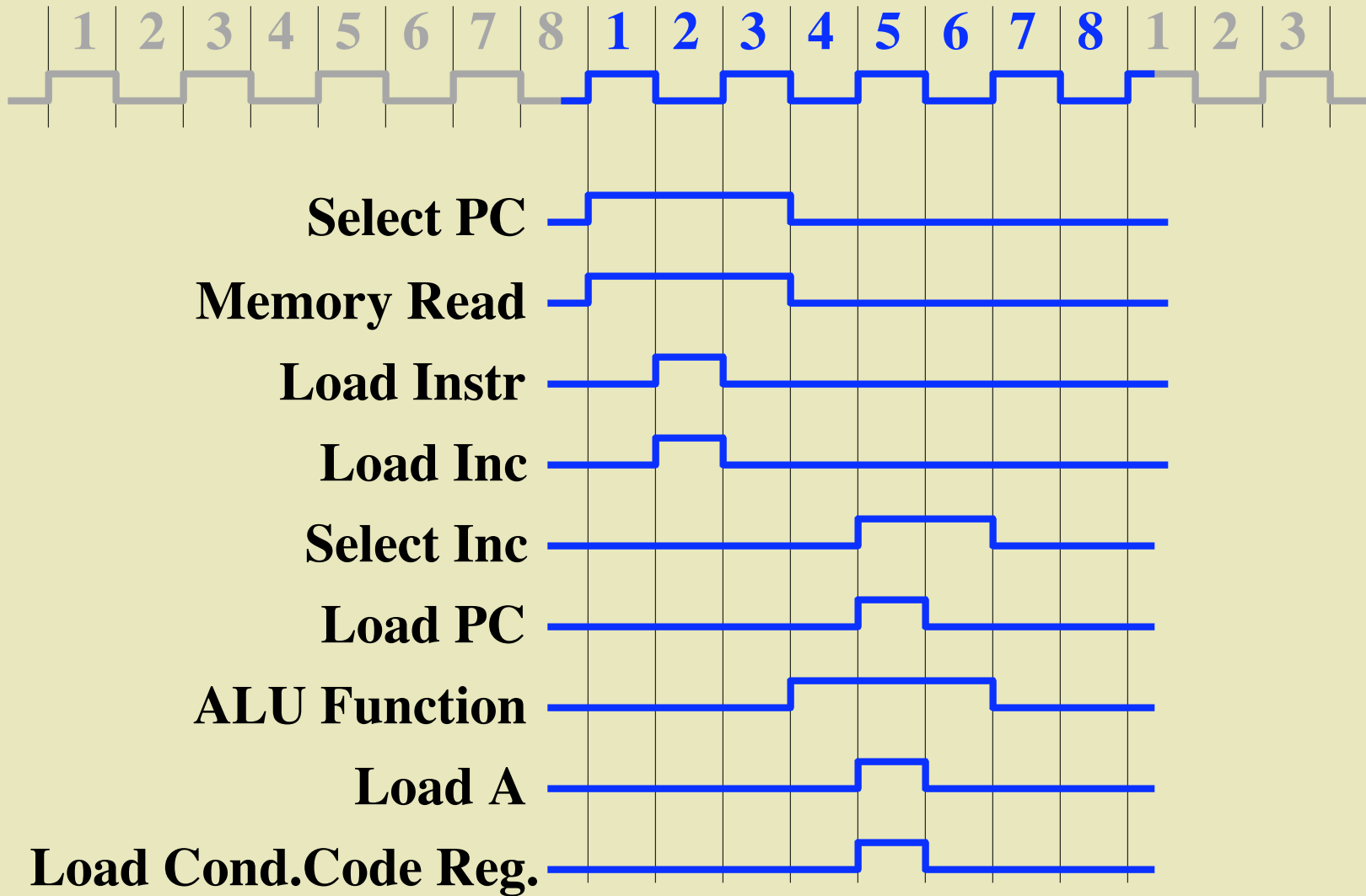

# Instruction Timing - ALU Instruction

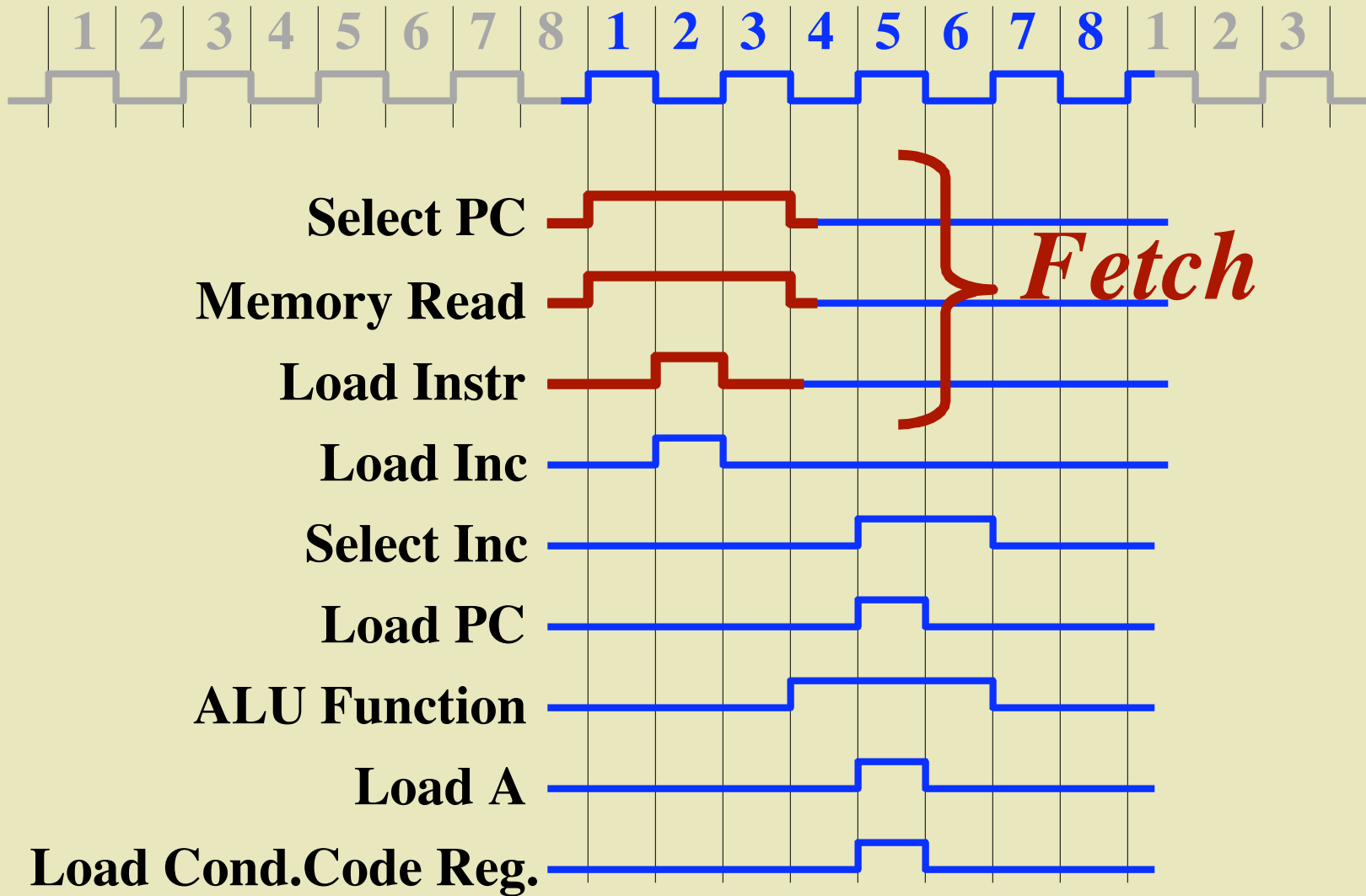


# Instruction Timing - ALU Instruction

 




# Instruction Timing - ALU Instruction


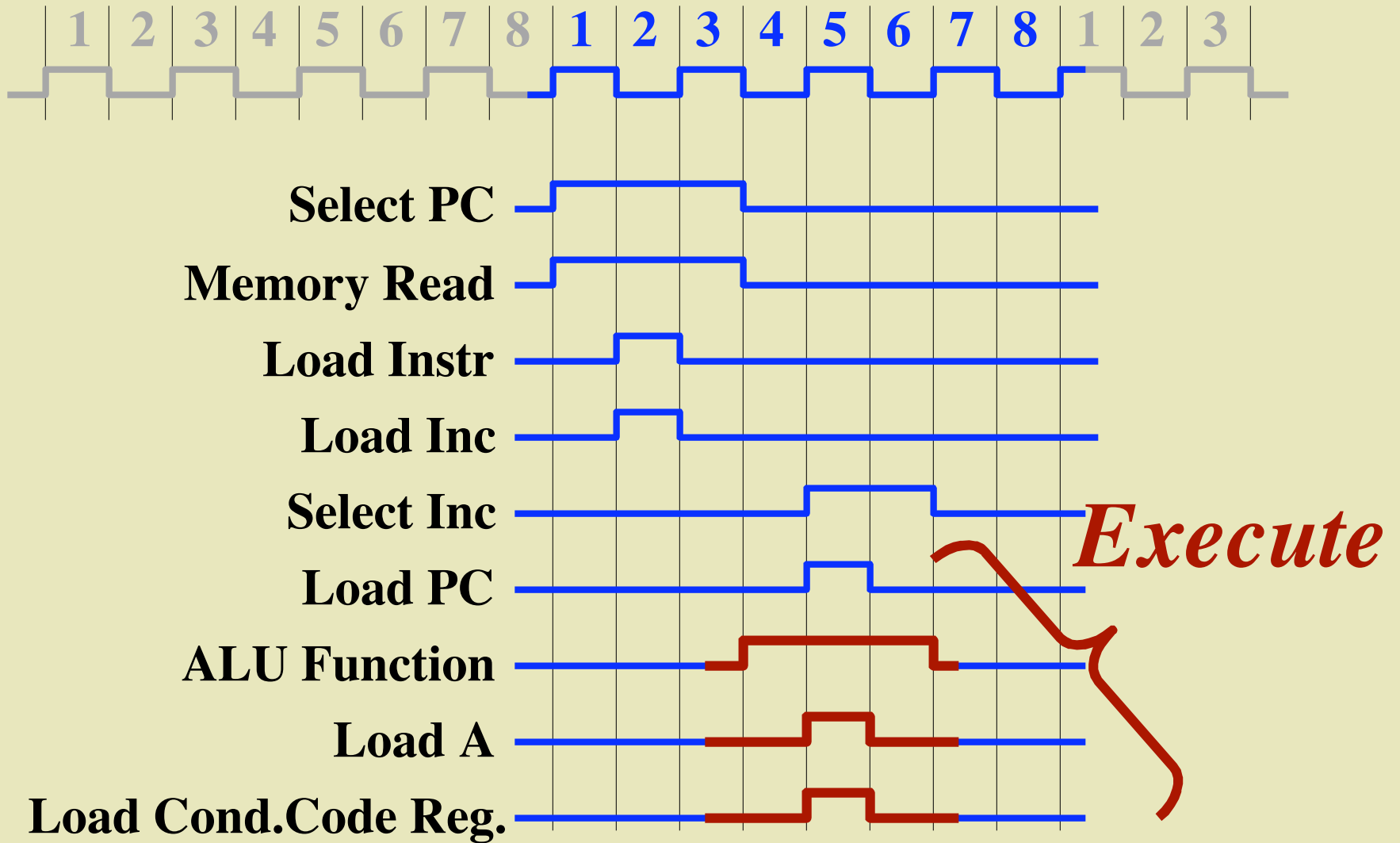


# Instruction Decoding

**Finite State Machine**

 


**Instruction Register**

  


**Control Signals**

*(Load, Select, Mem-Read, etc.)*


# Instruction Decoding

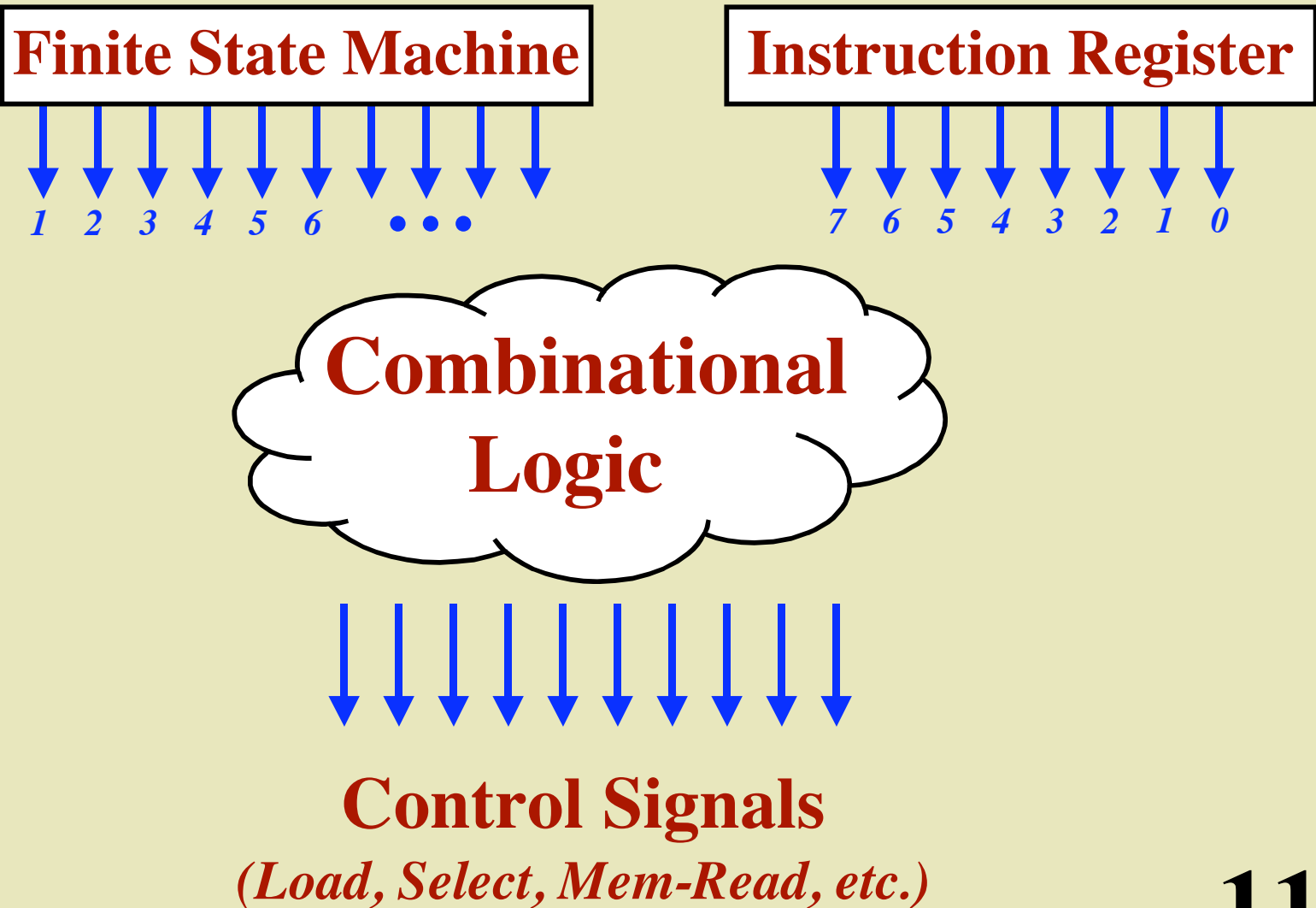


# Instruction Timing - 16-bit Move

 


# Finite State Machine

 

# Finite State Machine

 


# Instruction Decoding and Control

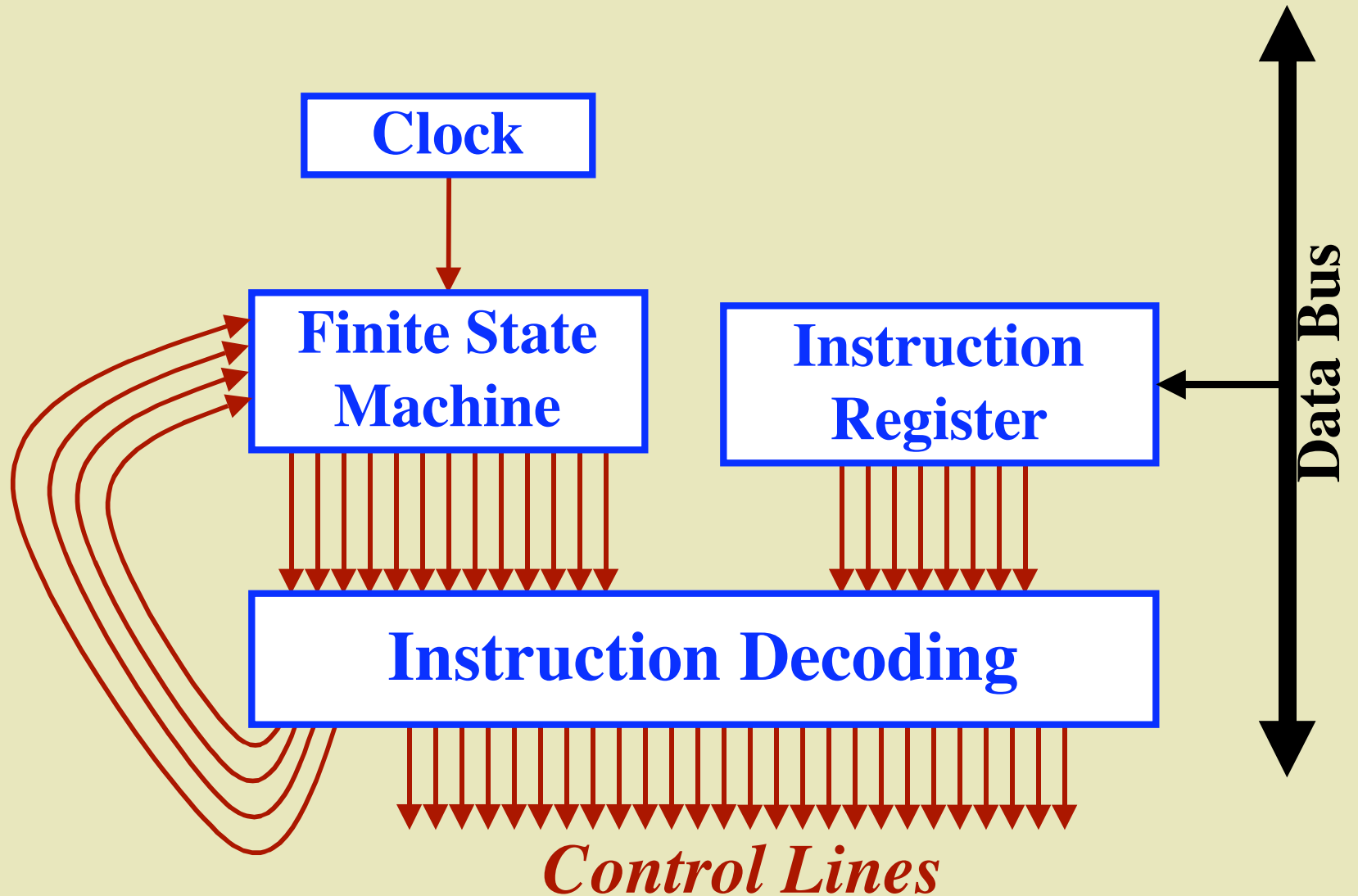


# The Instruction Set (1)

## Move

 


**ddd** = destination register  
**sss** = source register  
(A, B, C, D, M<sub>1</sub>, M<sub>2</sub>, X or Y)

## ALU

 


**r** = destination register (A or D)  
**fff** = function code  
(add, inc, and, or, xor, not, shl)

## Load Immediate

 

**r** = destination register (A or B)  
**dddd** = value (-16..15)

## 16-bit Increment

 

$XY \leftarrow XY + 1$



# The Instruction Set (2)

## Load

1	0	0	1	0	0	r	r
---	---	---	---	---	---	---	---

**rr** = destination register (A, B, C, D)  
**reg**  $\leftarrow$  [M]

## Store

1	0	0	1	1	0	r	r
---	---	---	---	---	---	---	---

**rr** = source register (A, B, C, D)  
[M]  $\leftarrow$  reg

## Load 16-bit Immediate

1	1	0	0	0	0	0	0
---	---	---	---	---	---	---	---

v	v	v	v	v	v	v	v
---	---	---	---	---	---	---	---

v	v	v	v	v	v	v	v
---	---	---	---	---	---	---	---


Load the immediate value into M (i.e., M<sub>1</sub> and M<sub>2</sub>)

## Halt

1	0	1	0	1	1	1	0
---	---	---	---	---	---	---	---

# The Instruction Set (3)


## Goto

 

Branch to the given address

---


## Call

 


Branch to the given address  
Save return location in XY register

---

## Return / Branch Indirect

 

## 16-Bit Move

 

**d** = destination register (PC or XY)  
**ss** = source register (M, XY or J)

# The Instruction Set (4)

## Branch If Negative

1 1 1 1 0 0 0 0

a a a a a a a a

a a a a a a a a

Branch to the given address if  $S = 1$

---

## Branch If Carry

1 1 1 0 1 0 0 0

a a a a a a a a

a a a a a a a a

Branch to the given address if  $Cy = 1$

---

## Branch If Zero

1 1 1 0 0 1 0 0

a a a a a a a a

a a a a a a a a

Branch to the given address if  $Z = 1$

---

## Branch If Not Zero

1 1 1 0 0 0 1 0

a a a a a a a a

a a a a a a a a

Branch to the given address if  $Z = 0$

# An Example Program

<u>address</u>	<u>instr</u>	<u>assembly</u>	<u>comment</u>
0000 0000	0011 1001	Y=B	Y ← B
0000 0001	0011 0110	X=0	X ← 0
0000 0010	1000 0101	A=¬B	If sign(Y)==1
0000 0011	1111 0000	BNEG Else	.
0000 0100	0000 0000	.	.
0000 0101	0000 0111	.	.
0000 0110	0011 0010	X=C	X ← C
		Else:	.
0000 0111	0101 1001	A=-7	D ← -7
0000 1000	0001 1000	D=A	.
		Loop:	Loop:
0000 1001	0000 1110	B=X	Shift X left (circular)
0000 1010	1000 0110	A=B<<1	.
0000 1011	0011 0000	X=A	.
0000 1100	0000 1111	B=Y	Shift Y left (circular)
0000 1101	1000 0110	A=B<<1	.
0000 1110	0011 1000	Y=A	.
0000 1111	0000 1111	B=Y	If sign(Y)==1
0001 0000	1000 0101	A=¬B	.
0001 0001	1111 0000	BNEG Else2	.
0001 0010	0000 0000	.	.
0001 0011	0001 0111	.	.
0001 0100	0000 1110	B=X	X ← X + C
0001 0101	1000 0000	A=B+C	.
0001 0110	0011 0000	X=A	.
		Else2:	.
0001 0111	0000 1011	B=D	D ← D + 1
0001 1000	1000 1001	D=B+1	.
0001 1001	1110 0010	BNZ Loop	If D != 0 goto Loop
0001 1010	0000 0000	.	.
0001 1011	0000 1001	.	.
0001 1100	1010 1110	HALT	HALT