
 


The Design of a Relay Computer


Harry Porter, Ph.D.
Portland State University

April 24, 2006

 





Double Throw Relay

 


Double Throw Relay

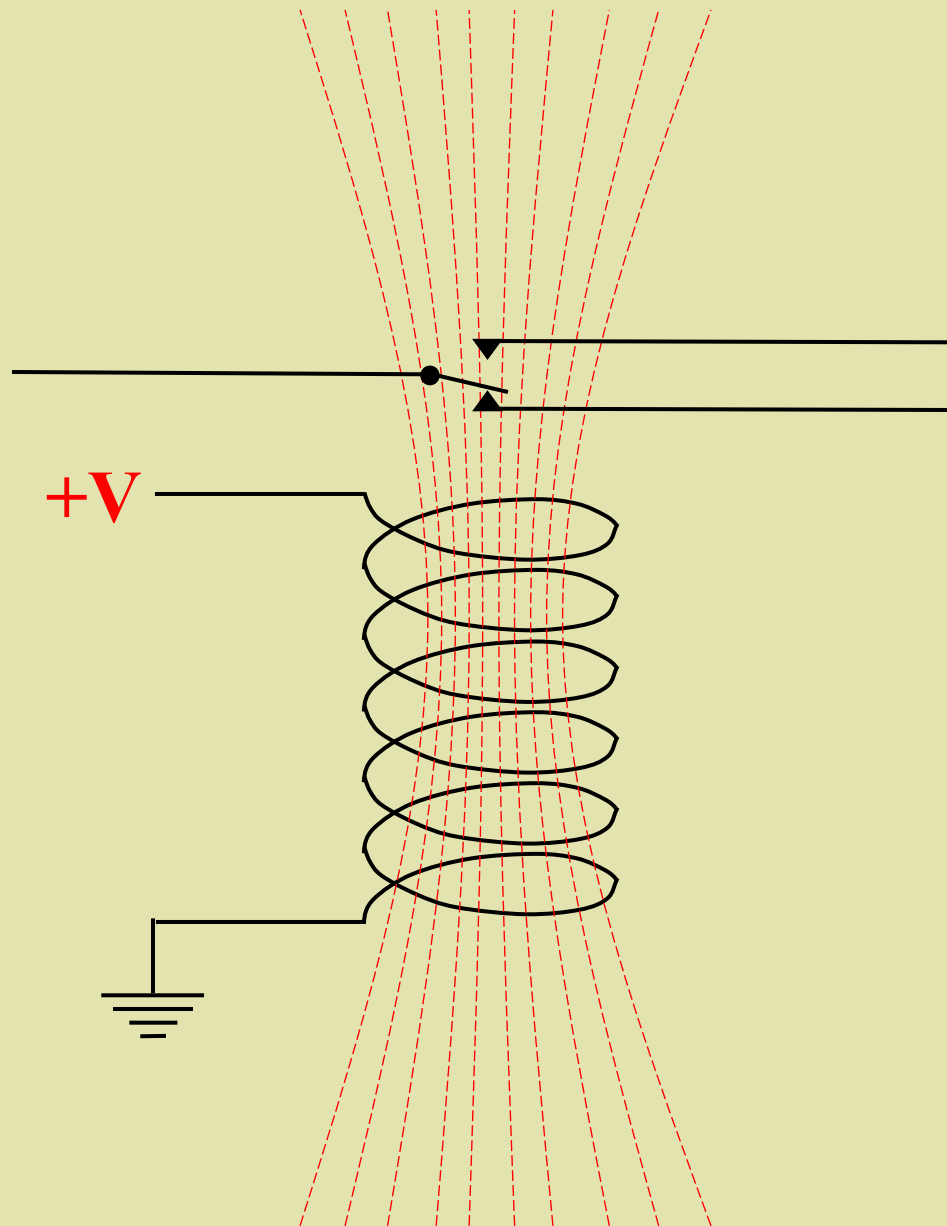


Four Pole, Double Throw Relay



 


Four Pole, Double Throw Relay



 


 

Schematic Diagrams

 
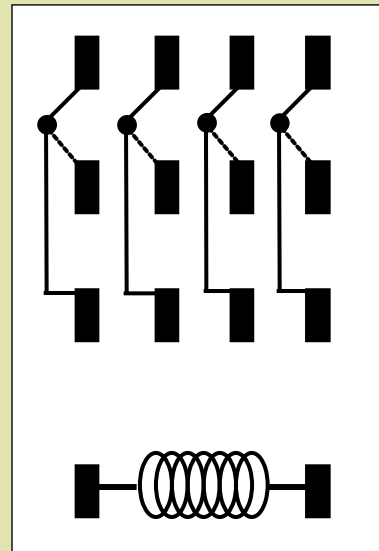
 


Schematic Diagrams

   


*Assume other terminal
is connected to ground*

Schematic Diagrams

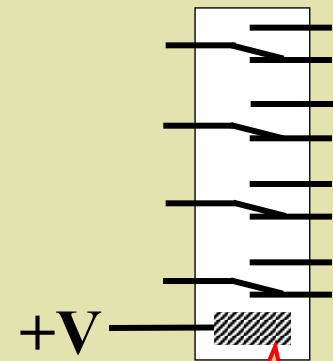  


*Assume other terminal
is connected to ground*


The “NOT” Circuit

 


<u>in</u>	<u>out</u>
0	1
1	0

 

The “NOT” Circuit

 


<u>in</u>	<u>out</u>
0	1
1	0

 


Convention:
“1” = +12V
“0” = not connected

The “NOT” Circuit

 


<u>in</u>	<u>out</u>
0	1
1	0

 


Convention:
“1” = +12V
“0” = not connected



The "OR" Circuit

 



<u>b</u>	<u>c</u>	<u>OUT</u>
0	0	0
0	1	1
1	0	1
1	1	1

 



An Optimization?

  

An Optimization?

 
 


An Optimization?

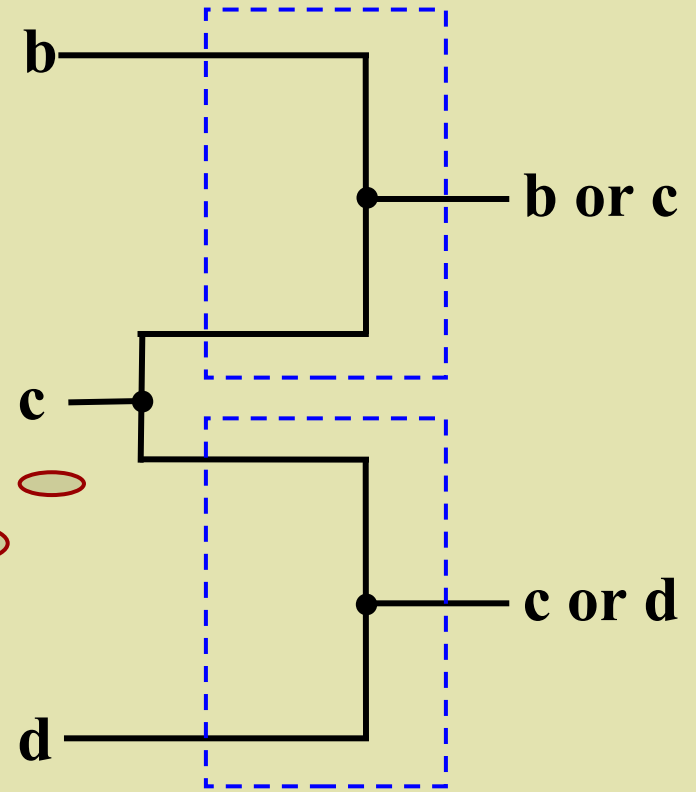 



Whoops!

An Optimization?

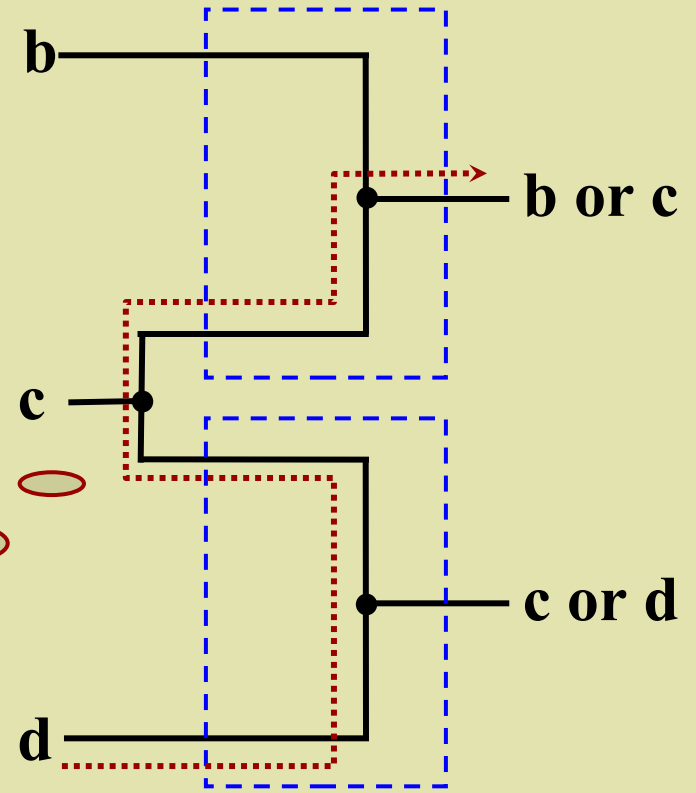 


Whoops!

An Optimization?

  


1-Bit Logic Circuit

b	c	NOT	AND	OR	XOR
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

 


1-Bit Logic Circuit

b	c	NOT	AND	OR	XOR
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

 


1-Bit Logic Circuit

b	c	NOT	AND	OR	XOR
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

 


1-Bit Logic Circuit

b	c	NOT	AND	OR	XOR
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

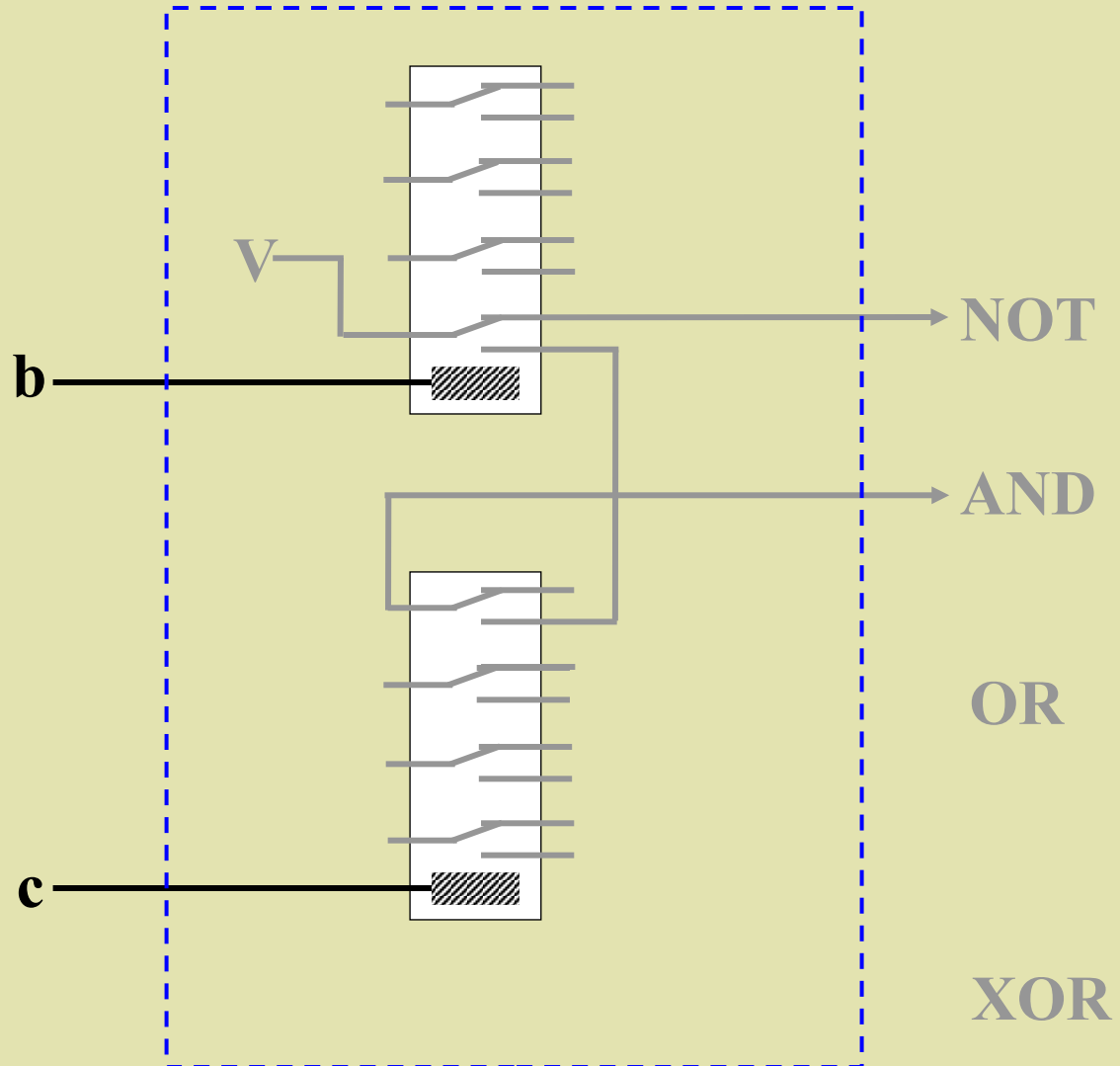


1-Bit Logic Circuit

b	c	NOT	AND	OR	XOR
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

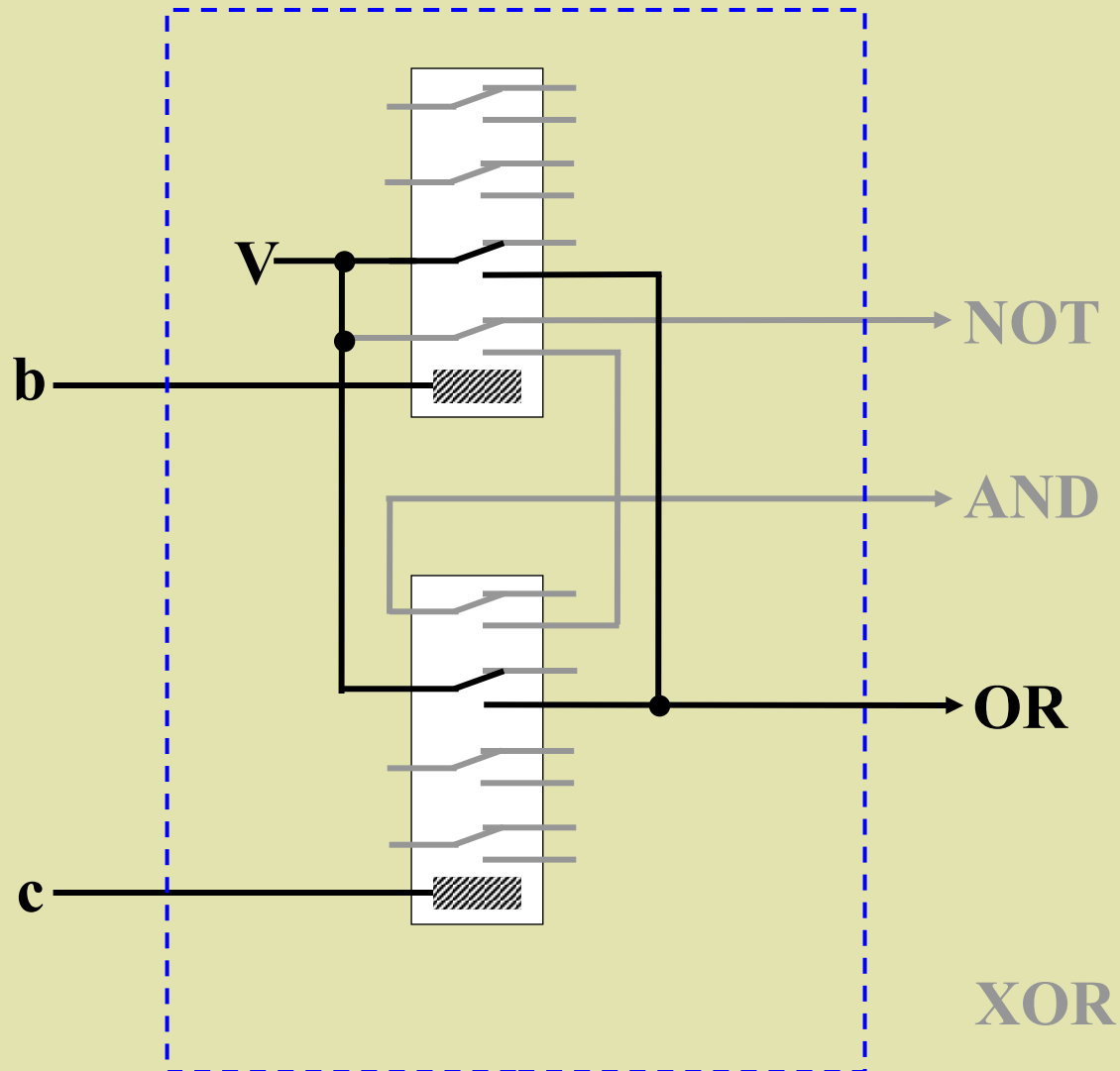


1-Bit Logic Circuit

b	c	NOT	AND	OR	XOR
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

 


1-Bit Logic Circuit

b	c	NOT	AND	OR	XOR
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

 


1-Bit Logic Circuit

b	c	NOT	AND	OR	XOR
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	1	1
1	1	0	1	1	0

 


*Eight 1-bit circuits can be combined
to build an...*

8-Bit Logic Circuit

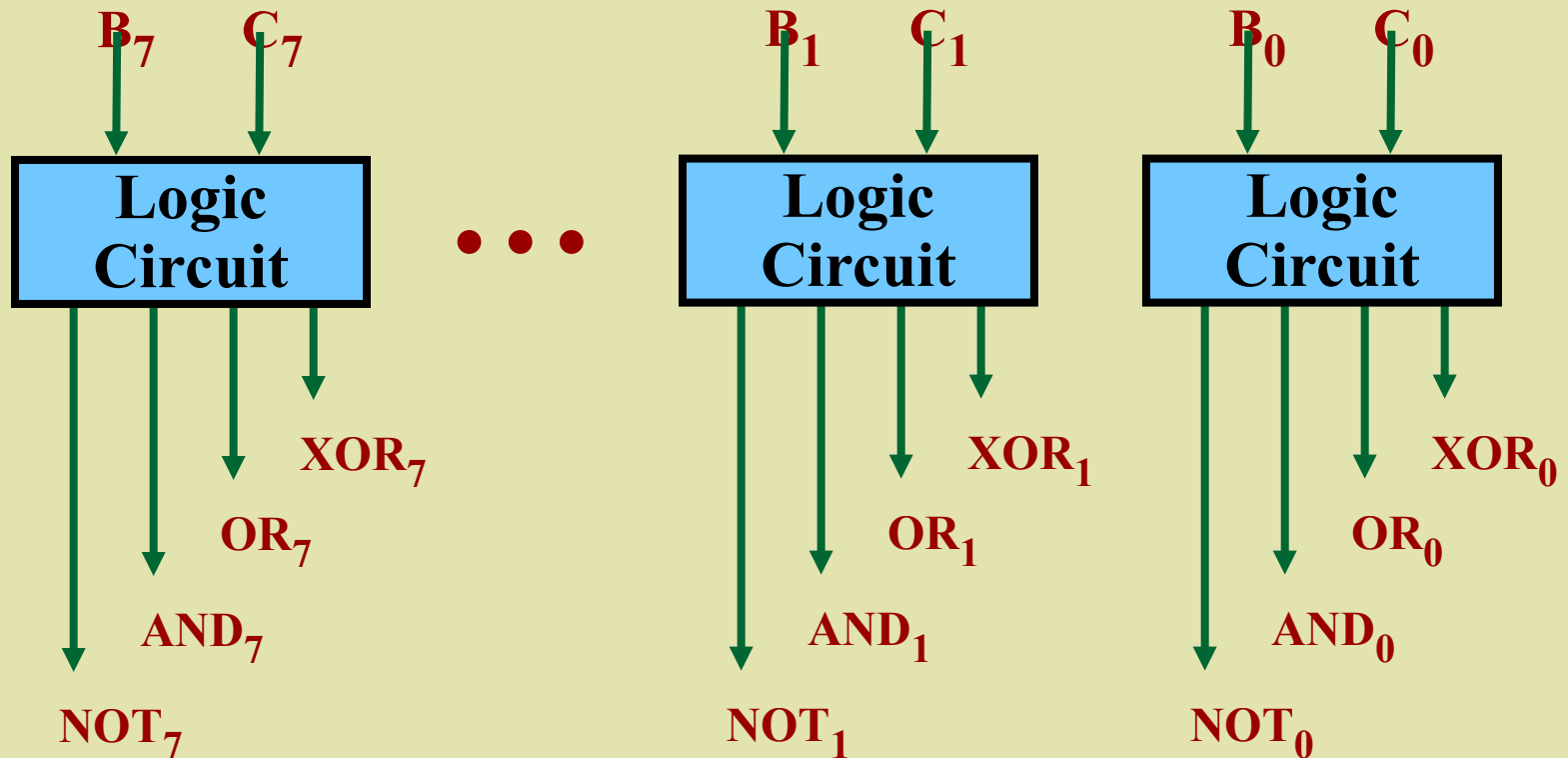


The “Full Adder” Circuit

Cy_{in}	B	C	Cy_{out}	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


8 full-adders can be combined to build an...

8-Bit Adder

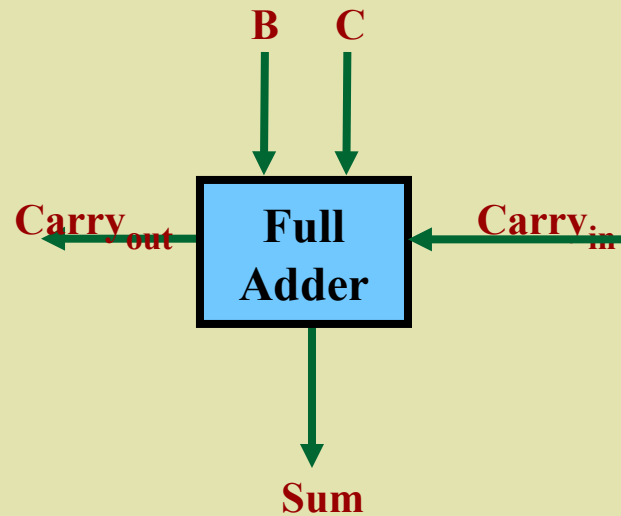



8 full-adders can be combined to build an...

8-Bit Adder

 


8 full-adders can be combined to build an...


8-Bit Adder

  


The Zero-Detect Circuit

 


The Zero-Detect Circuit

 


Enable Circuit

 


Enable Circuit

 

Enable Circuit

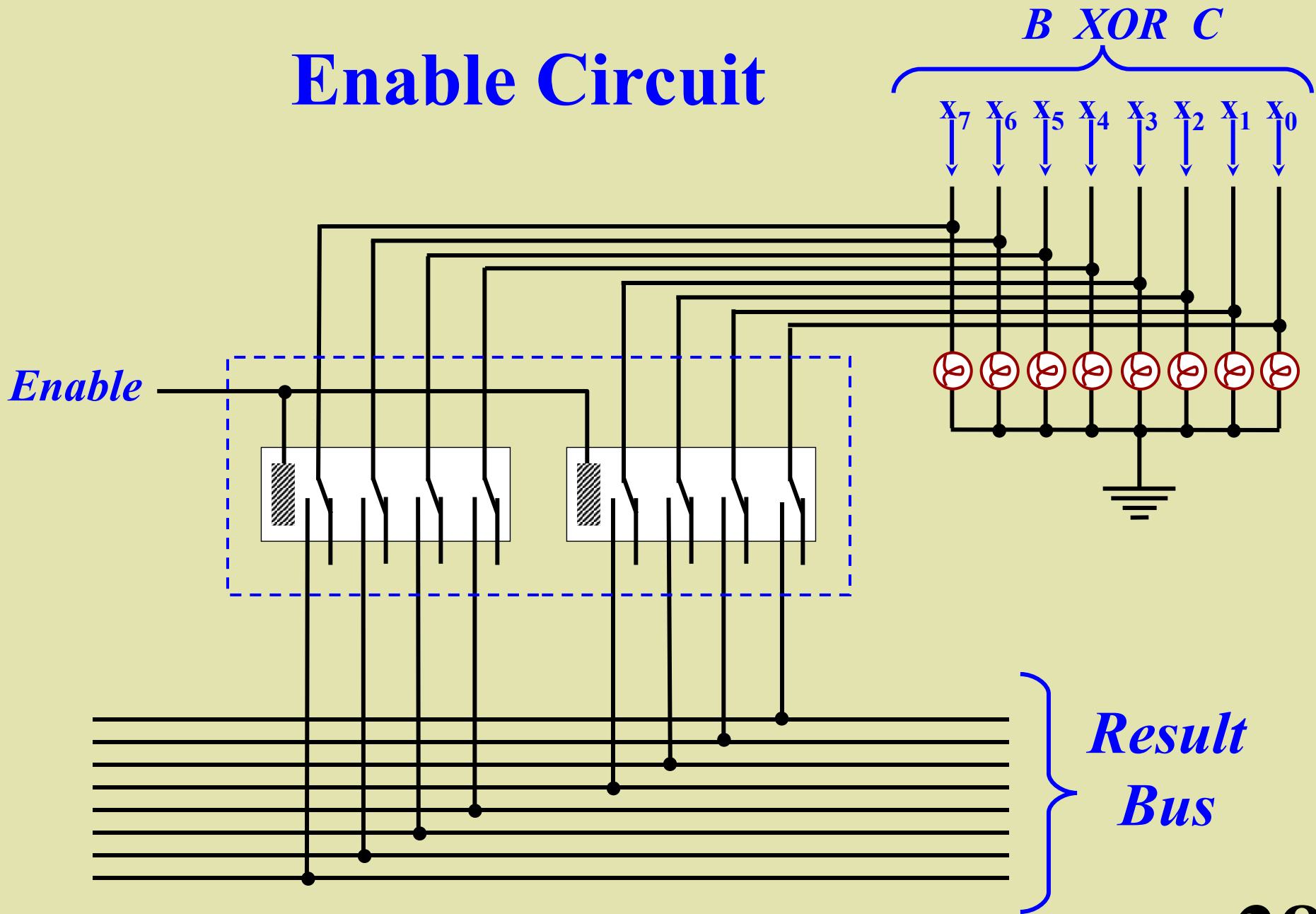

Shift Left Circular (SHL)

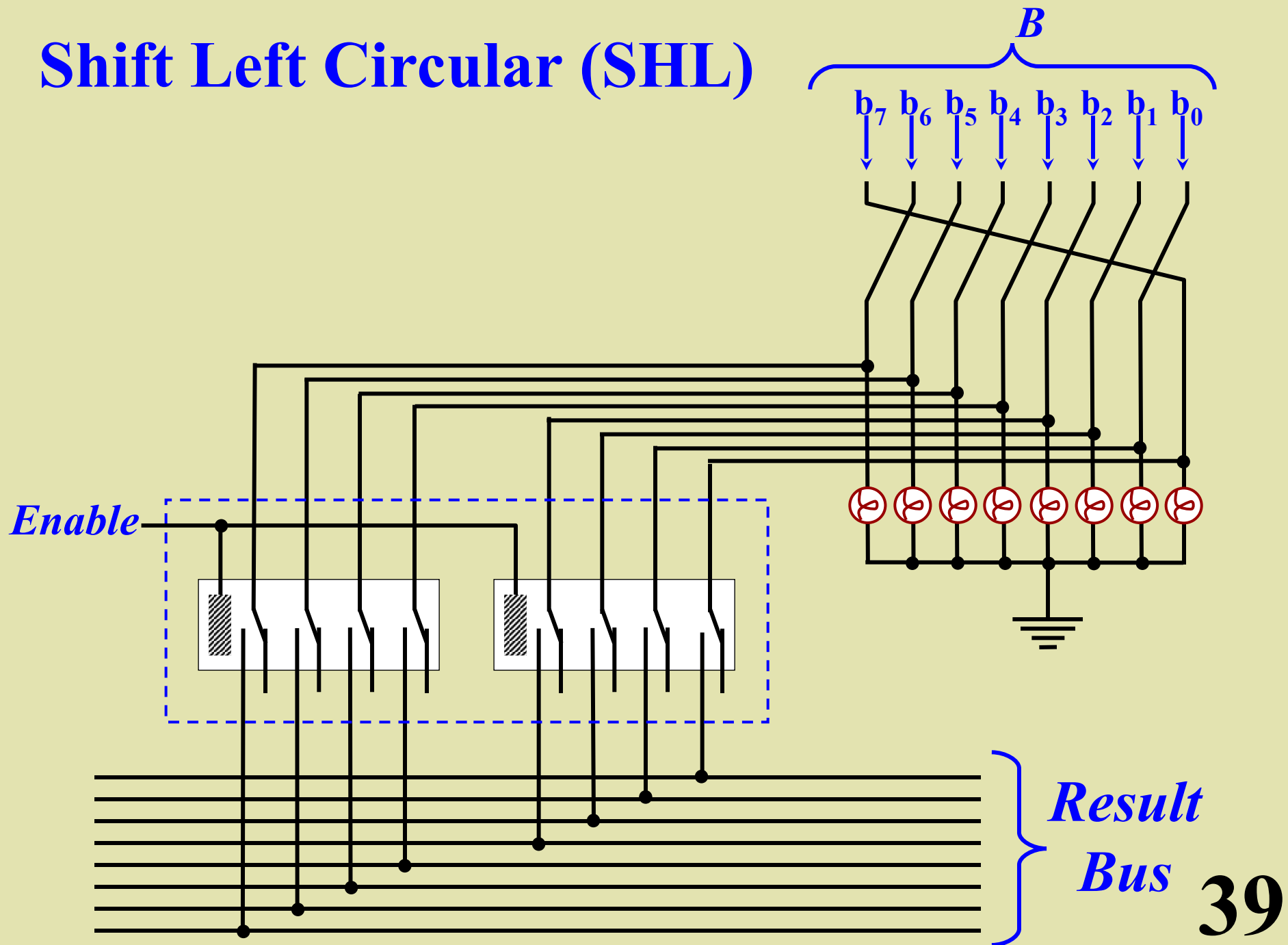


3-to-8 Decoder

f_0	f_1	f_2	OUTPUT							
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


3-to-8 Decoder

f_0	f_1	f_2	OUTPUT								
0	0	0	1	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	1	1

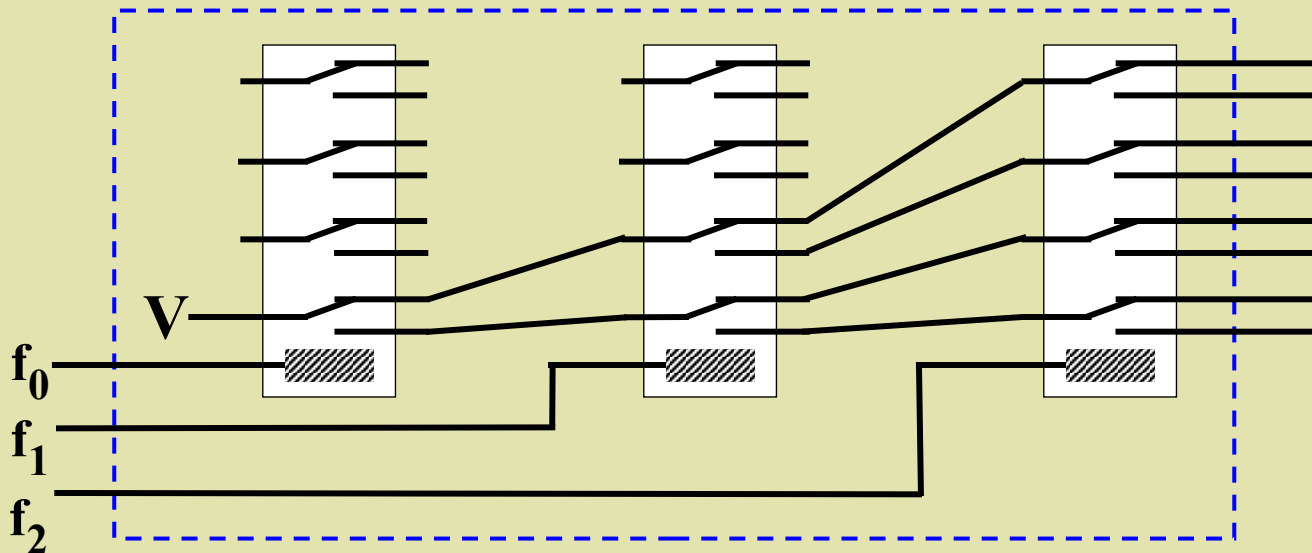


3-to-8 Decoder


f_0	f_1	f_2	OUTPUT							
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 


Arithmetic Logic Unit (ALU)

 


An 8-Bit ALU

 


Register Storage

 


Register Storage

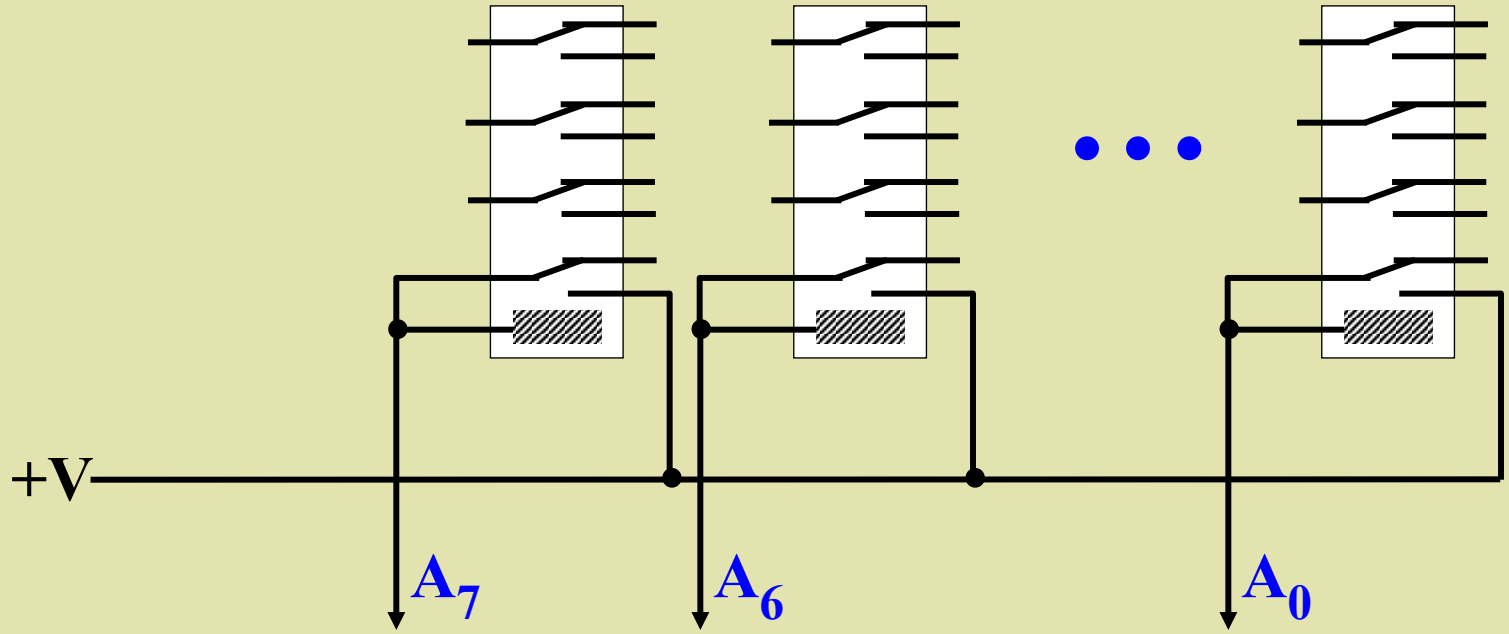


Register Storage

 


Register Storage

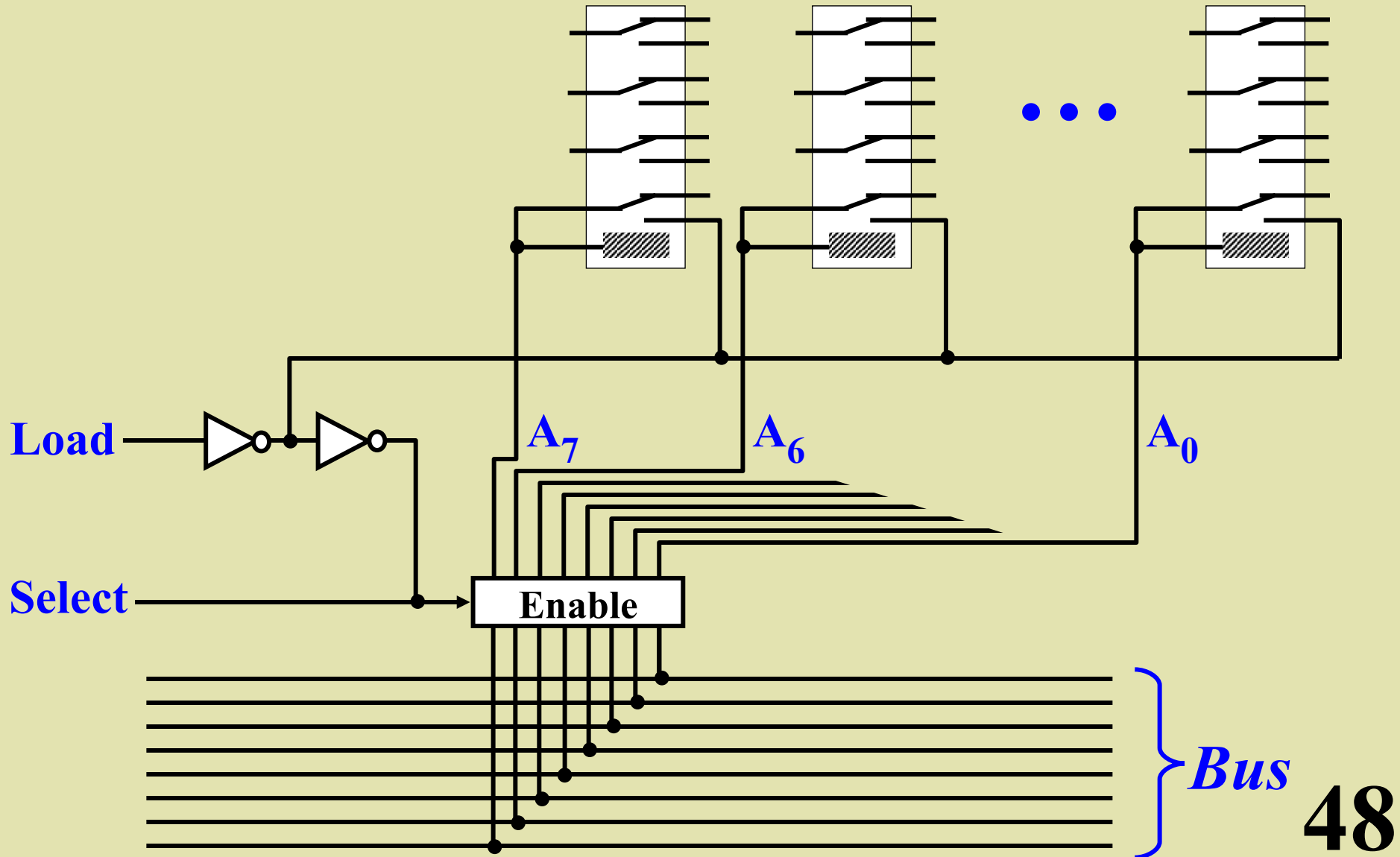

Register Storage

 


8-Bit Registers

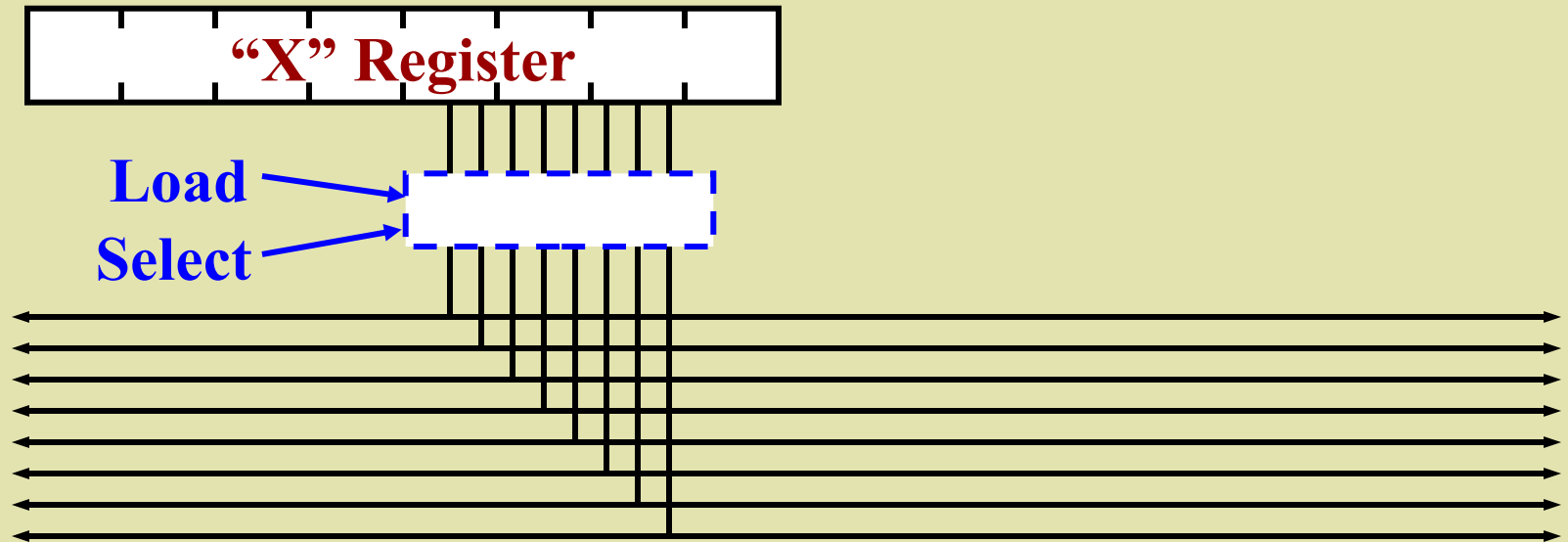


8-Bit "Data" Bus

8-Bit Registers

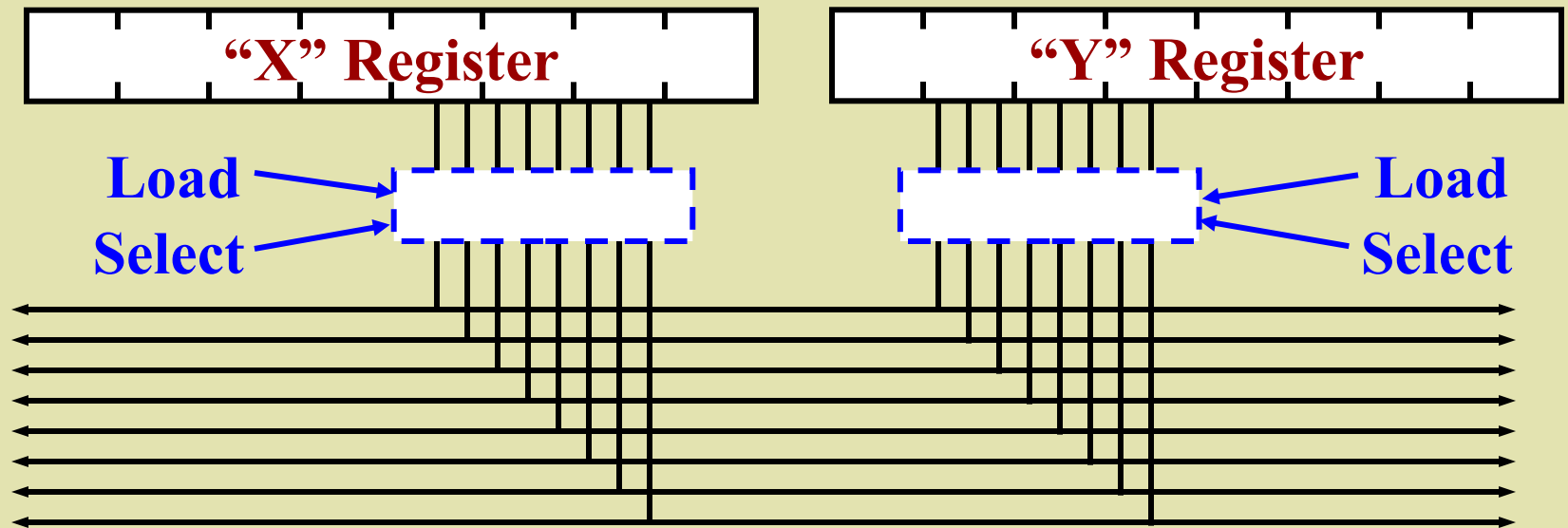


8-Bit "Data" Bus

16-Bit “Address” Bus

 


8-Bit “Data” Bus

8-bit Data Bus

 


System Architecture

8-bit Data Bus

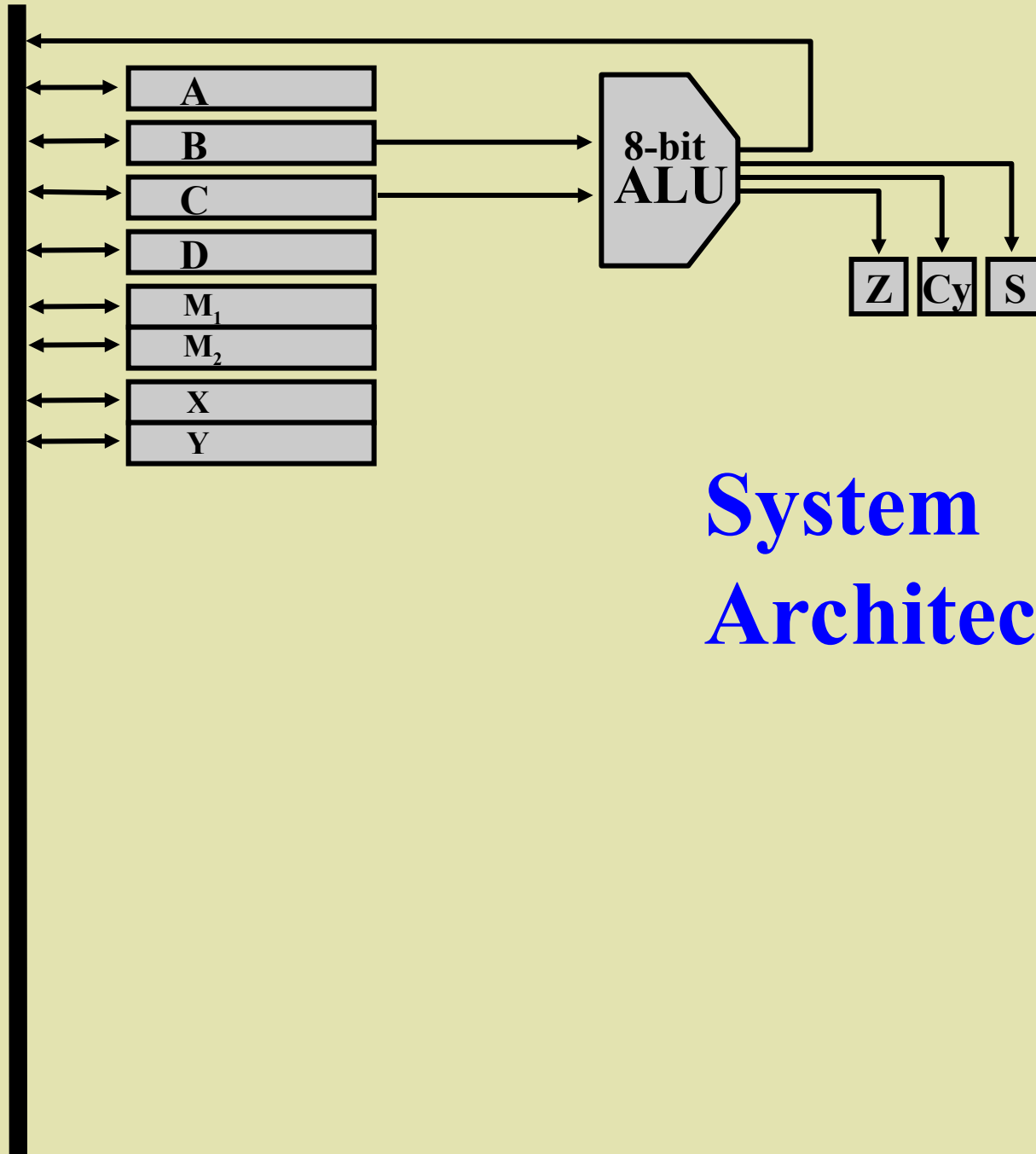


System Architecture

8-bit Data Bus

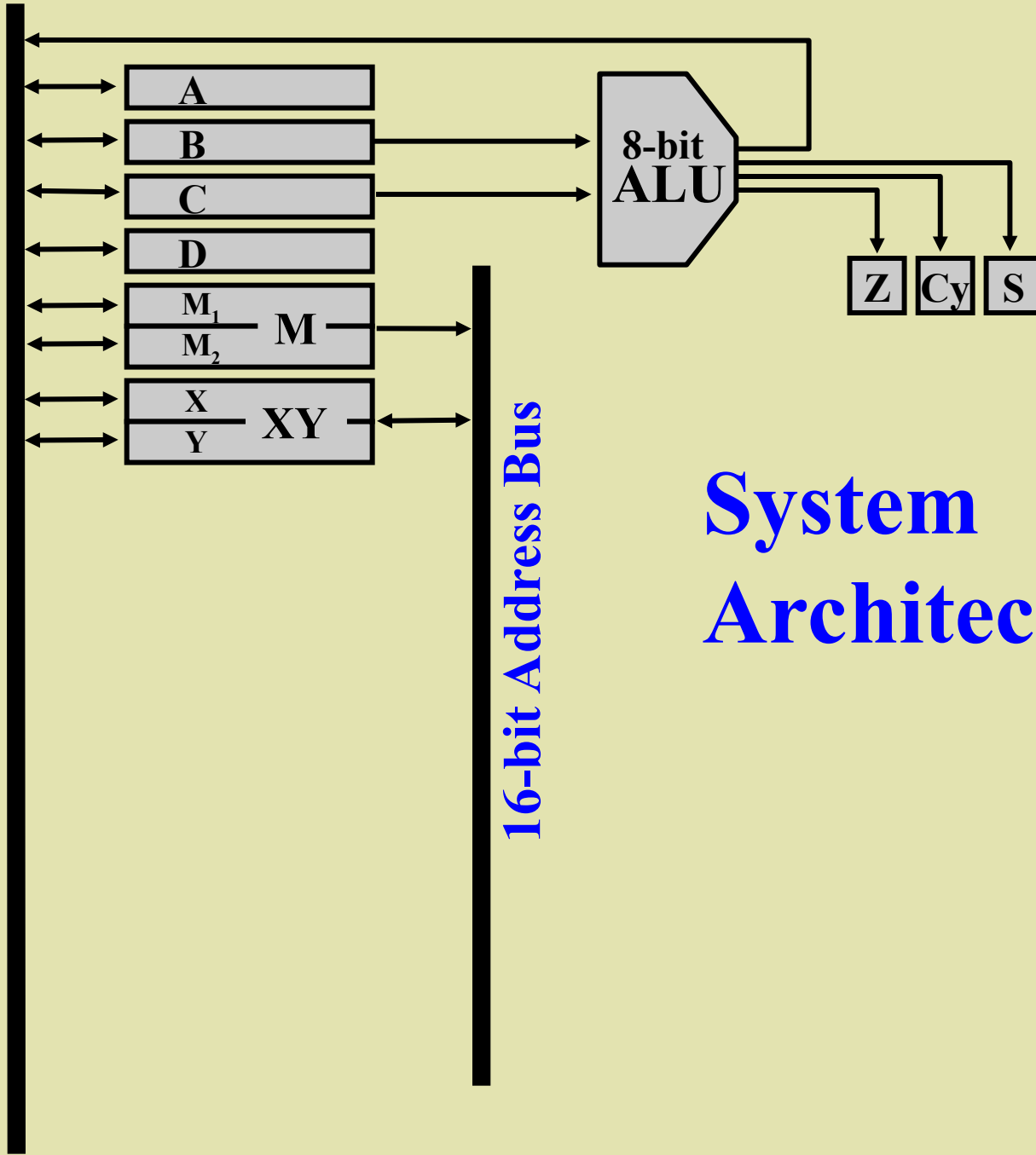


System Architecture

8-bit Data Bus

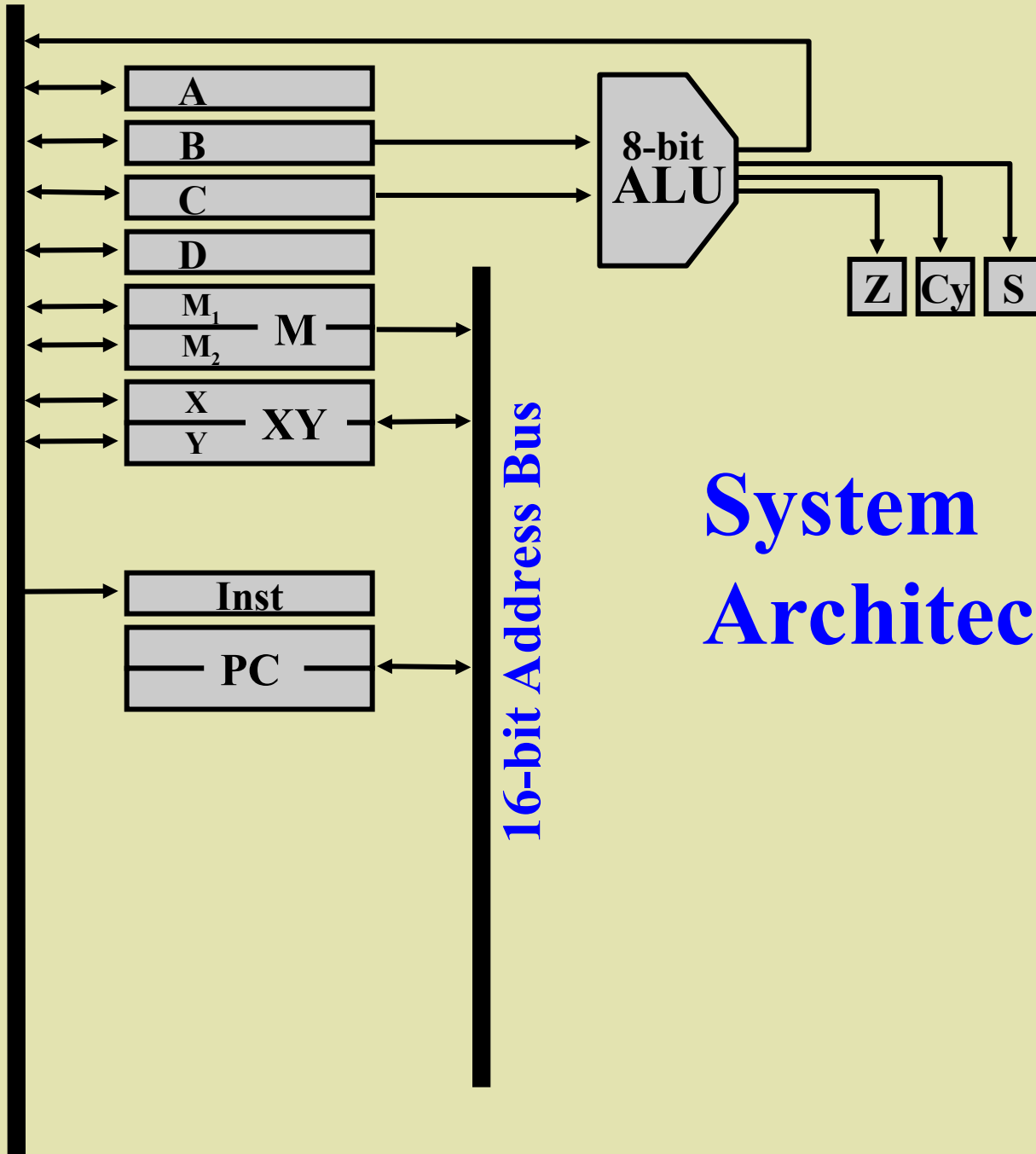



System Architecture

8-bit Data Bus

 


System Architecture

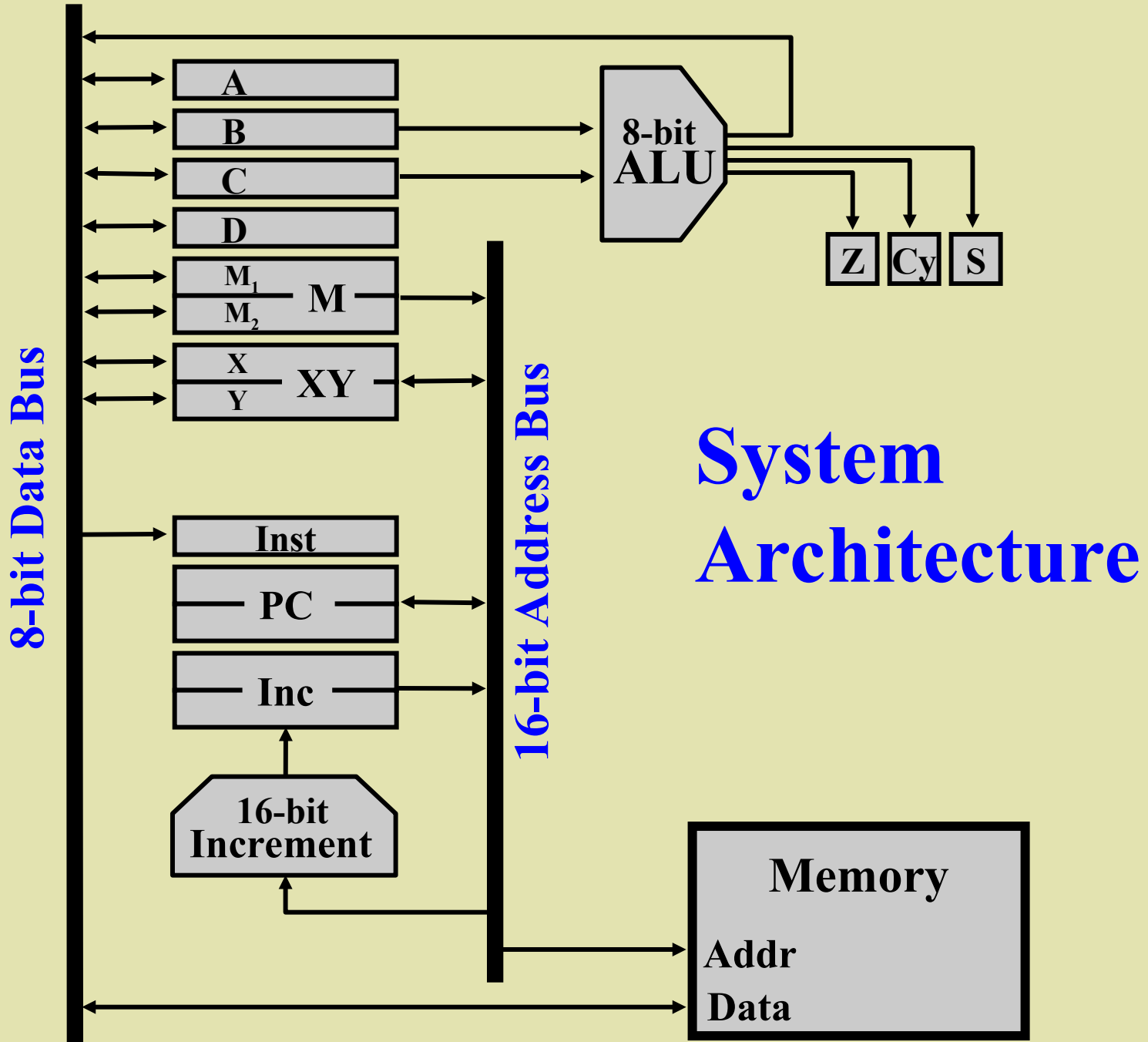

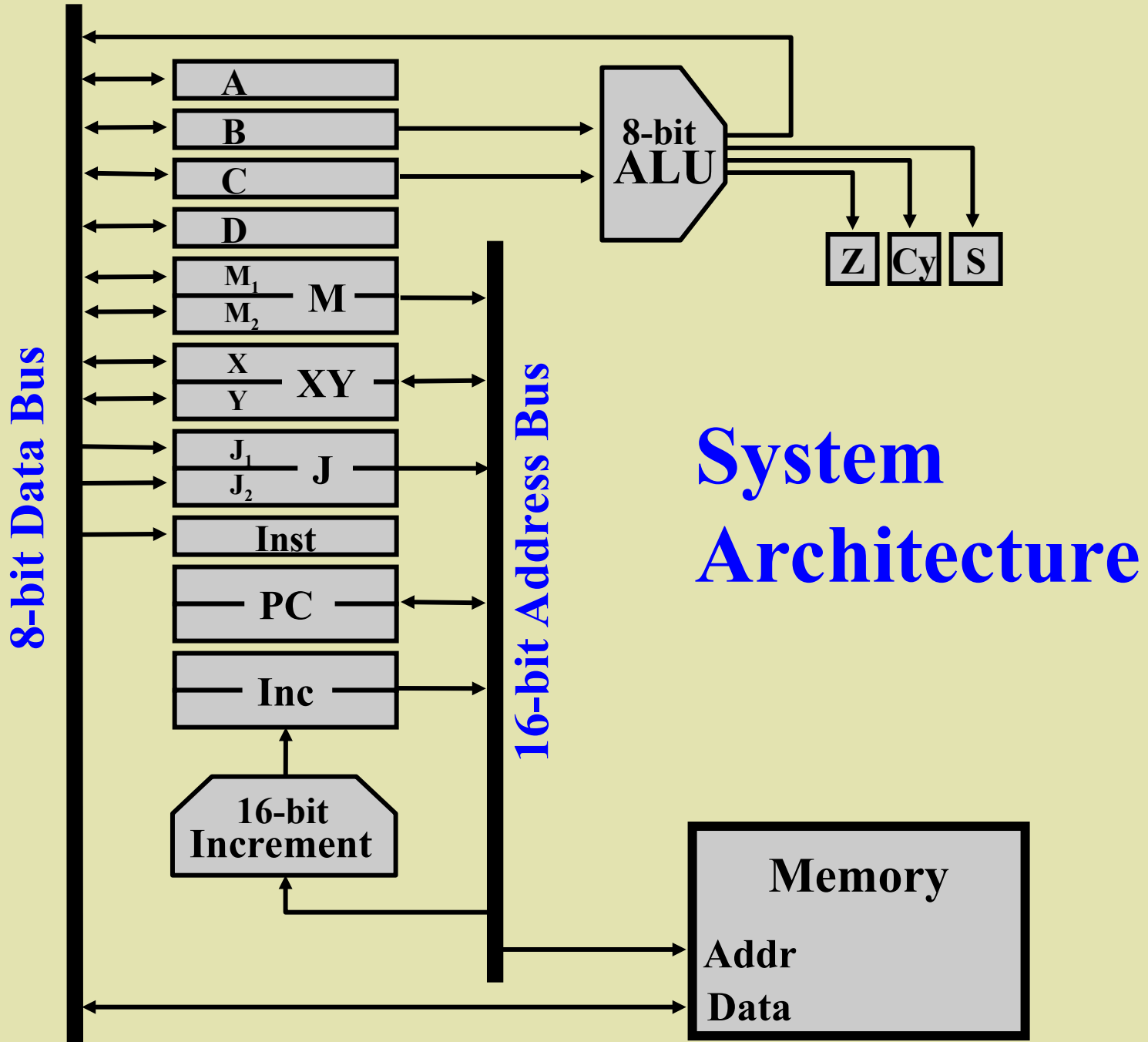

System Architecture

 


QuickTime™ and a
TIFF (LZW) decompressor
are needed to see this picture.

**32K Byte Static
RAM Chip**




LEDs

 


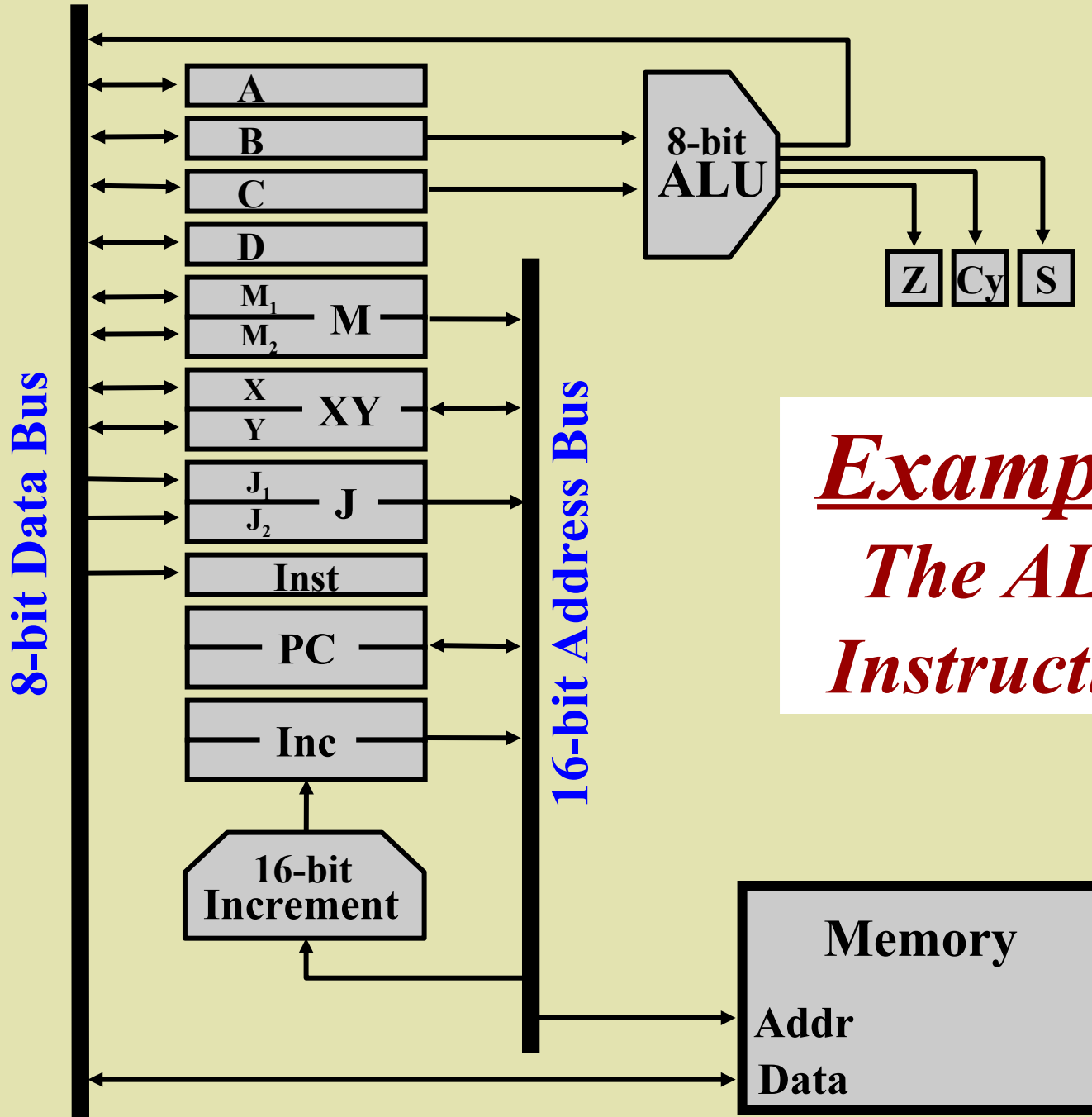8 FET Power Transistors
*(to drive relays during
a memory-read operation)*







Example:
The ALU
Instruction

 



Step 1:
Fetch Instruction

 



Step 1:
Fetch Instruction

 


 

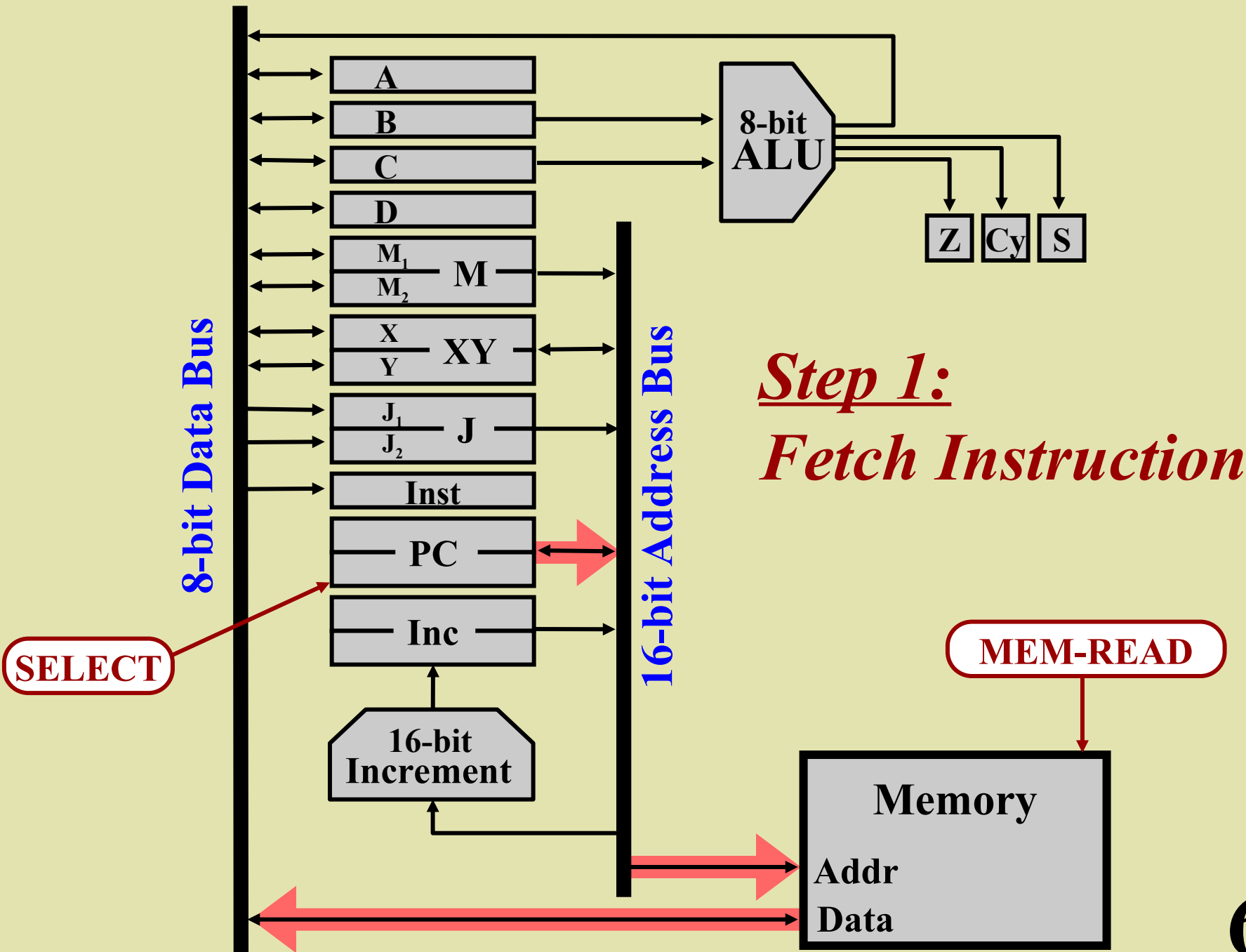


 

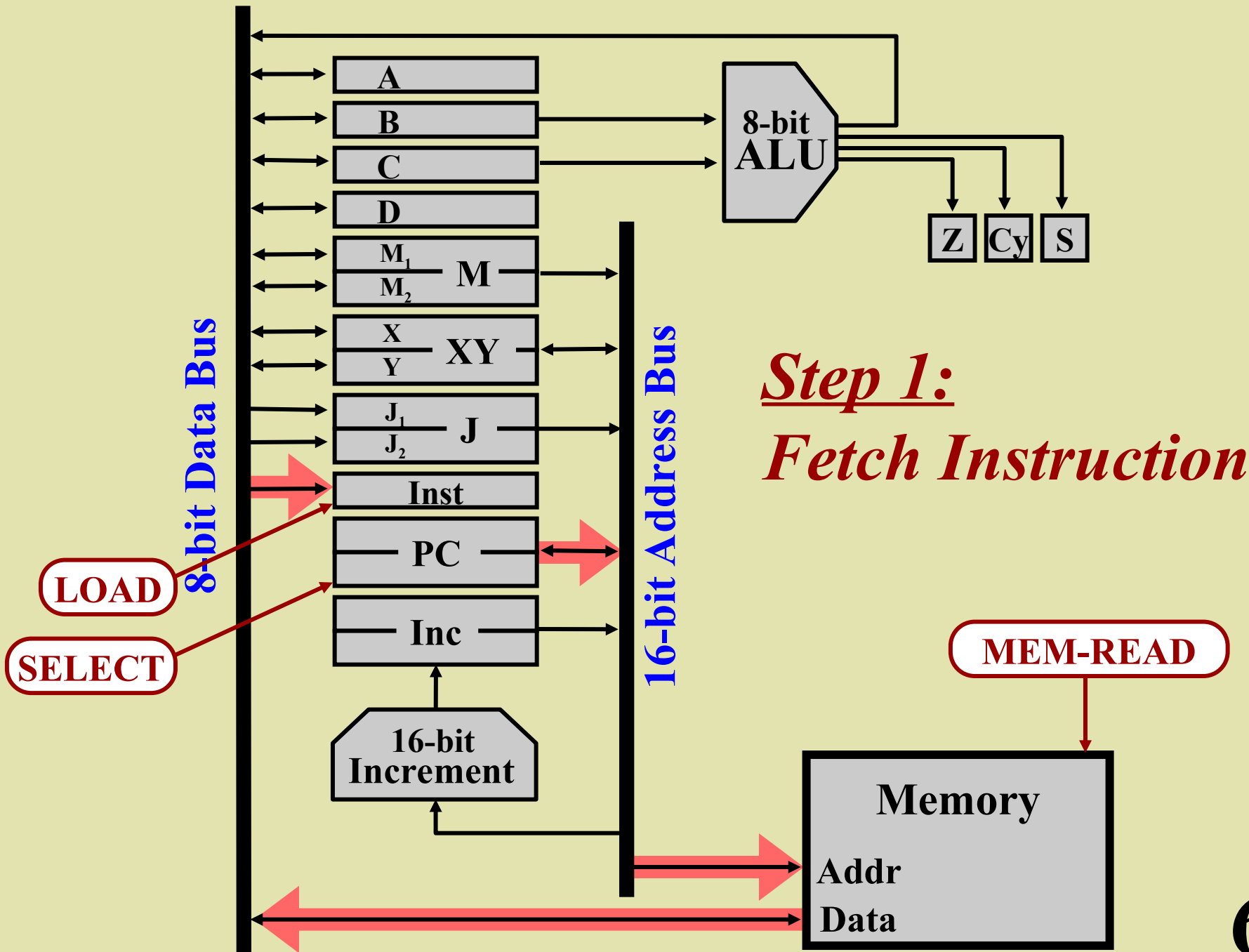


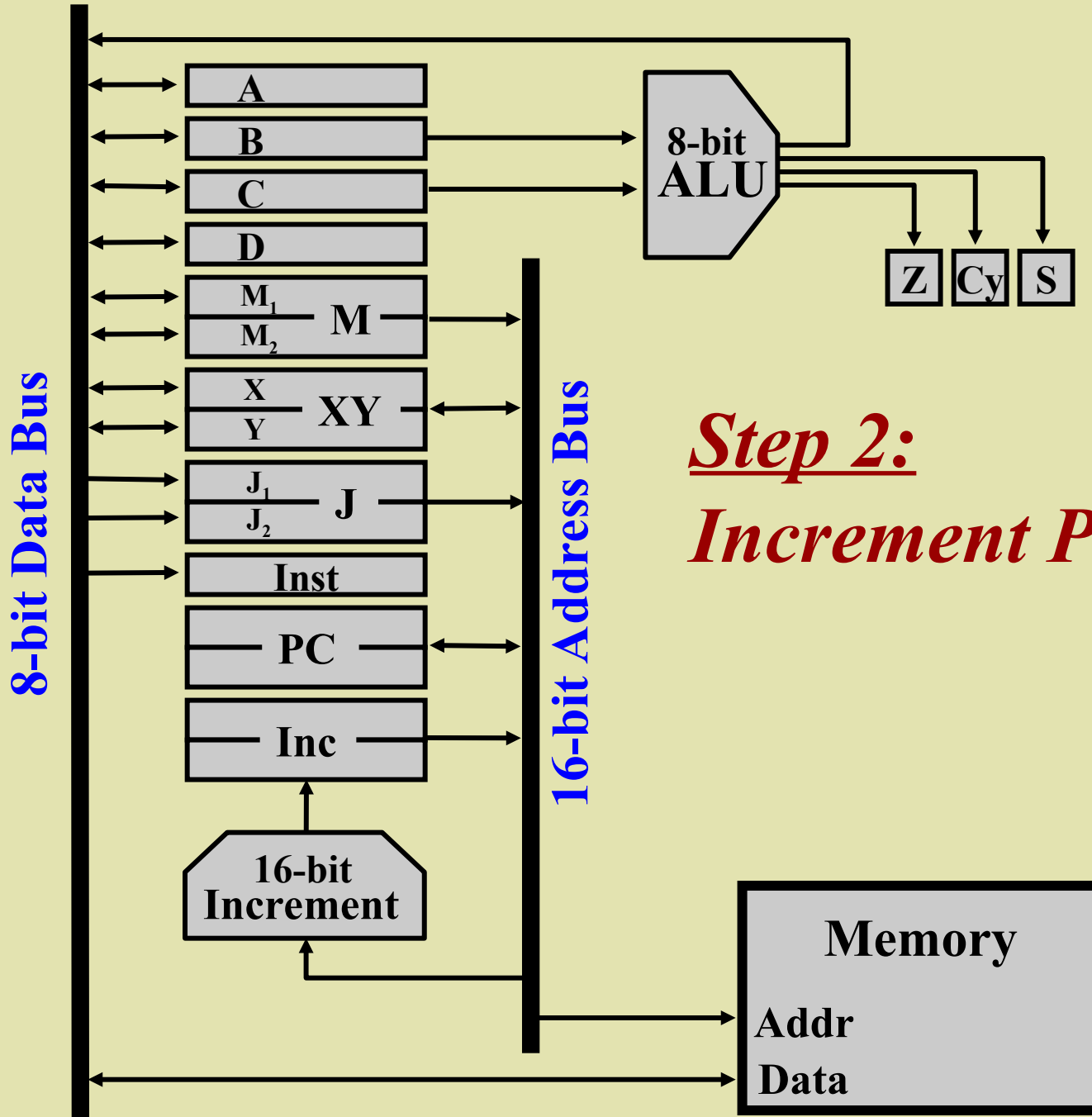


***Step 2:
Increment PC***

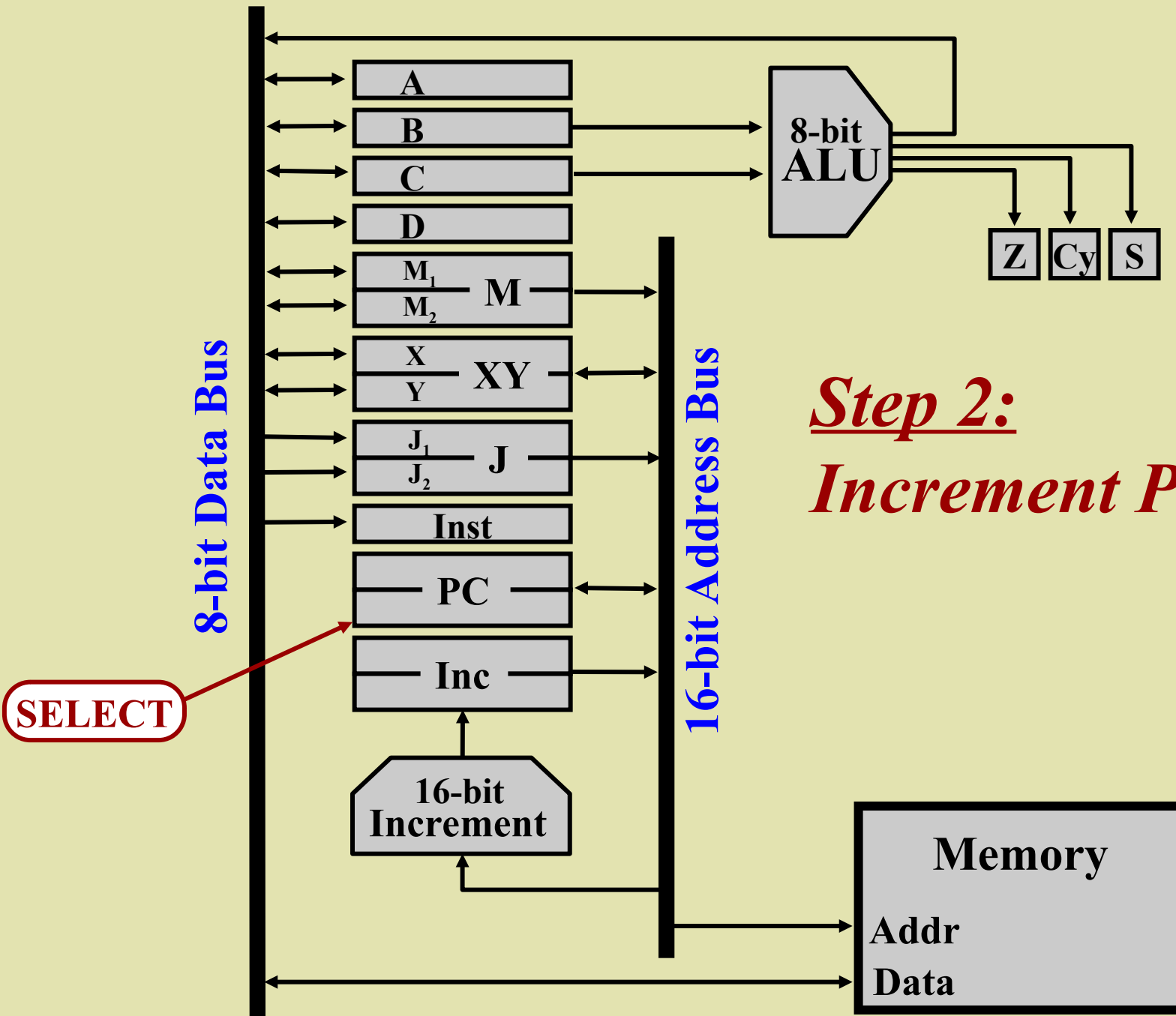


***Step 2:
Increment PC***

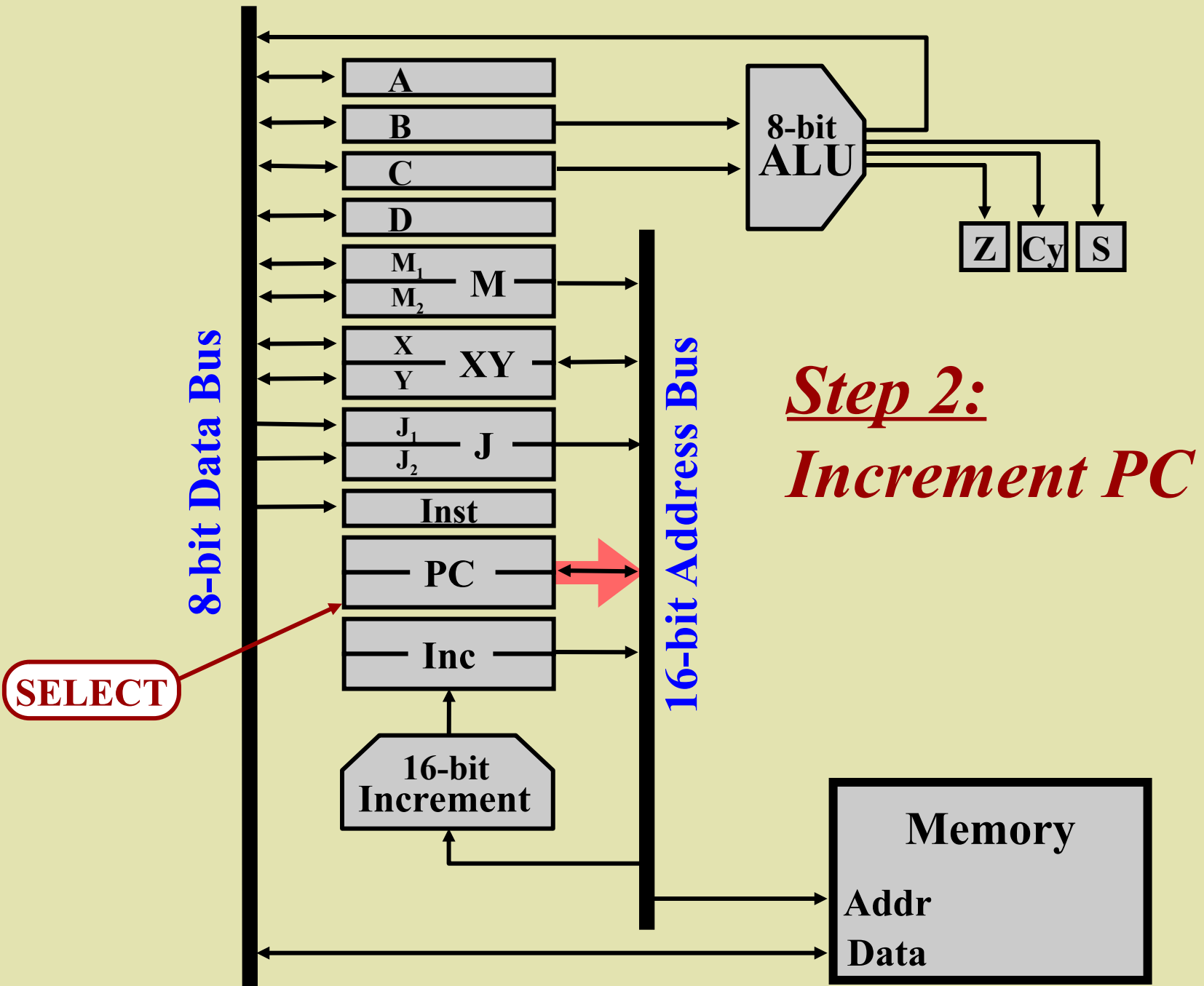


***Step 2:
Increment PC***

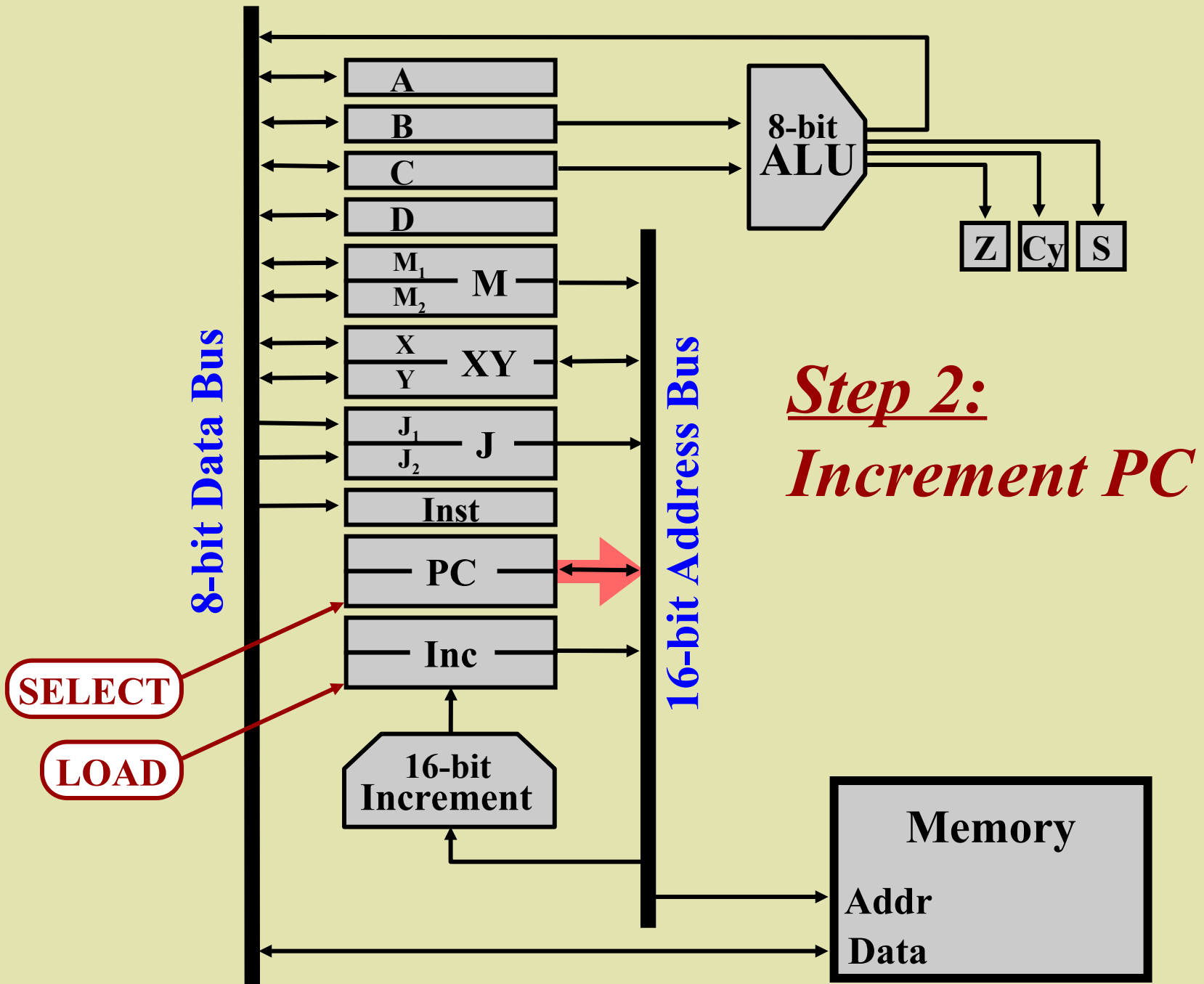


***Step 2:
Increment PC***

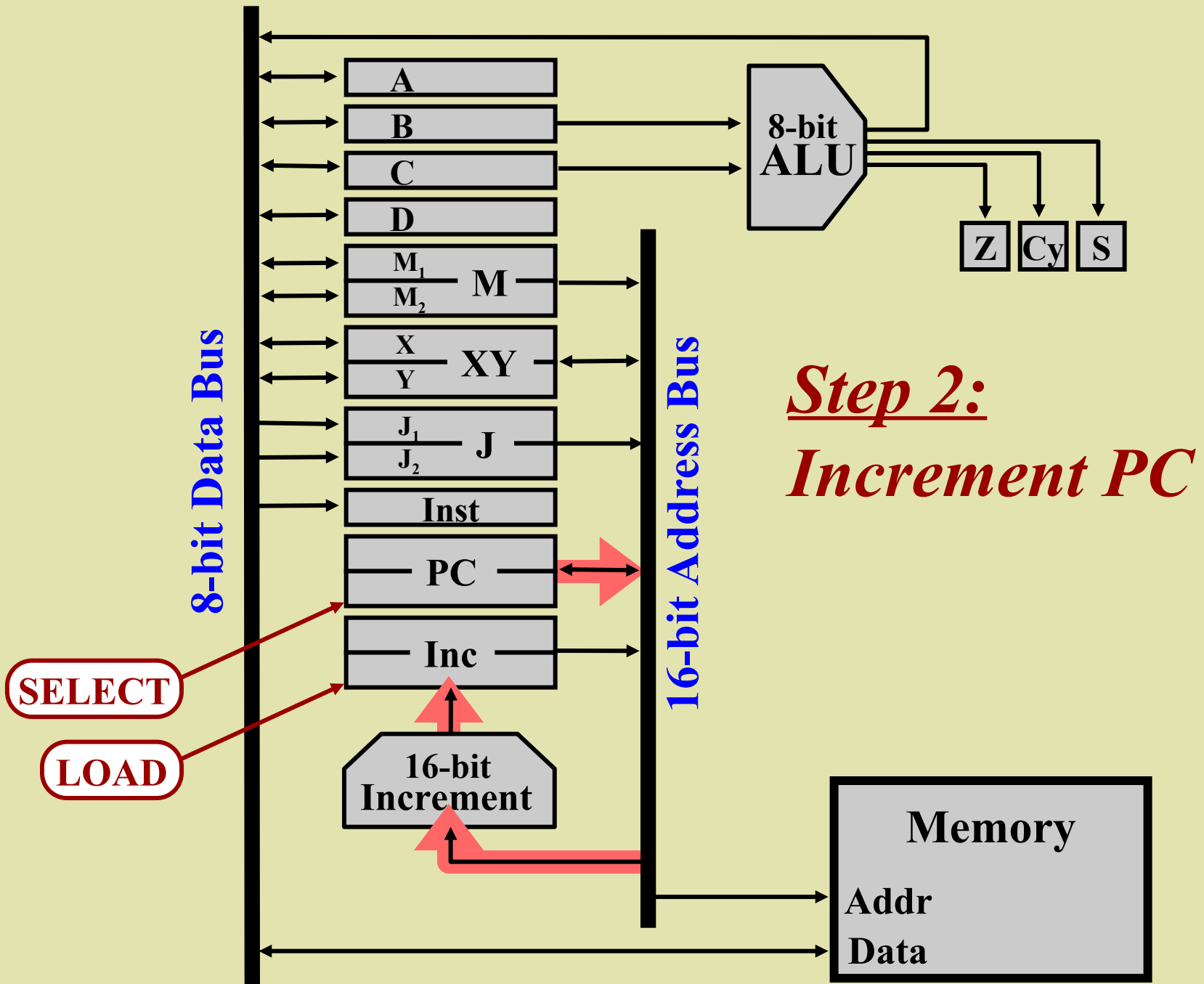


*Step 2:
Increment PC*

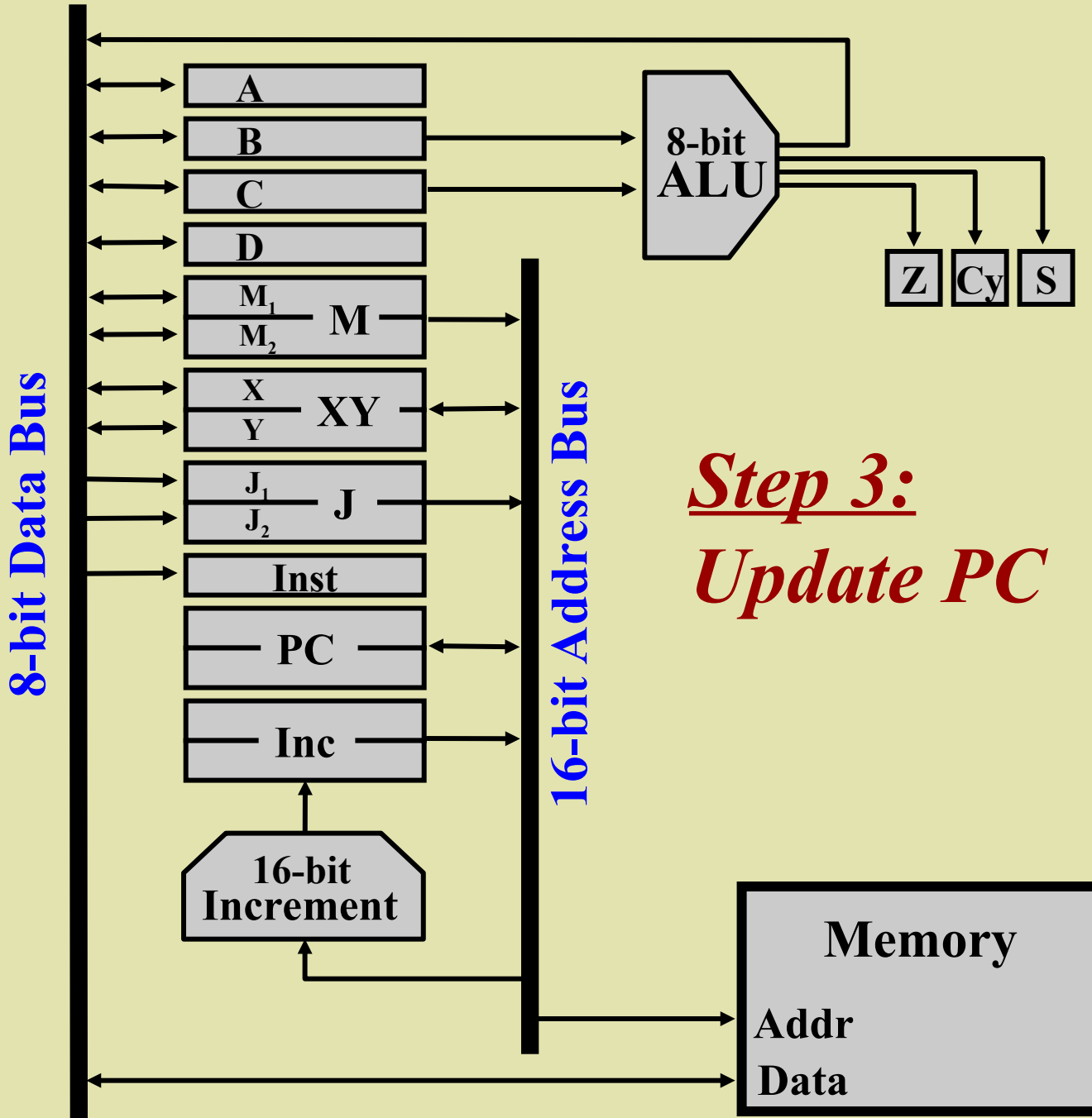


*Step 3:
Update PC*

 


 


*Step 3:
Update PC*

 


*Step 3:
Update PC*

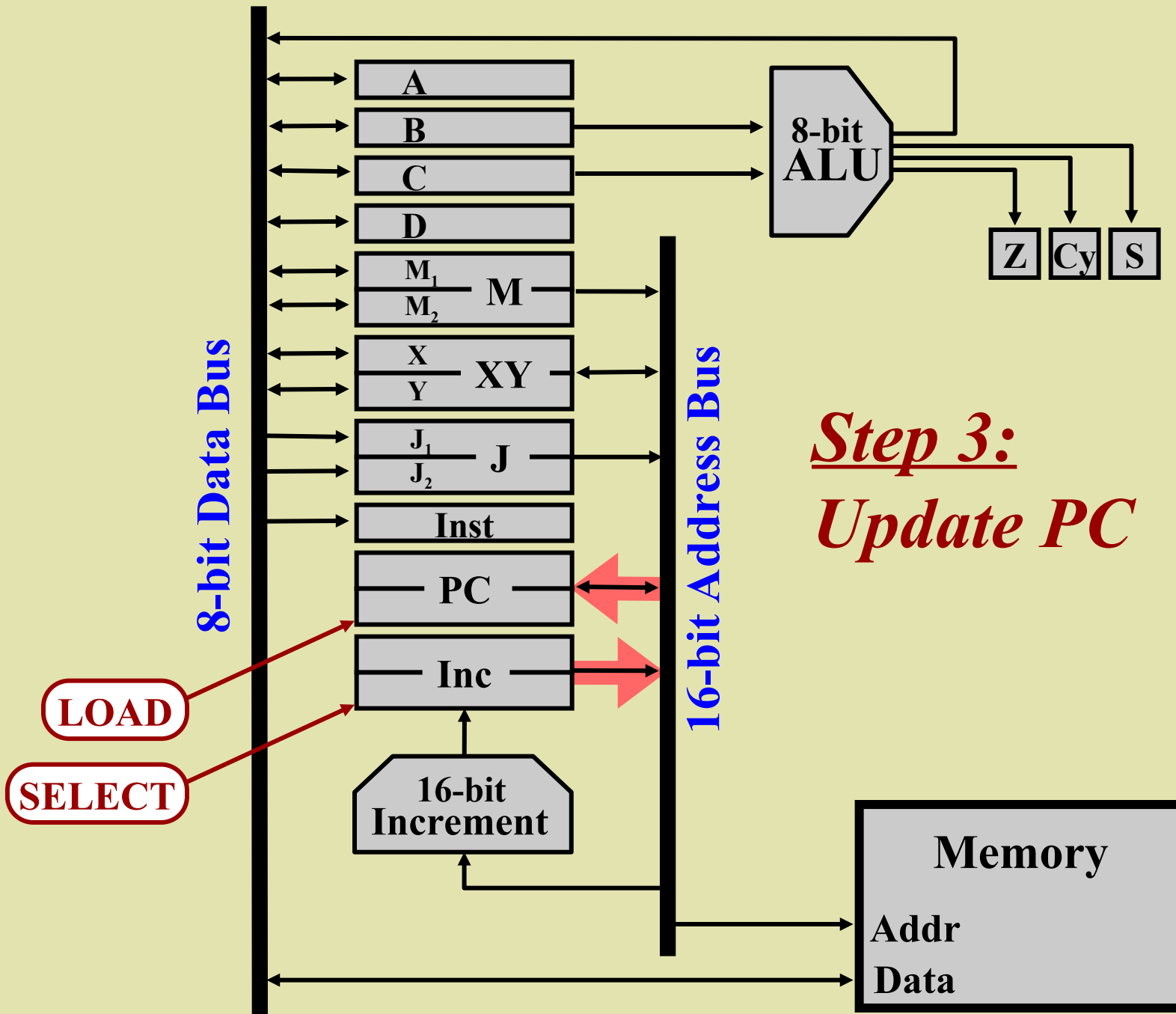


 

Step 4:
Execute Instruction

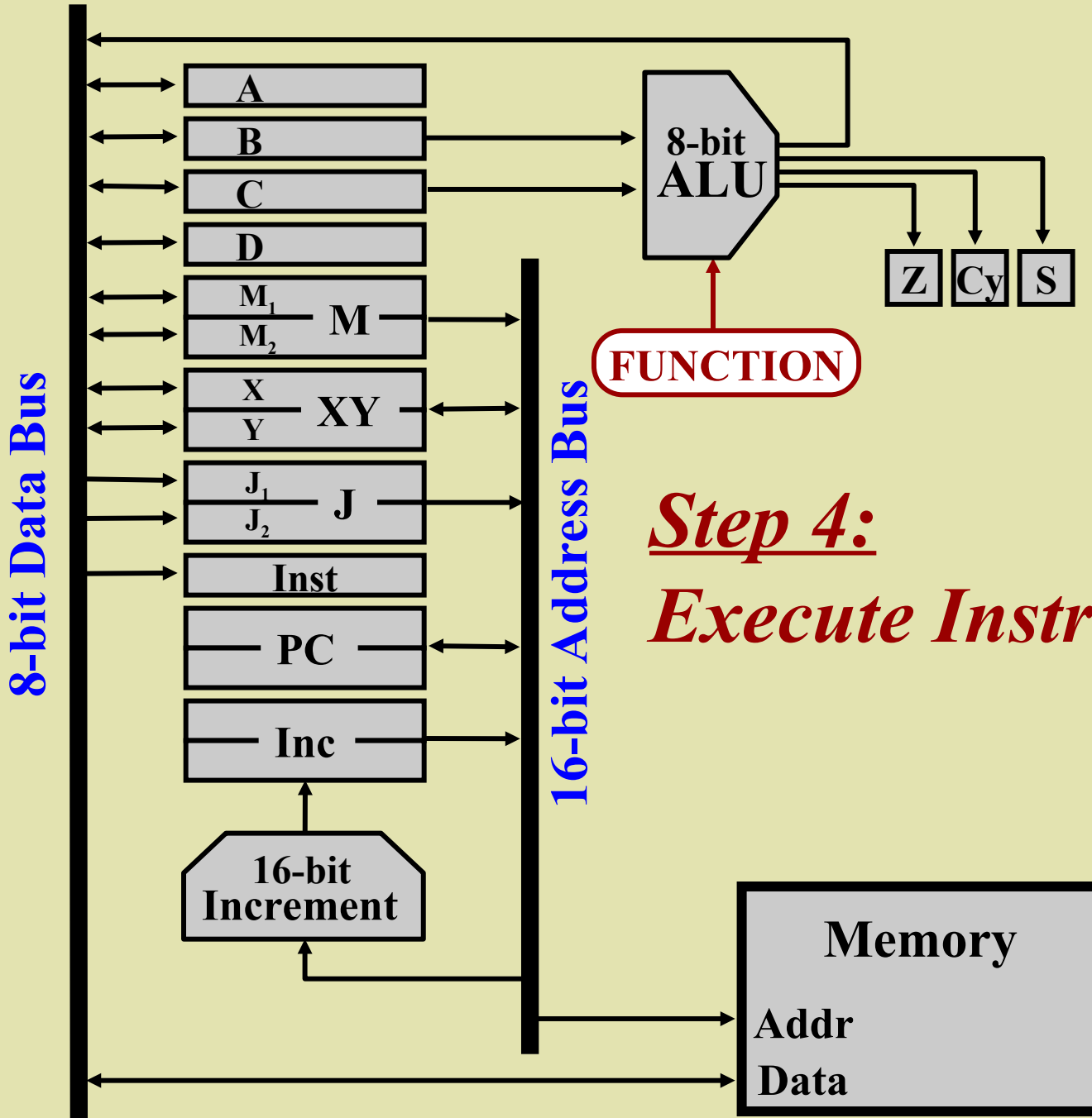


***Step 4:
Execute Instruction***

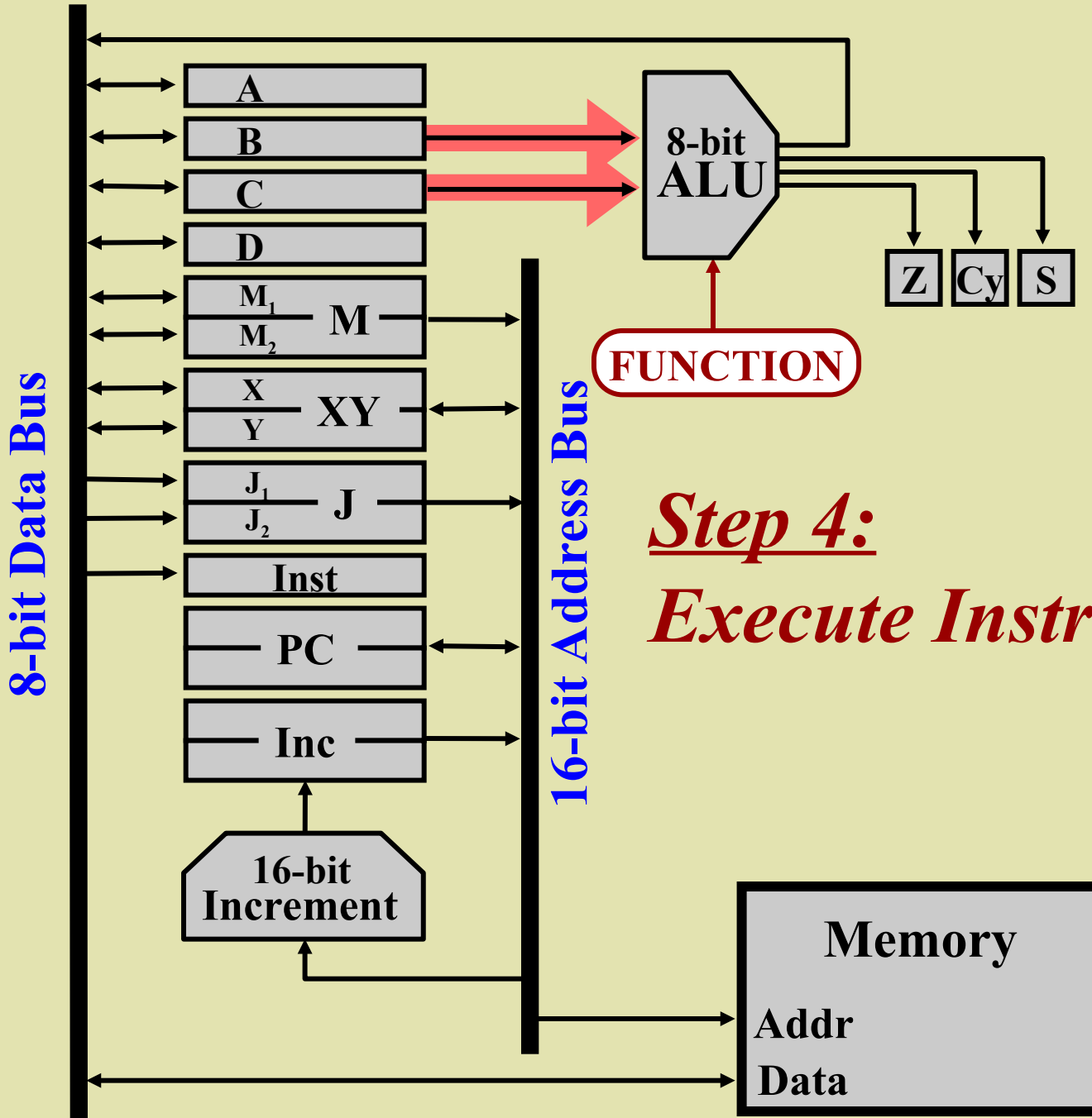



*Step 4:
Execute Instruction*

8-bit Data Bus

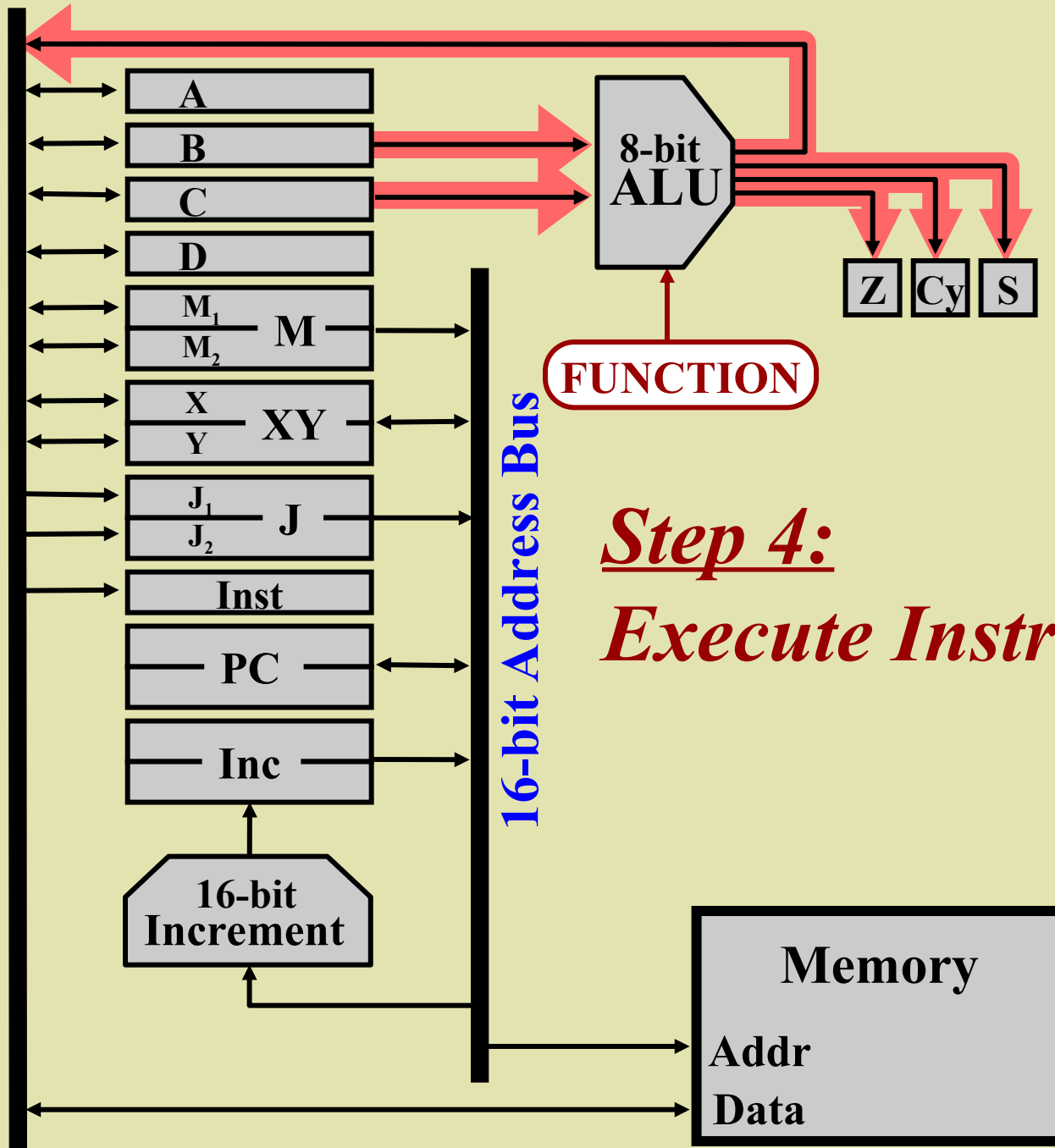


Step 4:
Execute Instruction

 


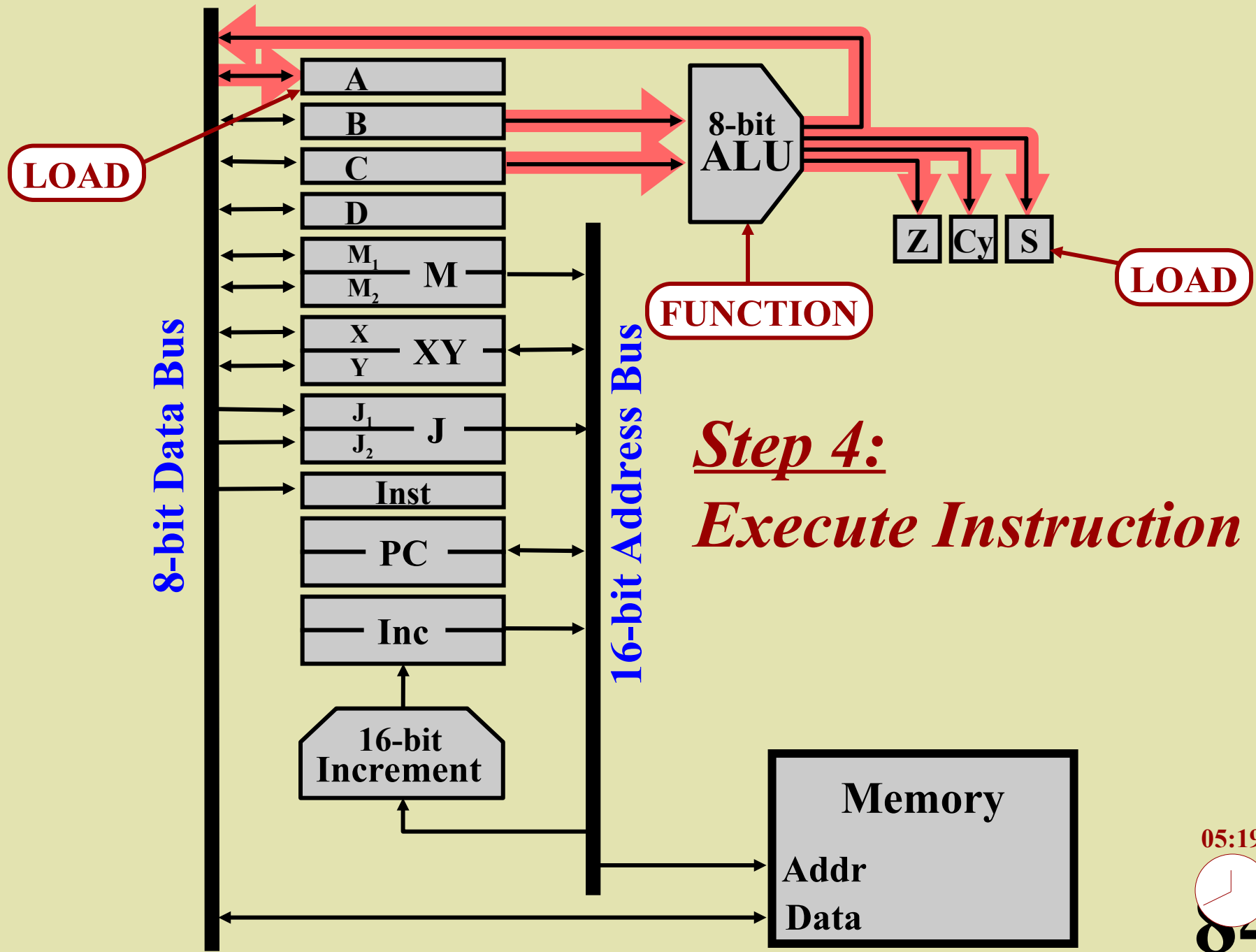


Clock

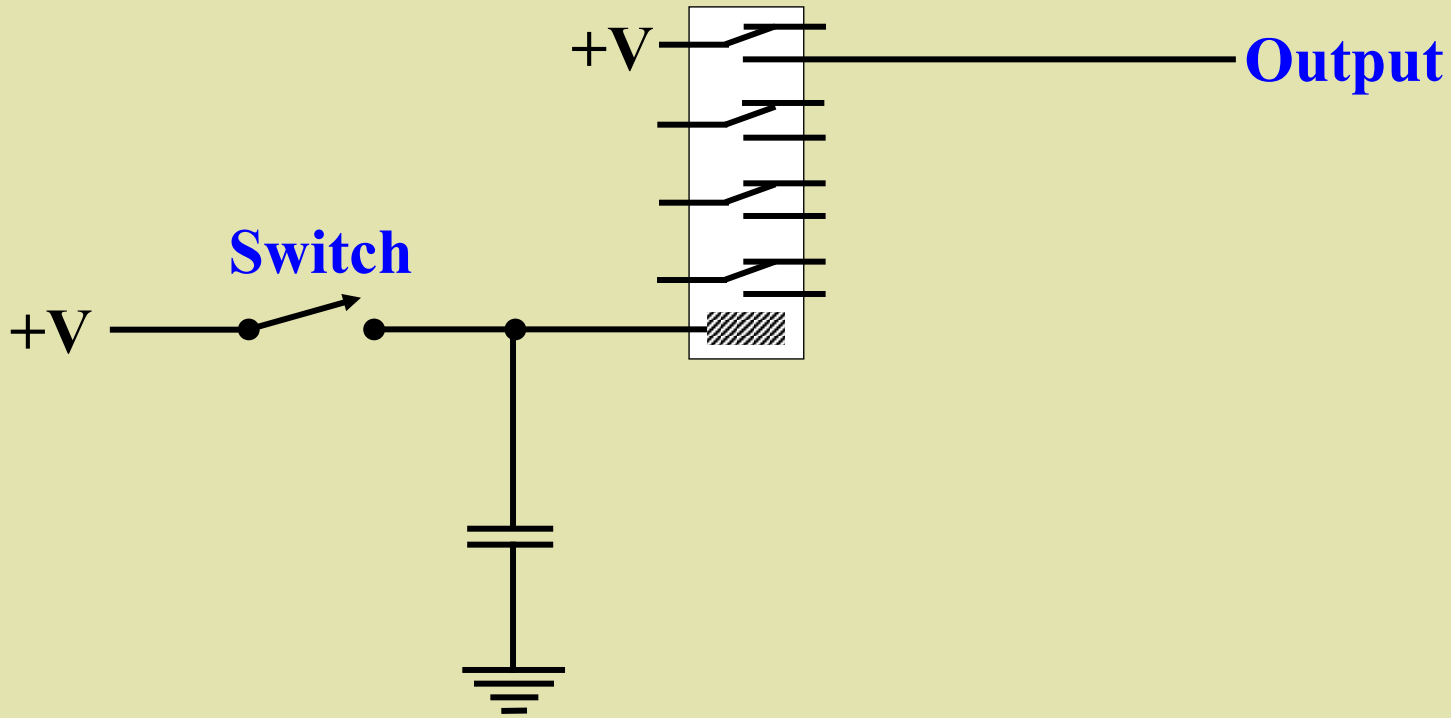


Clock

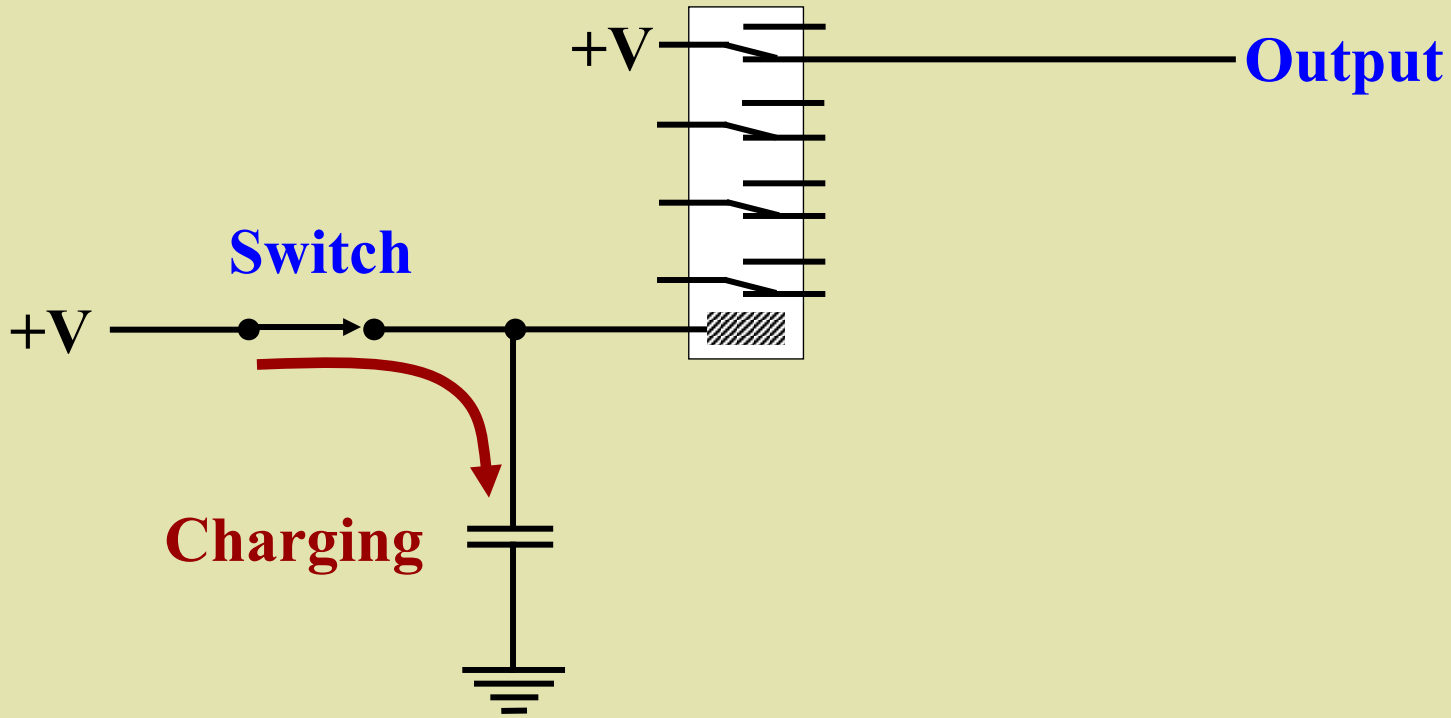


Clock

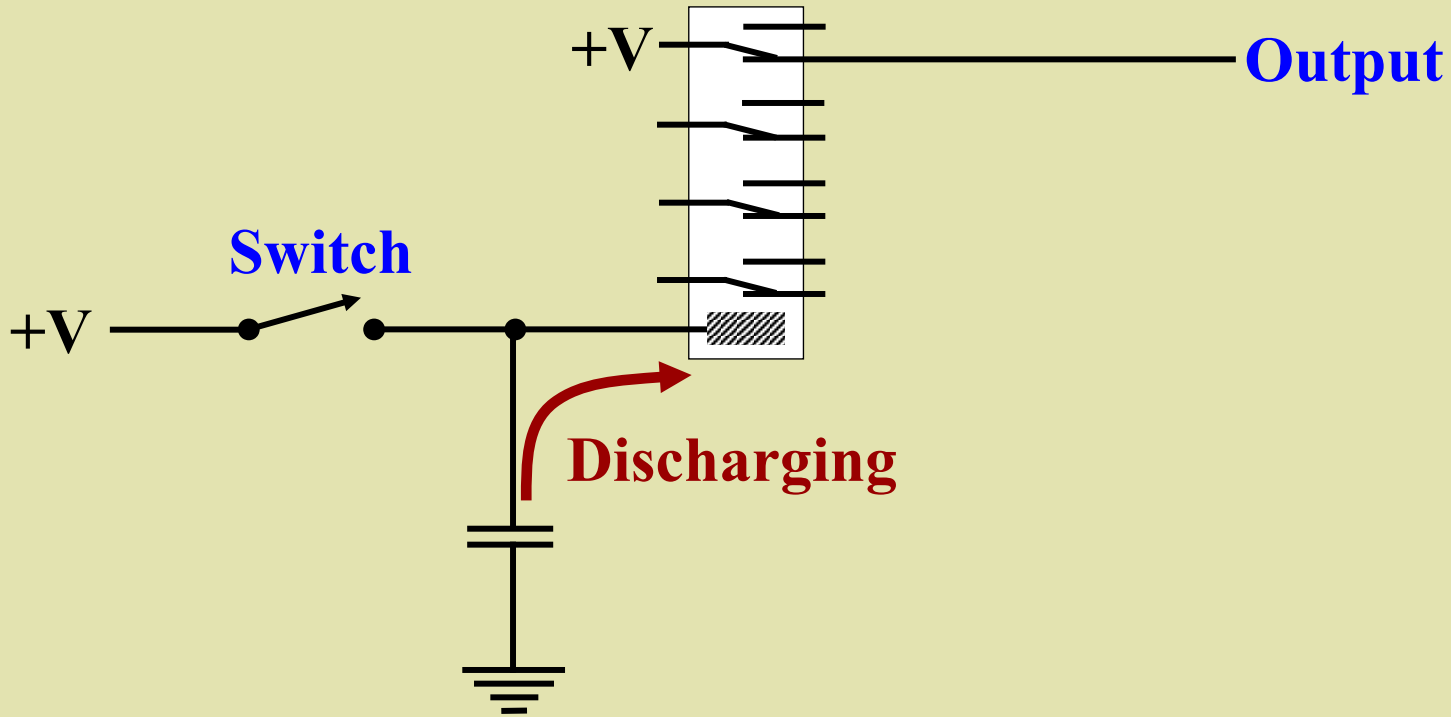


Clock

 


Clock

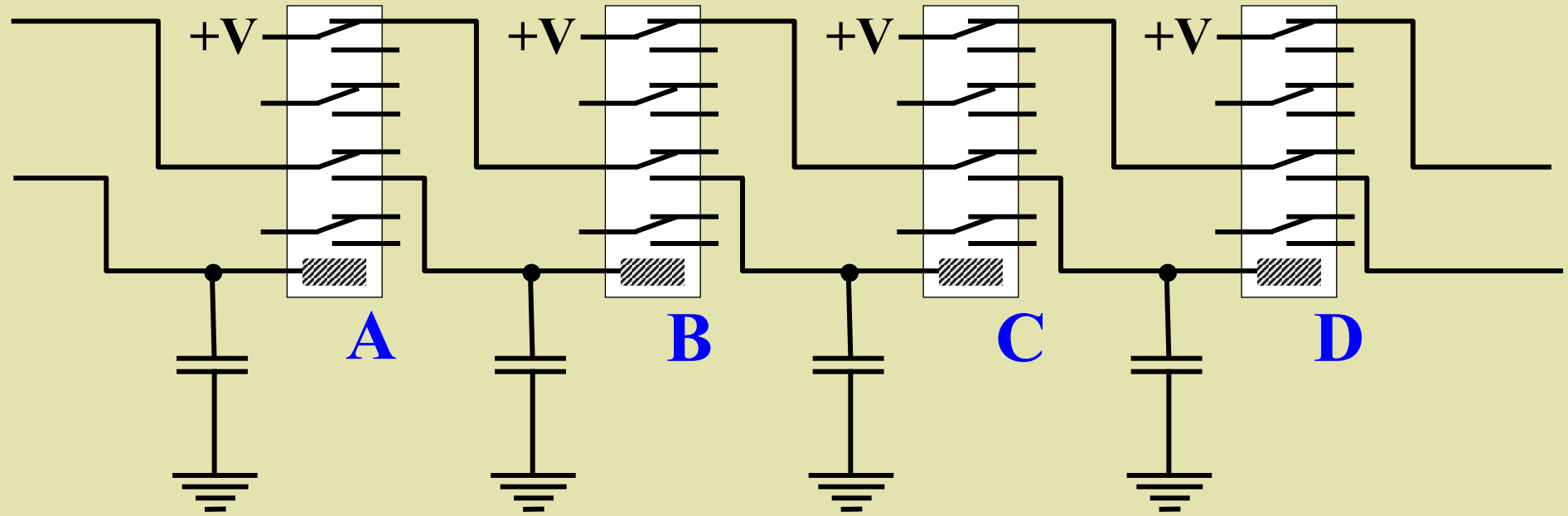


Clock

 


Clock

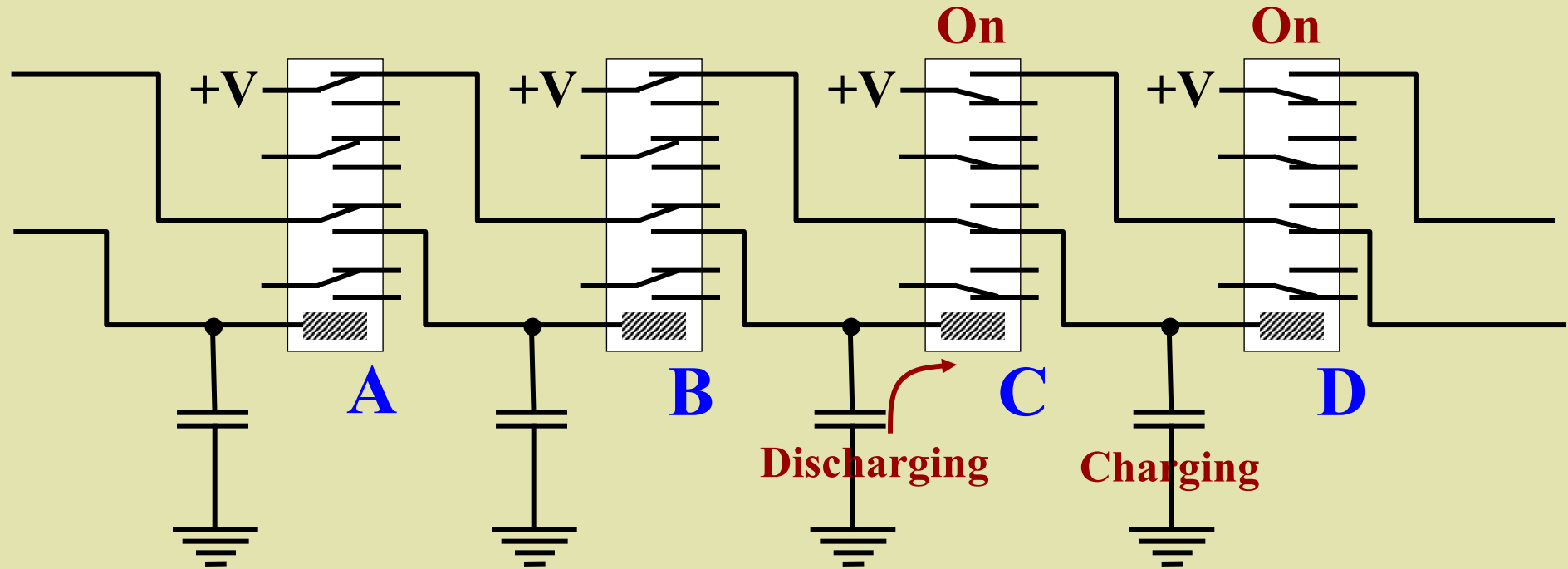


Clock

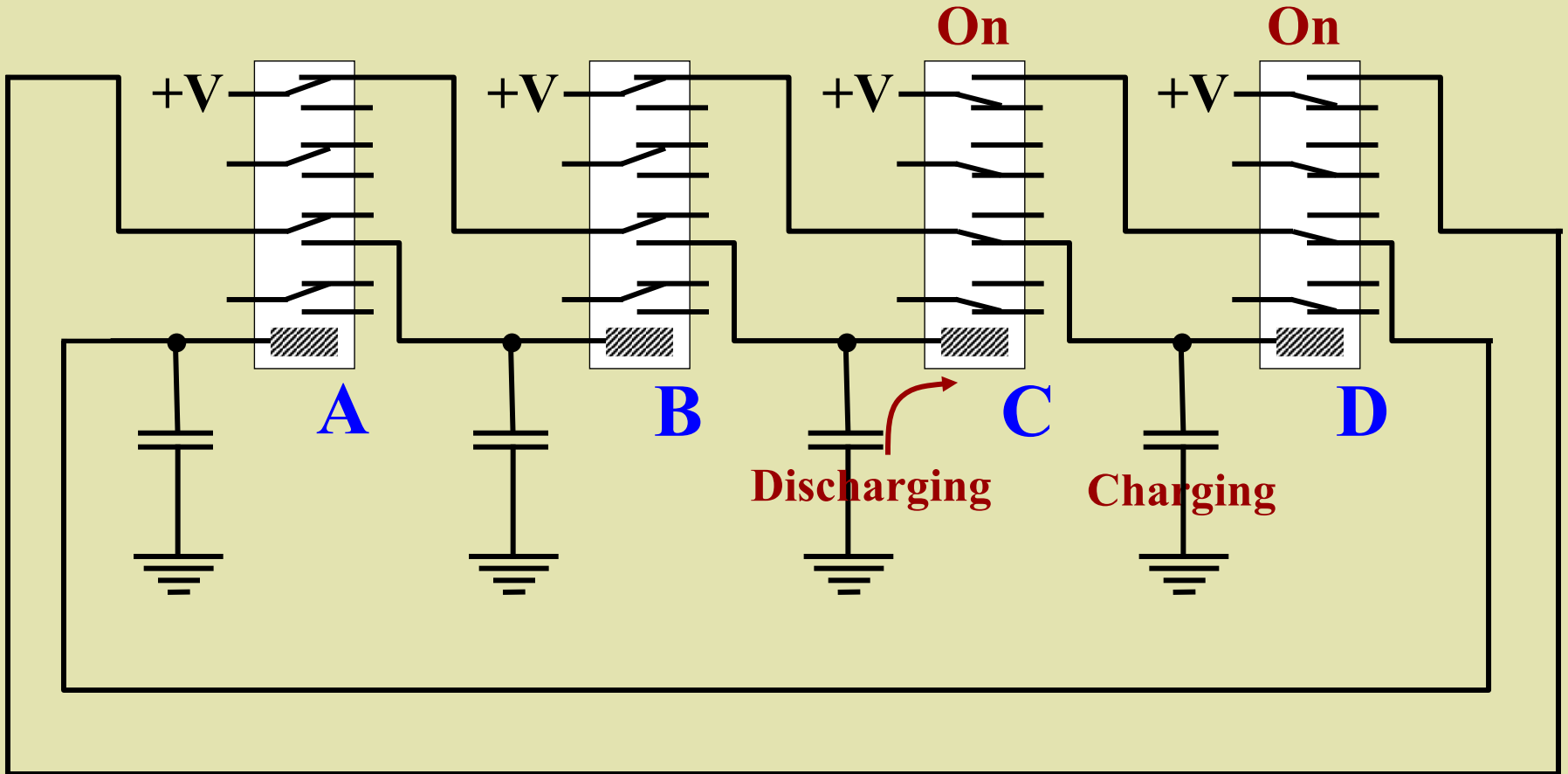


Clock

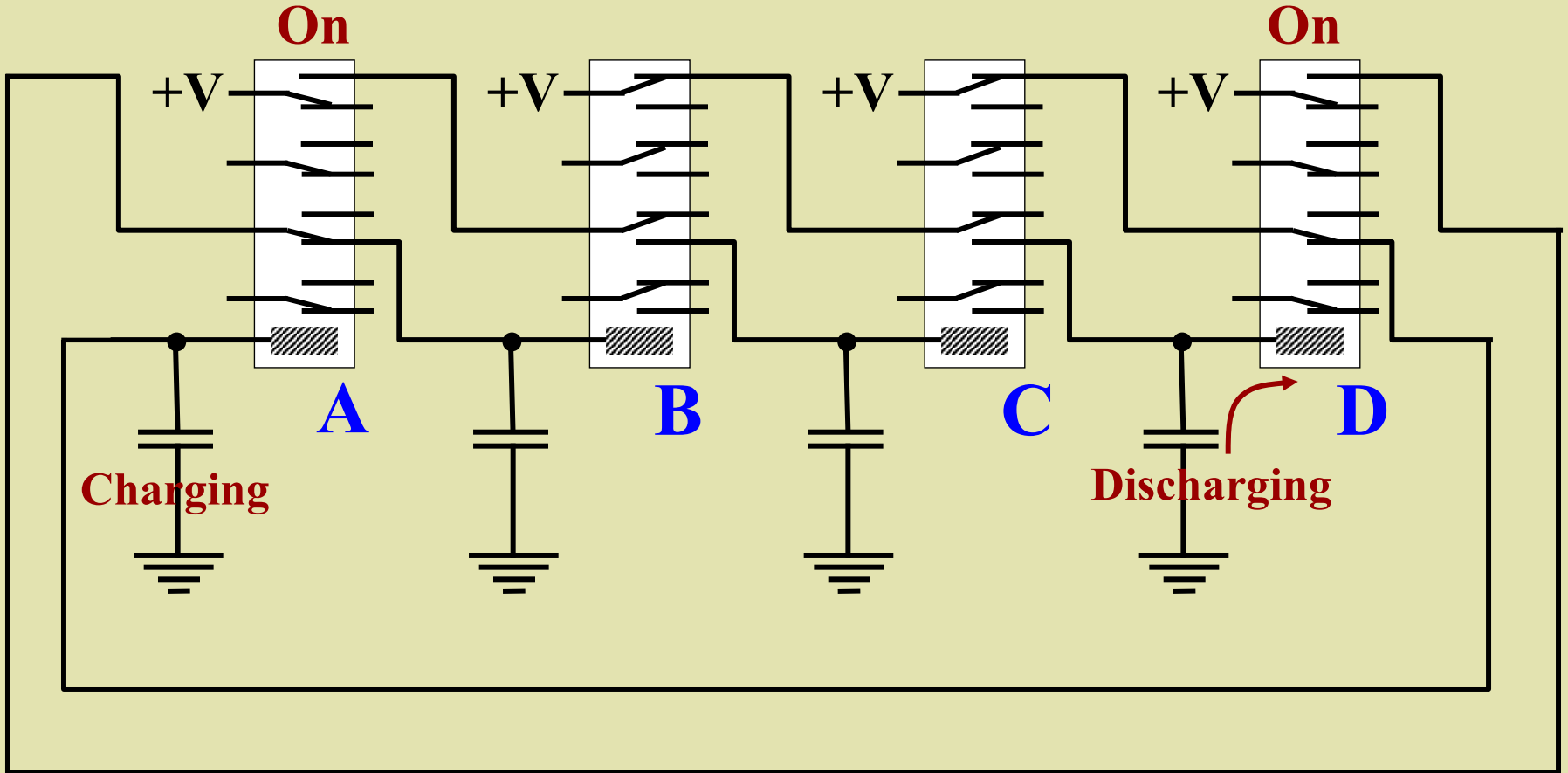


Clock

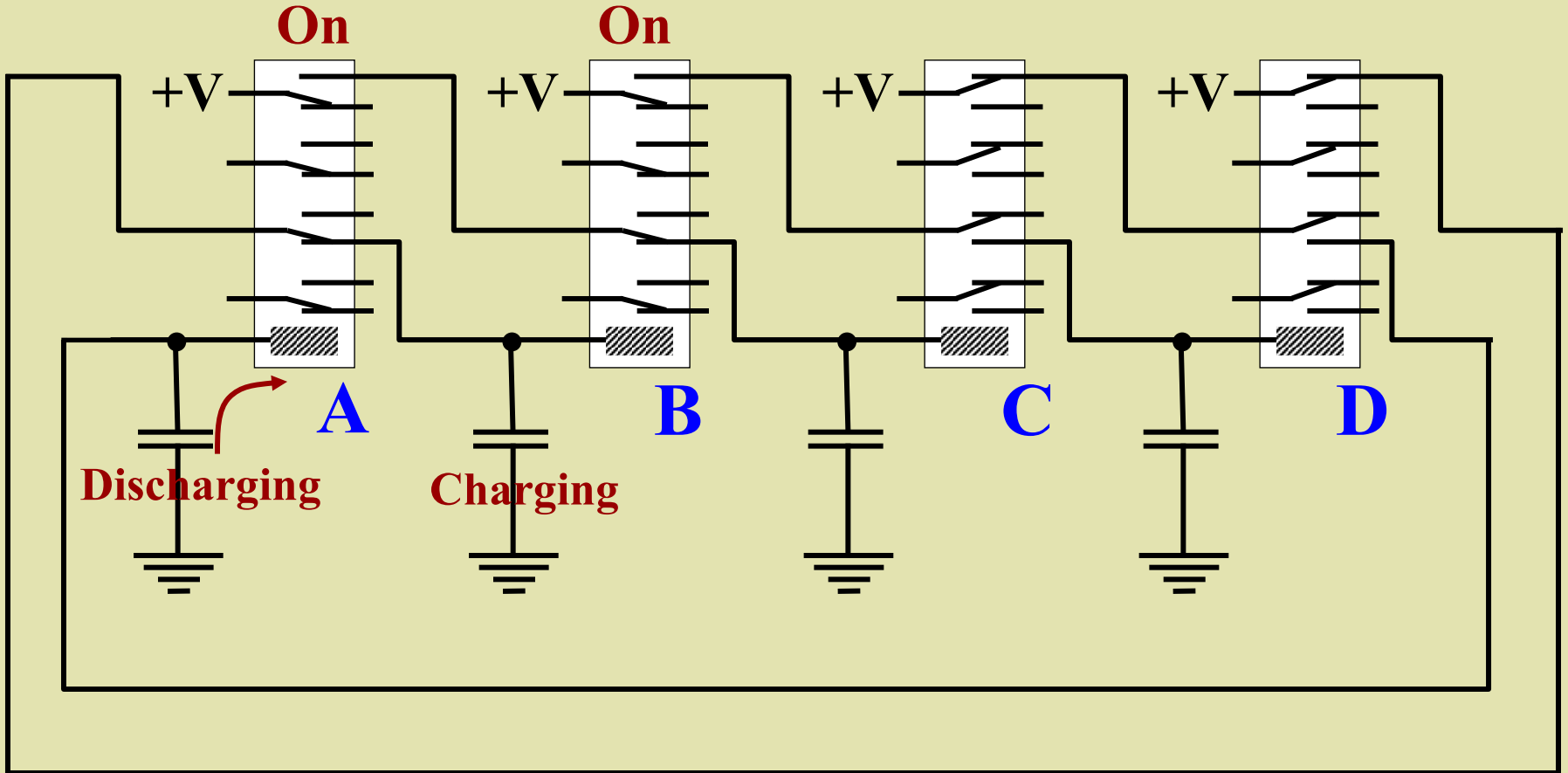


Clock Timing Diagram

 

Clock Timing Diagram

 


Clock Timing Diagram

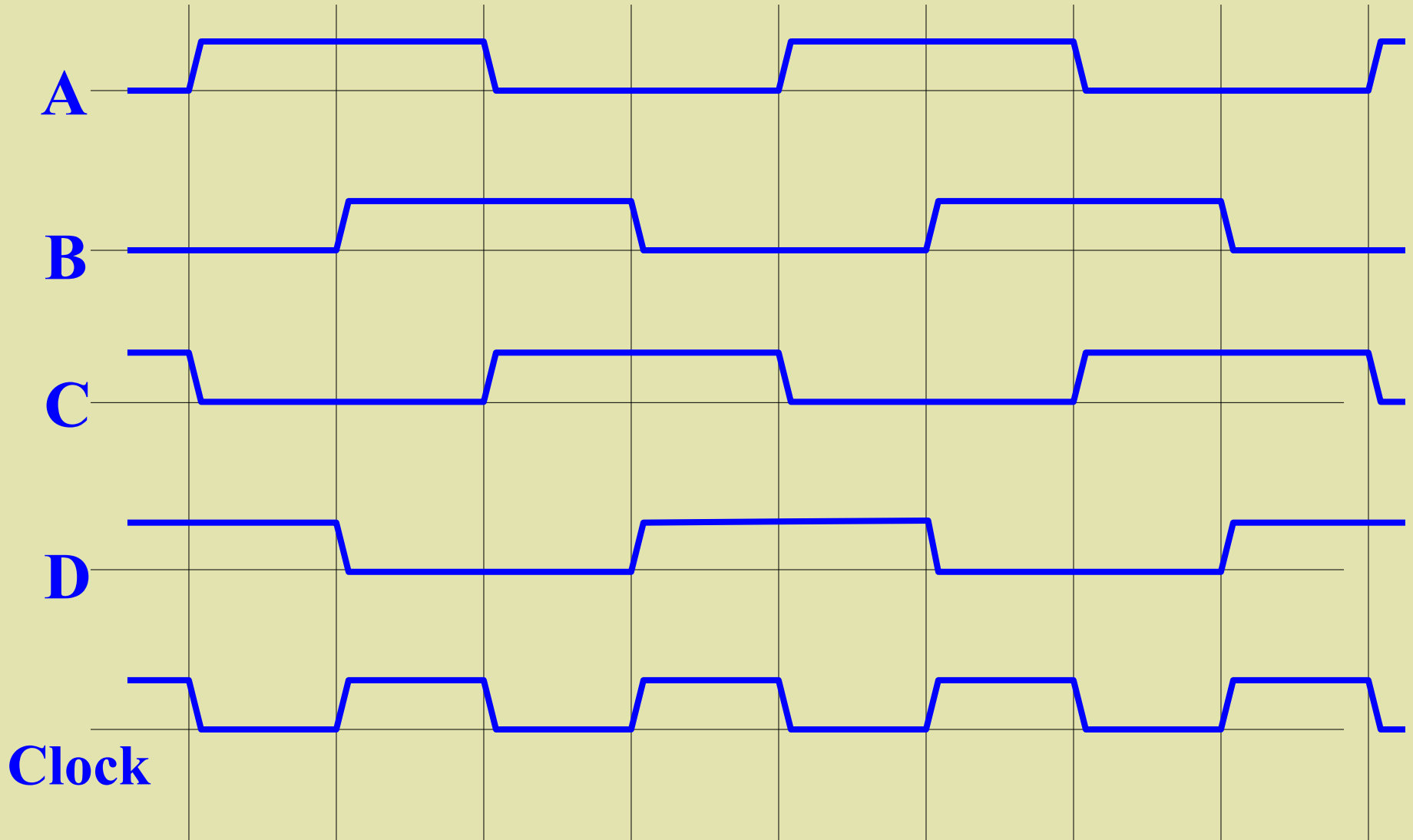


Clock = (A and B) or (C and D)


Finite State Machine

 


Finite State Machine

 


Finite State Machine

 


Finite State Machine

 


Finite State Machine

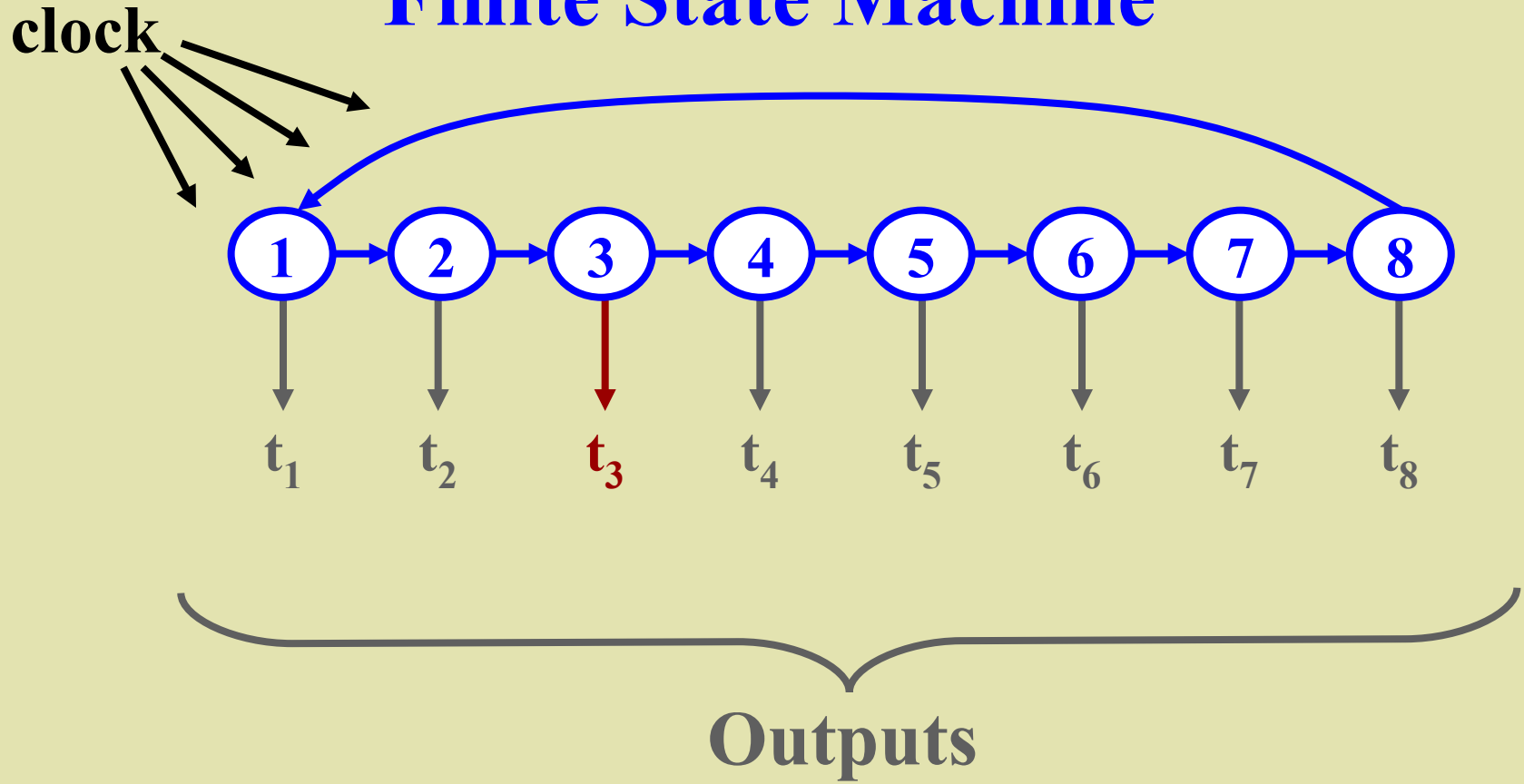


Finite State Machine

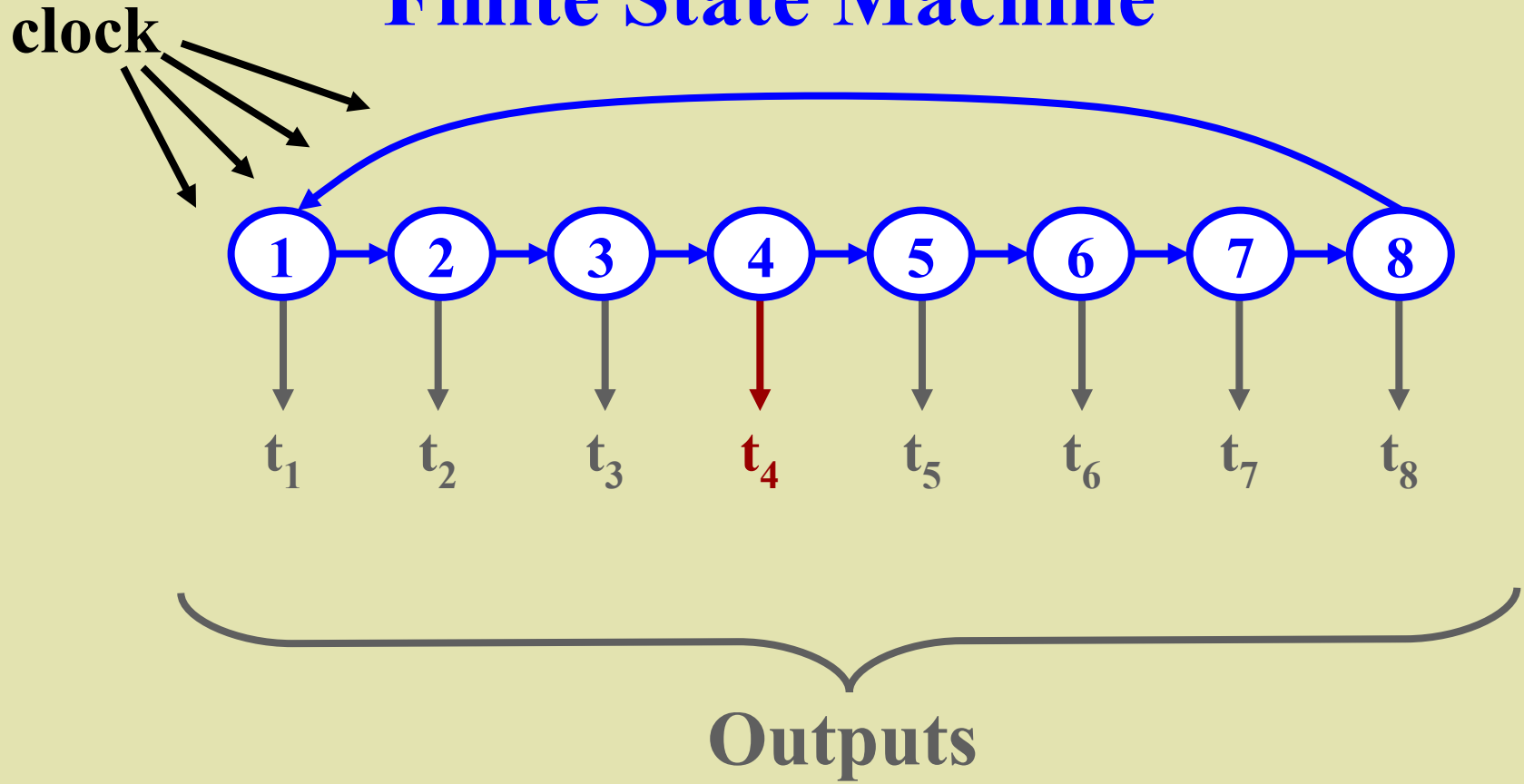


Finite State Machine

 


Finite State Machine

 


Finite State Machine

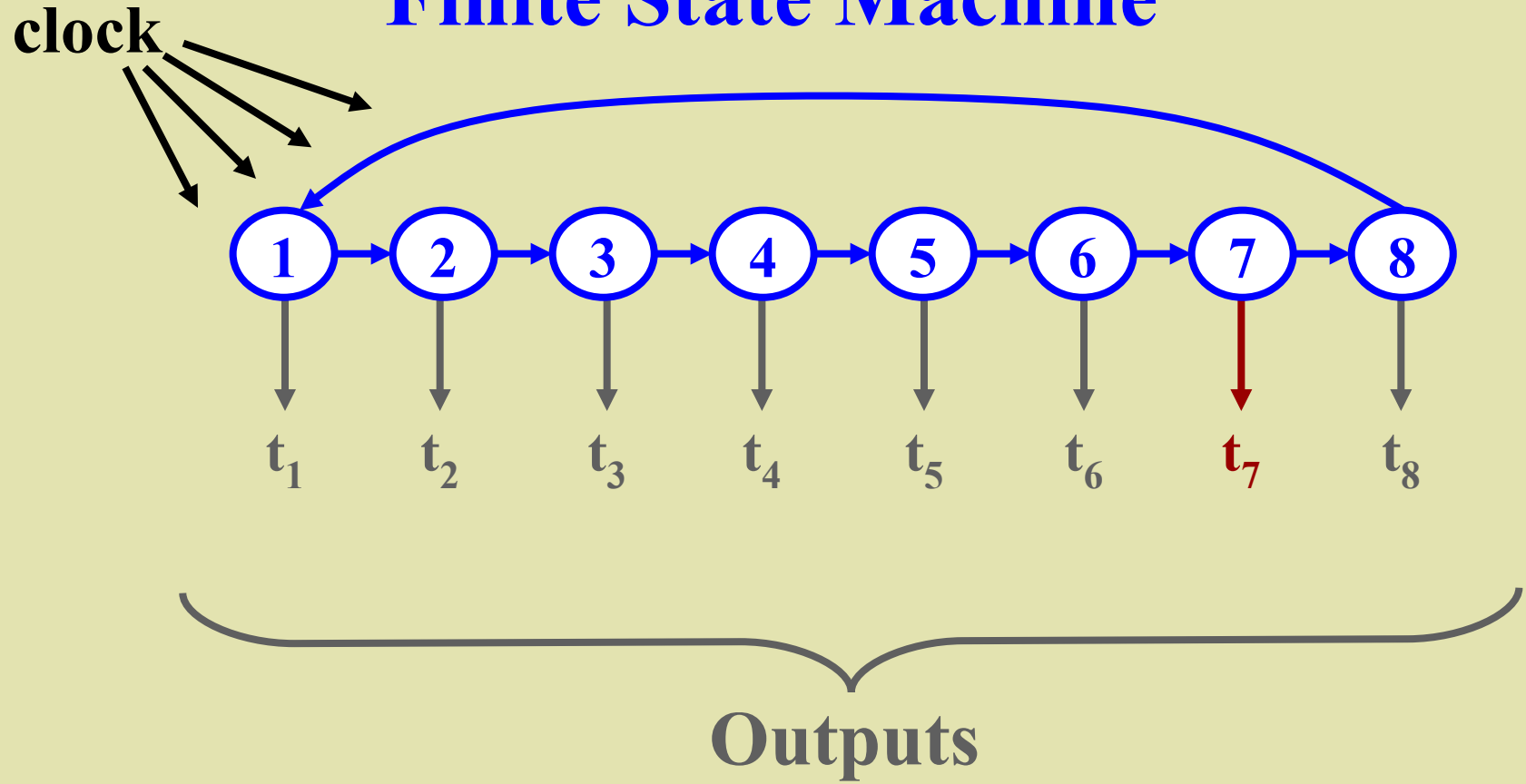


Finite State Machine

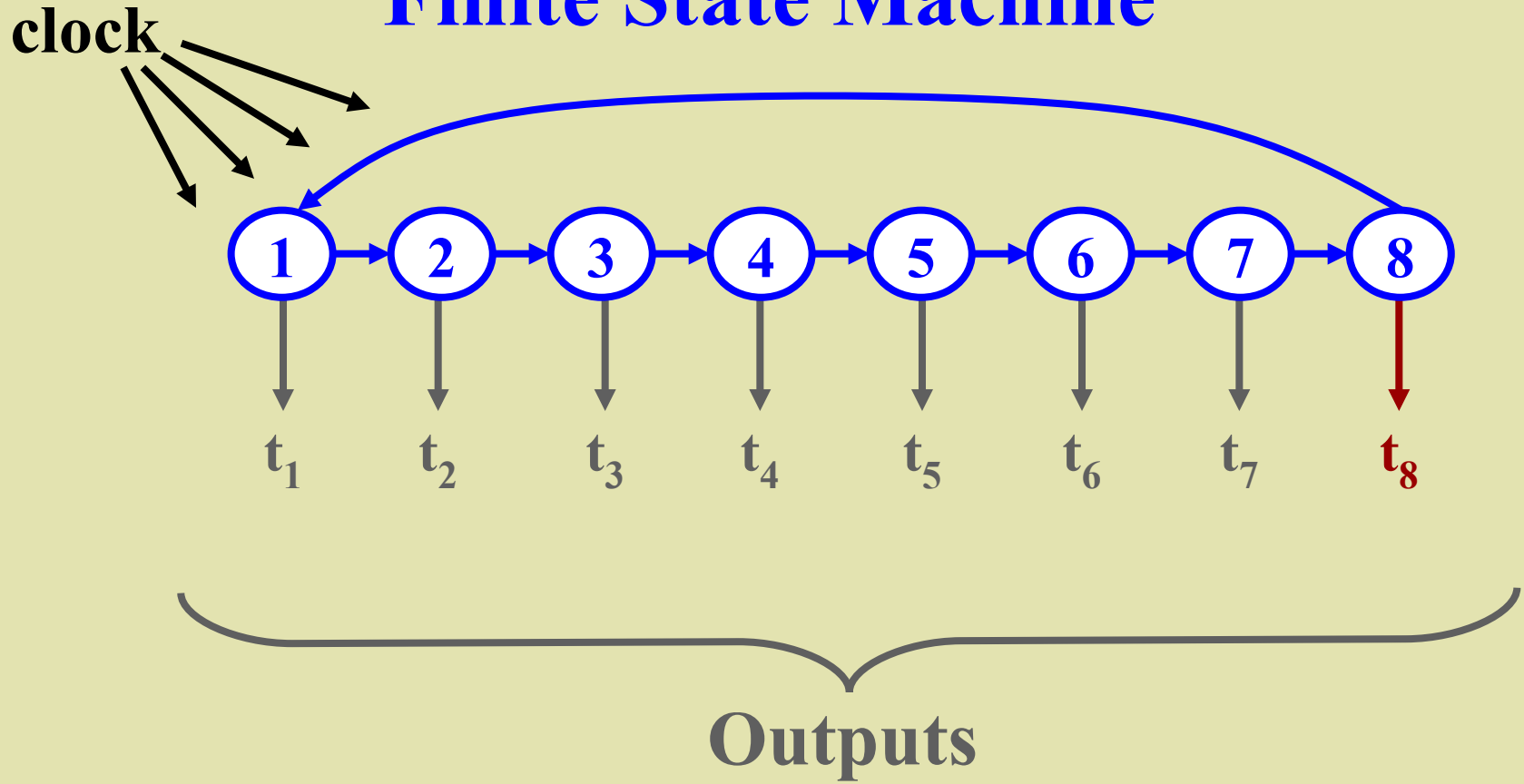


Finite State Machine

 


Output from FSA

 


Instruction Timing - ALU Instruction

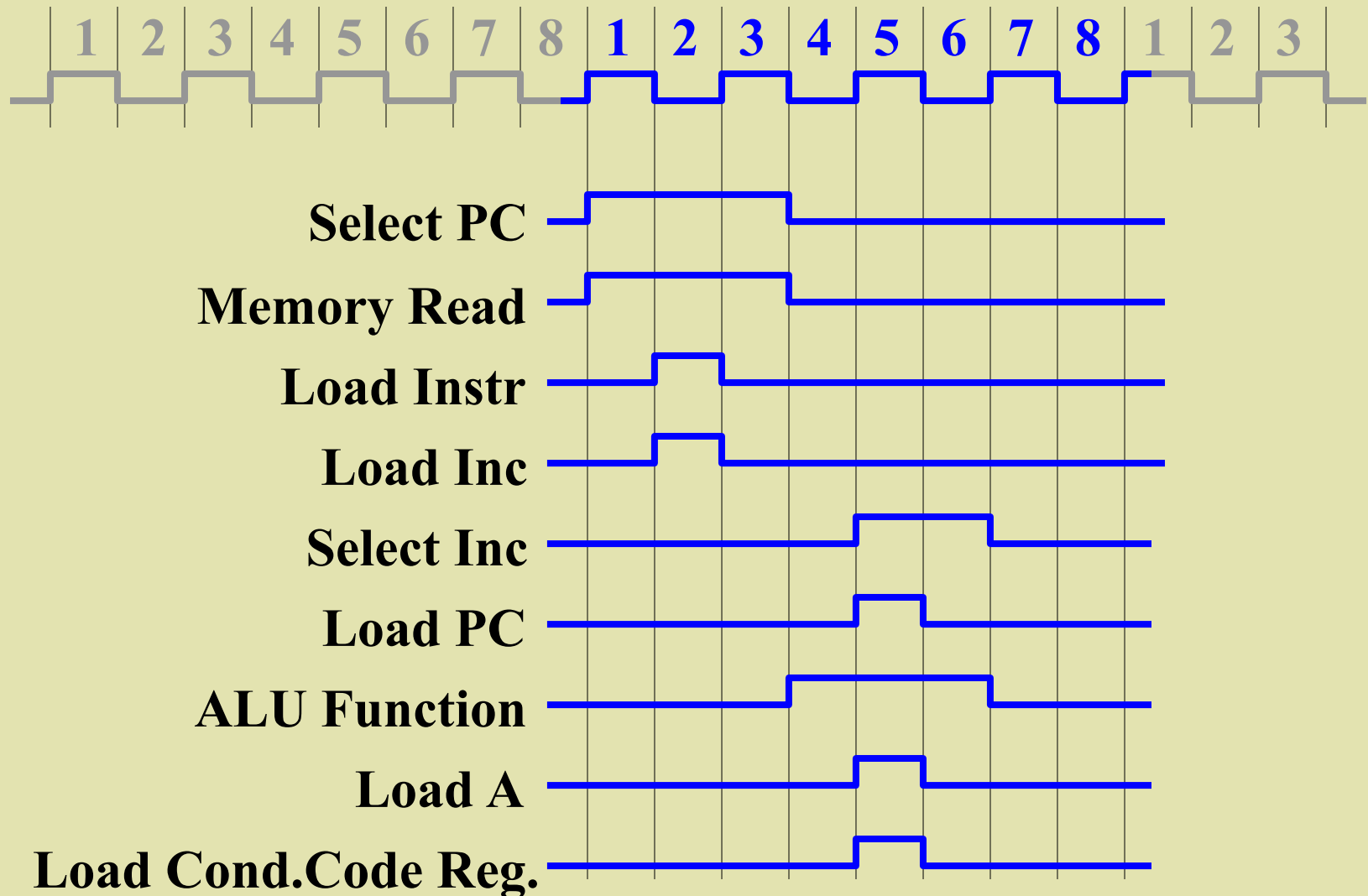


Instruction Timing - ALU Instruction

 



Instruction Timing - ALU Instruction

 

Instruction Timing - ALU Instruction

 


Instruction Decoding

  


Control Signals
(Load, Select, Mem-Read, etc.)


Instruction Decoding

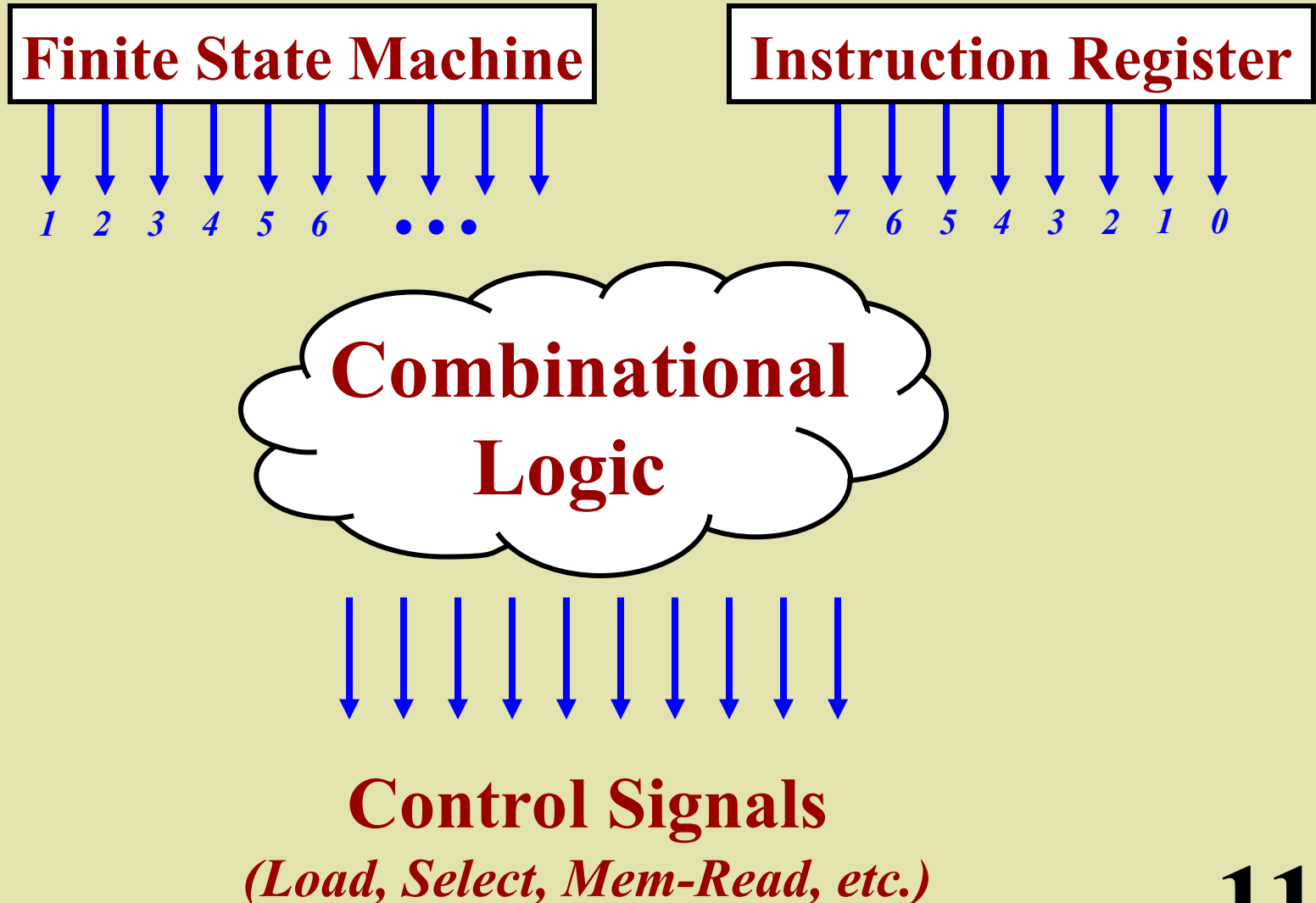


Instruction Timing - 16-bit Move

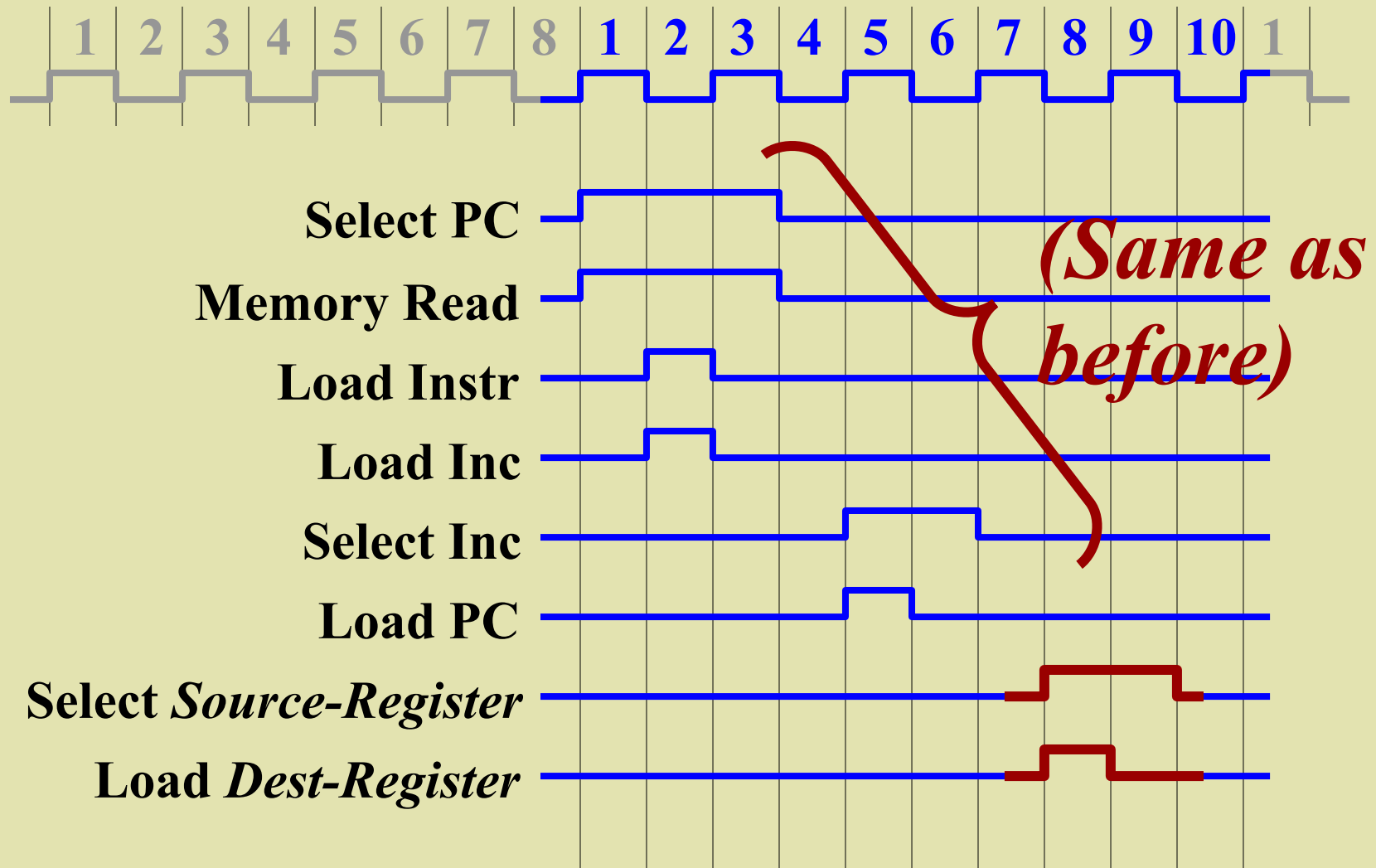


Finite State Machine

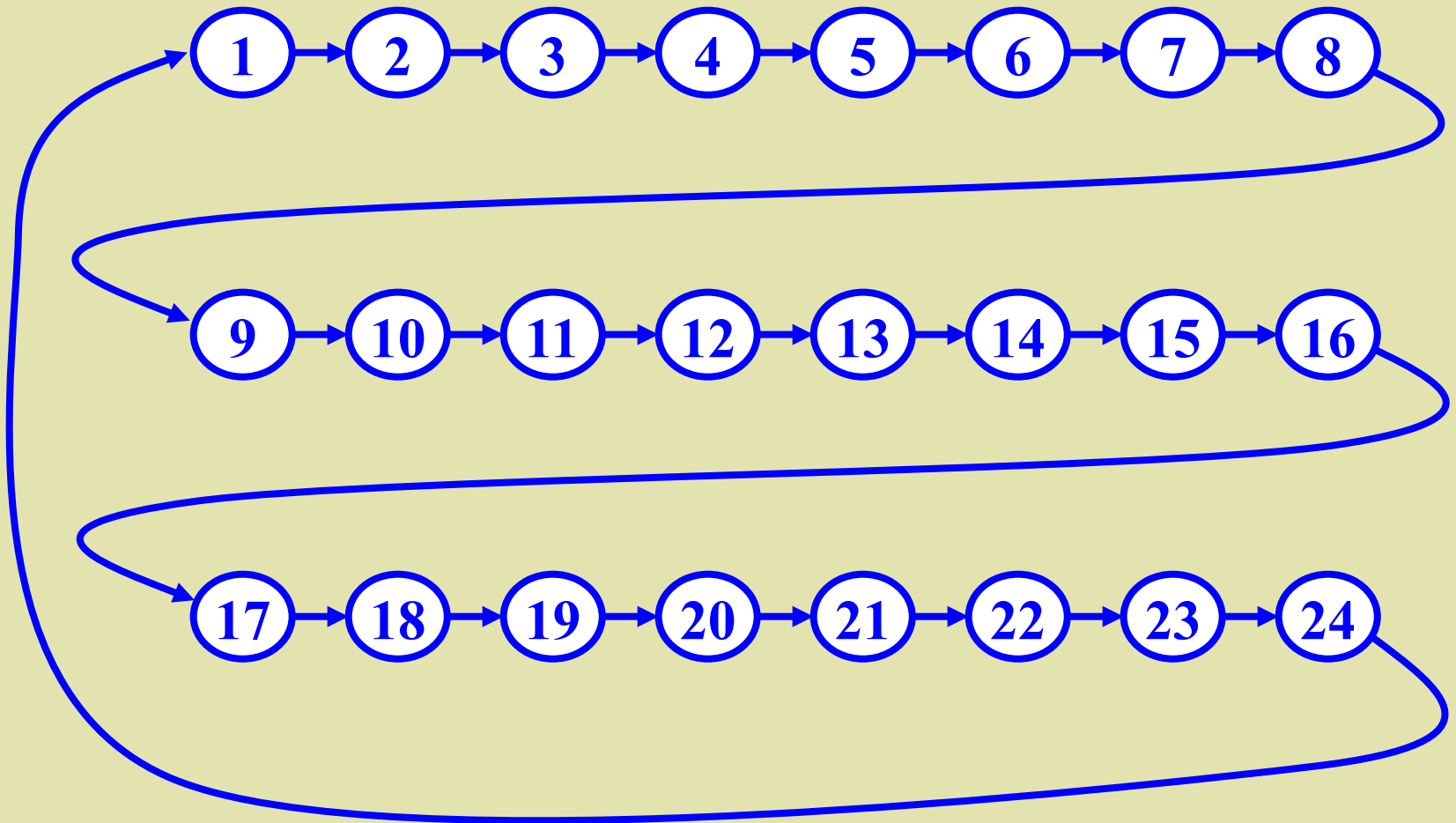

Finite State Machine

 


Instruction Decoding and Control

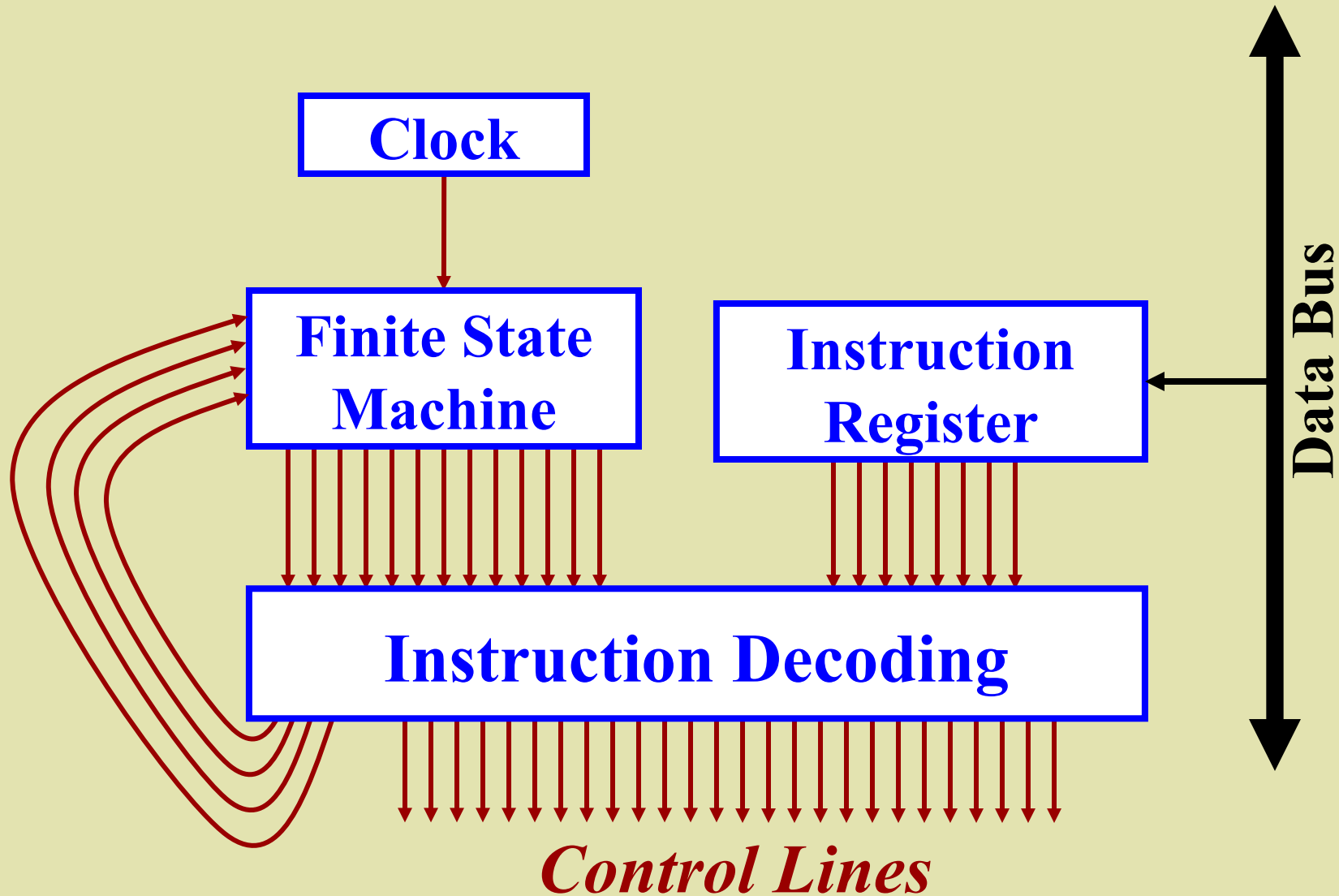

The Instruction Set (1)

Move

 


ddd = destination register

sss = source register

(A, B, C, D, M₁, M₂, X or Y)

ALU

 


r = destination register (A or D)

fff = function code

(add, inc, and, or, xor, not, shl)


Load Immediate

 

r = destination register (A or B)

dddddd = value (-16..15)


16-bit Increment

 

$XY \leftarrow XY + 1$


The Instruction Set (2)

Load

 


rr = destination register (A, B, C, D)
 $\text{reg} \leftarrow [M]$

Store

 


rr = source register (A, B, C, D)
 $[M] \leftarrow \text{reg}$

Load 16-bit Immediate

 


Load the immediate value into M (i.e., M_1 and M_2)

Halt

 


The Instruction Set (3)

Goto

 

Branch to the given address

Call

 


Branch to the given address
Save return location in XY register

Return / Branch Indirect



16-Bit Move

 

d = destination register (PC or XY)
ss = source register (M, XY or J)

The Instruction Set (4)

Branch If Negative

1 1 1 1 0 0 0 0

a a a a a a a a

a a a a a a a a

Branch to the given address if $S = 1$

Branch If Carry

1 1 1 0 1 0 0 0

a a a a a a a a

a a a a a a a a

Branch to the given address if $Cy = 1$

Branch If Zero

1 1 1 0 0 1 0 0

a a a a a a a a

a a a a a a a a

Branch to the given address if $Z = 1$

Branch If Not Zero

1 1 1 0 0 0 1 0

a a a a a a a a

a a a a a a a a

Branch to the given address if $Z = 0$

An Example Program

<u>address</u>	<u>instr</u>	<u>assembly</u>	<u>comment</u>
0000 0000	0011 1001	Y=B	Y ← B
0000 0001	0011 0110	X=0	X ← 0
0000 0010	1000 0101	A=¬B	If sign(Y)==1
0000 0011	1111 0000	BNEG Else	.
0000 0100	0000 0000	.	.
0000 0101	0000 0111	.	.
0000 0110	0011 0010	X=C	X ← C
		Else:	.
0000 0111	0101 1001	A=-7	D ← -7
0000 1000	0001 1000	D=A	.
		Loop:	Loop:
0000 1001	0000 1110	B=X	Shift X left (circular)
0000 1010	1000 0110	A=B<<1	.
0000 1011	0011 0000	X=A	.
0000 1100	0000 1111	B=Y	Shift Y left (circular)
0000 1101	1000 0110	A=B<<1	.
0000 1110	0011 1000	Y=A	.
0000 1111	0000 1111	B=Y	If sign(Y)==1
0001 0000	1000 0101	A=¬B	.
0001 0001	1111 0000	BNEG Else2	.
0001 0010	0000 0000	.	.
0001 0011	0001 0111	.	.
0001 0100	0000 1110	B=X	X ← X + C
0001 0101	1000 0000	A=B+C	.
0001 0110	0011 0000	X=A	.
		Else2:	.
0001 0111	0000 1011	B=D	D ← D + 1
0001 1000	1000 1001	D=B+1	.
0001 1001	1110 0010	BNZ Loop	If D != 0 goto Loop
0001 1010	0000 0000	.	.
0001 1011	0000 1001	.	.
0001 1100	1010 1110	HALT	HALT