



<a href="#">AN501</a>	SGS-THOMSON SLIC KIT AC MODELS
<a href="#">AN502</a>	SGS-THOMSON SLIC KITS AND COMBO II
<a href="#">AN504</a>	SLICS PROTECTION CIRCUITS
<a href="#">AN505</a>	M3488 DIGITAL SWITCHING MATRIX
AN509	* INFLUENCE OF GATE AND BASE DRIVE ON POWER SWITCH BEHAVIOUR
AN510	* CIRCUITS FOR POWER FACTOR CORRECTION WITH REGARDS TO MAINS FILTERING
AN511	* MODULAR DESIGN FOR MULTI-FACTOR SMPS WITH SYNCHRONOUS POST REGULATION
AN512	* CHARACTERISTICS OF POWER SEMICONDUCTORS
AN513	* TOPOLOGIES FOR SWITCH MODE POWER SUPPLIERS
AN514	* HIGH SIDE DRIVERS
AN515	* THE POWER SO-10(TM) - A NEW SURFACE MONT POWER PACKAGE
AN516	* FROM STANDARD TO INTELLIGENT MOSFETS
AN517	* THE VB027- ELECTRONIC IGNITION IN VIPOWER TECHNOLOGY
AN518	* SOFT LIGHT DIMMER
AN519	* PWM TECHNIQUE FOR ACOUSTIC NOISE REDUCTION IN POWER APPLICATIONS
AN520	* HORIZONTAL DEFLECTION IN TVS AND MONITORS
AN521	* AN INTRODUCTION TO IGBTS
AN522	* PULSE CONTROLLED INVERTER
AN523	* UNDERSTANDING POWER FACTOR

*\* To obtain a copy of a document marked with an asterisk, please contact your local Sales Office*



<a href="#">AN524</a>	* DRIVE CIRCUITS FOR POWER MOSFETS AND IGBTs
<a href="#">AN525</a>	* AN INTRODUCTION TO INTELLIGENT POWER
<a href="#">AN526</a>	* PLASTIC PACKAGES FOR POWER DISCRETES AND ICS
<a href="#">AN527</a>	* ELECTRONIC FLOURESCENT LAMP BALLAST
<a href="#">AN528</a>	* ELECTRONIC TRANSFORMER FOR 12V HALOGEN LAMP
<a href="#">AN533</a>	* SCRS AND TRIACS THERMAL MANAGEMENT
<a href="#">AN534</a>	4.5W FLYBACK CONVERTER FOR POWER LINE MODEM APPLICATIONS
<a href="#">AN535</a>	POWER LINE MODEM APPLICATION REMOTE CONTROL USING ST7537 AND ST6
<a href="#">AN536</a>	RAM MAPPING ST75C50
<a href="#">AN537</a>	ST75C502-DEFAULT TONE DETECTORS
<a href="#">AN538</a>	ST75C502-BULK DELAY MANAGEMENT
<a href="#">AN539</a>	ST75C502-RAM MAPPING
<a href="#">AN540</a>	TDA9102C
<a href="#">AN547</a>	CASCADING IMSA110S
<a href="#">AN548</a>	THE IMSA110 BACK-END POST PROCESSOR
<a href="#">AN549</a>	THINNING DIGITAL PATTERNS USING THE IMSA110
<a href="#">AN550</a>	TECHNICAL NOTE TDA9102C SELECTION VS HORIZONTAL DUTY CYCLE
<a href="#">AN551</a>	TEA5750 ASO PLUS
<a href="#">AN553</a>	PROTECTION STANDARD APPLICABLE TO AUTOMOBILES
<a href="#">AN554</a>	CHOICE OF PROTECTION IN AUTOMOTIVE APPLICATIONS
<a href="#">AN555</a>	AUTOMOTIVE PROTECTION WITH THE RBOXX SERIES

*\* To obtain a copy of a document marked with an asterisk, please contact your local Sales Office*



<a href="#">AN557</a>	EASY DESIGNER WITH L4970
AN558	* 150W TV BAND V POWER AMPLIFIER
AN559	* TV LINEAR POWER TRANSISTORS BANDS I,II,III,IV, & V (SD1492)
AN560	* NEW TRANSISTORS FOR THE NEXT GENERATION OF CELLULAR BASE STATIONS (SD1660)
AN561	* DEVICE NOTE #101 WIDE BAND DESIGN OF PULSED POWER UHF AMPLIFIERS (SD1563)
AN562	* DEVICE NOTE #104 BALANCED UHF PULSED AMPLIFIER (SD1565)
AN563	* DEVICE NOTE #105 HIGH POWER UHF PULSED PUSH-PULL
AN564	* POWER TRANSISTORS BALLASTING IMPROVES PERFORMANCE OF SURVEILLANCE RADAR INTERROGATORS AND TRANSPONDERS
AN565	* M.T.F. OF A L-BAND POWER TRANSISTOR UNDER RF CONDITIONS
AN566	* S-BAND TRANSISTORS FOR RADAR APPLICATIONS
AN567	* BIPOLARS READY FOR S-BAND RADAR
AN569	* PHASE MEASUREMENT AND CHARACTERIZATION OF MICROWAVE POWER TRANSISTORS
<a href="#">AN572</a>	TSH150 AND TSH151 DEMOBOARD
<a href="#">AN573</a>	486 COMMON SOCKET IMPLEMENTATION
<a href="#">AN574</a>	TRANSIL-TRISIL COMPARISON
<a href="#">AN575</a>	CALCULATION OF TRANSIL APPARENT DYNAMIC RESISTANCE
<a href="#">AN576</a>	PCB LAYOUT OPTIMISATION
<a href="#">AN577</a>	SURFACE MOUNT DEVICES SOD6 AND SOD15

*\* To obtain a copy of a document marked with an asterisk, please contact your local Sales Office*



<a href="#"><u>AN578</u></a>	POWER CROSSING BEHAVIOUR OF LINE CAR PROTECTION
<a href="#"><u>AN579</u></a>	PROTECTION CONCEPTS IN TELECOMMUNICATIONS EQUIPMENTS
<a href="#"><u>AN580</u></a>	VOLTAGE TO CURRENT WAVEFORM CONVERSION
<a href="#"><u>AN581</u></a>	PROTECTION STANDARDS APPLICABLE TO TERMINALS
<a href="#"><u>AN582</u></a>	PROTECTION SCHEMATICS FOR TELEPHONE SET
<a href="#"><u>AN583</u></a>	PROTECTION STANDARDS APPLICABLE TO SWITCHING EQUIPMENT
<a href="#"><u>AN584</u></a>	PROTECTION SCHEMATICS FOR SWITCHING SYSTEM
<a href="#"><u>AN585</u></a>	ISDN INTERFACE PROTECTION
<a href="#"><u>AN586</u></a>	USE OF TRANSIL AS RECTIFIER DIODES
<a href="#"><u>AN587</u></a>	TRANSISTOR PROTECTION BY TRANSIL
<a href="#"><u>AN588</u></a>	CHOOSING AN ITAXX REQUIRES A SYSTEM APPROACH
<a href="#"><u>AN589</u></a>	CROSSTALK BEHAVIOUR OF ITA25 IN RS232 TRANSMISSION
<a href="#"><u>AN590</u></a>	ST6 - PWM GENERATION WITH ST62 AUTO-RELOAD TIMER
<a href="#"><u>AN591</u></a>	ST6 - INPUT CAPTURE WITH ST62 AUTO-RELOAD CAPTURE
<a href="#"><u>AN592</u></a>	ST6 - PLL GENERATION WITH ST62 AUTO-RELOAD TIMER
<a href="#"><u>AN593</u></a>	ST6 - ST62 IN-CIRCUIT PROGRAMMING
<a href="#"><u>AN594</u></a>	ST6 - DIRECT SOFTWARE LCD DRIVE WITH ST621X AND ST626X
<a href="#"><u>AN595</u></a>	ST6 - FUZZY VACUUM CLEANER USING ST6220 AND FUZZYTECH ST6 EXPLORER
<a href="#"><u>AN597</u></a>	ST6 - TEMPERATURE CONTROL USING FUZZY LOGIC
<a href="#"><u>AN598</u></a>	ST6 - CASCADING FUZZY MODULES WITH ST6 FUZZYTECH

*\* To obtain a copy of a document marked with an asterisk, please contact your local Sales Office*



AN599

## PARALLEL OPERATION OF FAST RECTIFIERS