



- AN813 \* TRANSISTORIZED POWER SWITCHES WITH IMPROVED EFFICIENCY
- [AN814](#) V.17 FAX EQUIPMENT REPLACING THE R144EFX WITH THE ST75C52/520
- [AN815](#) A STEREO AUDIO SOLUTION FOR MULTIMEDIA APPLICATIONS USING TWO ST7546 A/D AND D/A CONVERTERS
- [AN816](#) SET-UP, HANDSHAKE AND COMMUNICATION MONITORING IN MODEM AND FAX MODE WITH THE ST75C502
- [AN819](#) CAPACITIVE DISCHARGE IGNITION
- [AN820](#) INPUT/OUTPUT PROTECTION FOR AUTOMOTIVE COMPUTER
- [AN821](#) NEW LAYOUT INSULATION REQUIREMENT
- [AN822](#) COMPUTATION OF TONE DETECTOR COEFFICIENTS USING TD SOFTWARE FOR ST75C502
- [AN823](#) ST75C52/ST75C520-SINGLE ENDED AND SINGLE POWER SUPPLY HYBRID CIRCUIT
- [AN824](#) UNDERSTANDING POWER FACTOR
- [AN825](#) PFC APPLICATION IDEAS USING MAINS TRANSFORMER
- [AN826](#) 250W HIGH POWER FACTOR SUPPLY FOR TV
- [AN827](#) A 500W HIGH POWER FACTOR WITH THE L4981A CONTINUES MODE IC
- [AN828](#) 1500W-440V POWER FACTOR CORRECTOR PREREGULATOR
- [AN829](#) SEMICONDUCTOR KIT FOR POWER FACTOR CORRECTOR
- [AN830](#) L6560/A PFC IN LAMP BALLAST APPLICATIONS
- [AN831](#) MAGNETIC SNUBBER FOR 200W PFC WITH UNIVERSAL MAINS

*\* To obtain a copy of a document marked with an asterisk, please contact your local Sales Office*



<a href="#">AN832</a>	L4981A SYNCHRONIZATION
<a href="#">AN833</a>	FREQUENCY MODULATION ON L4981B
<a href="#">AN835</a>	486 / 5X86 MOTHERBOARD CONFIGURATION GUIDELINES
<a href="#">AN836</a>	LOW FORWARD VOLTAGE SCHOTTKY DIODE
<a href="#">AN837</a>	ALTERNATOR LOAD DUMP PROTECTION WITH APC CONCEPT
<a href="#">AN838</a>	STV0042/STV0056 APPLICATION NOTE
<a href="#">AN839</a>	ST6 - ANALOG MULTIPLE KEY DECODING USING THE ST6-REALIZER
<a href="#">AN840</a>	ST6 - CODED LOCK USING THE ST6-REALIZER
<a href="#">AN841</a>	ST6 - A CLOCK DESIGN USING THE ST6-REALIZER
<a href="#">AN842</a>	ST6 - 7 SEGMENT DISPLAY DRIVE USING THE ST6-REALIZER
<a href="#">AN843</a>	ST9 - BANKSWITCH AND GNU C EXAMPLE
<a href="#">AN846</a>	TEA7088A - TELEPHONE SET DEVICE
<a href="#">AN847</a>	ST5080 ST5090 DEMOTOOL
<a href="#">AN848</a>	TEA7092 - TELEPHONE SET INTEGRATED CIRCUIT
<a href="#">AN849</a>	SPEECH AND DIALLER L3914A/16A AND ST3947A/B
<a href="#">AN850</a>	TS3V555 - A LOW COST 2V TO 5V STEP UP CONVERTER
<a href="#">AN851</a>	SAMPLES AND HOLD USING TSH94 AND STANDBY MODE
<a href="#">AN852</a>	SIGNAL MULTIPLEXING USING TSH94 STANDBY MODE
<a href="#">AN853</a>	HIGH SIDE DRIVING WITH TD310
<a href="#">AN854</a>	VOLTAGE QUADRUPLER USING TD310
<a href="#">AN855</a>	TSH94 - VIDEO TRANSCEIVER WITH REMOTE CONTROL

*\* To obtain a copy of a document marked with an asterisk, please contact your local Sales Office*



<a href="#">AN856</a>	TRIPLE GALVANIC INSULATED HIGH SIDE DRIVING WITH TD310
<a href="#">AN857</a>	TS912 - DRIVING A PIEZOELECTRIC CELL WITH A RAIL TO RAIL OP-AMPS
<a href="#">AN858</a>	SCRS AND TRIACS DICE
<a href="#">AN859</a>	ST6 - AN INTELLIGENT ONE HOUR MULTICHARGER FOR LI-ION, NIMH AND NICD BATTERIES
<a href="#">AN860</a>	ST20 - REAL-TIME KERNELS ON THE ST20
<a href="#">AN862</a>	ST9 - ST9058 MICROCONTROLLER PLL CLOCK APPLICATION NOTE AND DEMOBOARD
<a href="#">AN863</a>	ST6 - IMPROVED SENSORLESS CONTROL WITH THE ST62 MCU FOR UNIVERSAL MOTOR
<a href="#">AN865</a>	ST6X86 AND PENTIUM BUS DIFFERENCES
<a href="#">AN866</a>	ST6X86 THERMAL DESIGN CONSIDERATIONS
<a href="#">AN867</a>	6X86 BIOS WRITER'S GUIDE
<a href="#">AN869</a>	TJ MAX LIMIT OF SCHOTTKY DIODE
<a href="#">AN871</a>	LOW FORWARD VOLTAGE SCHOTTKY DIODE
<a href="#">AN872</a>	VIDEO DISTRIBUTOR TSH10/TSH11/TSH150/TSH151
<a href="#">AN873</a>	AUDIO LINE DRIVER TSH22
<a href="#">AN874</a>	HIGH FREQUENCIES DAMPER DIODE
<a href="#">AN875</a>	FUZZY PROGRAMMABLE BOARD W.A.R.P.2.0 GENERAL PURPOSE APPLICATION BOARD
<a href="#">AN876</a>	STV0117A APPLICATION NOTE
<a href="#">AN877</a>	TURBOSWITCH IN AN ASYNCHRONOUS MOTOR DRIVE
<a href="#">AN879</a>	STI3520A PLL



<a href="#">AN880</a>	THE L6569: A NEW HIGH VOLTAGE IC DRIVER FOR ELECTRONIC LAMP BALLAST
<a href="#">AN881</a>	LOW COST ACTIVE CLAMP FOR HIGH FREQUENCY APPLICATIONS
<a href="#">AN883</a>	A MINI GUIDE TO THE APPLICATION NOTE INDEX IN THE 8-BIT MCUS BULLETIN BOARD SYSTEM
<a href="#">AN884</a>	ST62XX APPLICATION NOTES ABSTRACTS BY TOPIC
<a href="#">AN885</a>	ST6 - MICROCONTROLLERS DRIVE HOME APPLIANCE MOTOR TECHNOLOGY
<a href="#">AN886</a>	MCUS - SELECTING BETWEEN ROM AND OTP FOR A MICROCONTROLLER
<a href="#">AN887</a>	MCUS - MAKING IT EASY WITH MICROCONTROLLERS
<a href="#">AN888</a>	STV0196 - DIGITAL SATELLITE RECEIVER LINK I.C.
<a href="#">AN889</a>	25W OFF-LINE AUTORANGING BATTERY CHARGER WITH L4990
<a href="#">AN890</a>	300W SECONDARY CONTROLLED TWO-SWITCH FORWARD CONVERTER WITH L4990
<a href="#">AN891</a>	SMPS WITH L4990 FOR MULTISYNC MONITORS
<a href="#">AN895</a>	A VOLTAGE SUPERVISOR USING THE TSM101
<a href="#">AN896</a>	A BATTERY CHARGER USING THE TSM101
<a href="#">AN897</a>	A LINEAR BATTERY CHARGER USING THE TSM101
<a href="#">AN898</a>	MCUS - EMC GENERAL INFORMATION